

# Electrical Level 1



Electrical Theory 26104-14



# Objectives

**When trainees have completed this lesson, they should be able to do the following:**


1. Explain the basic characteristics of combination circuits.
2. Calculate, using Kirchhoff's voltage law, the voltage drop in series, parallel, and series-parallel circuits.
3. Calculate, using Kirchhoff's current law, the total current in parallel and series-parallel circuits.
4. Using Ohm's law, find the unknown parameters in series, parallel, and series-parallel circuits.

This is a knowledge-based module; there are no Performance Tasks.



# 1.0.0 – 2.1.0

## Introduction; Resistive Circuits


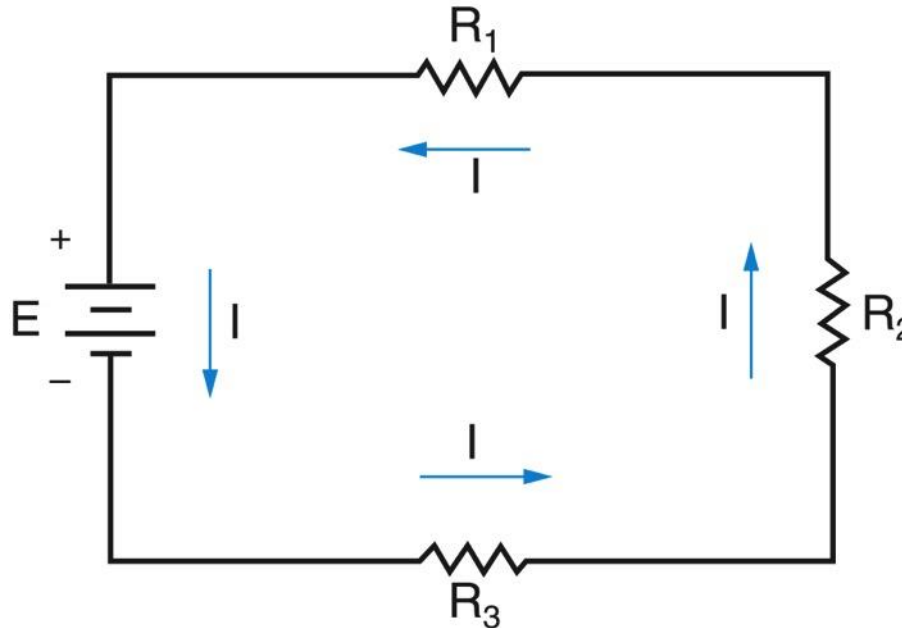


26104-14\_F01.EPS

- A series circuit contains only one path for current flow.
- In a series circuit, the current is equal at each point in the circuit.

# 1.0.0 – 2.1.0

## Total Resistance

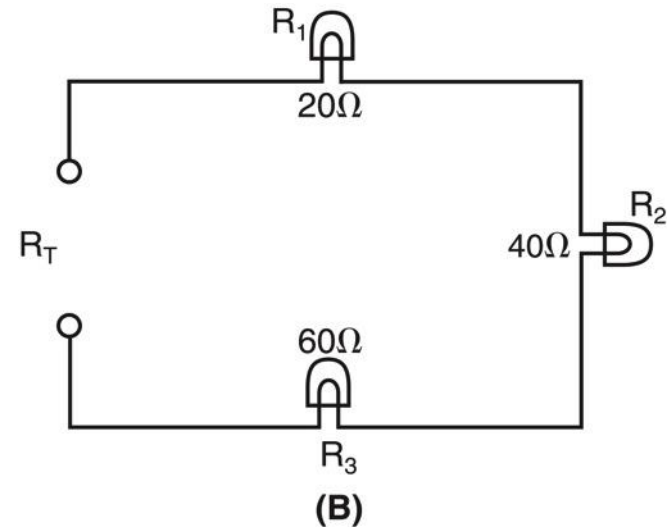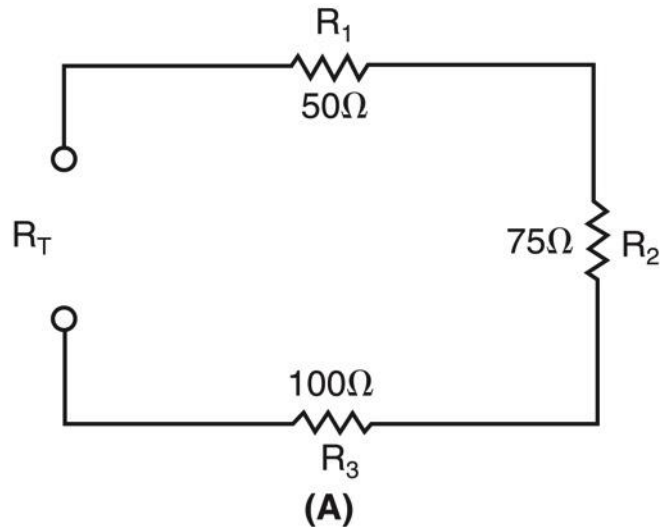

26104-14\_F02.EPS

- In a series circuit, the total resistance is equal to the sum of the individual resistances.
- In the circuits shown here, the total resistance is:  
Circuit A,  $50\Omega + 75\Omega + 100\Omega = 225\Omega$   
Circuit B,  $20\Omega + 40\Omega + 60\Omega = 120\Omega$

## 2.2.0 – 2.1.0


# Resistances in Parallel

- In a parallel circuit, the resistance is calculated by dividing the sum of the inverse values of the individual resistances by one:

$$\frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}}$$

- In the circuit shown, the total resistance is :

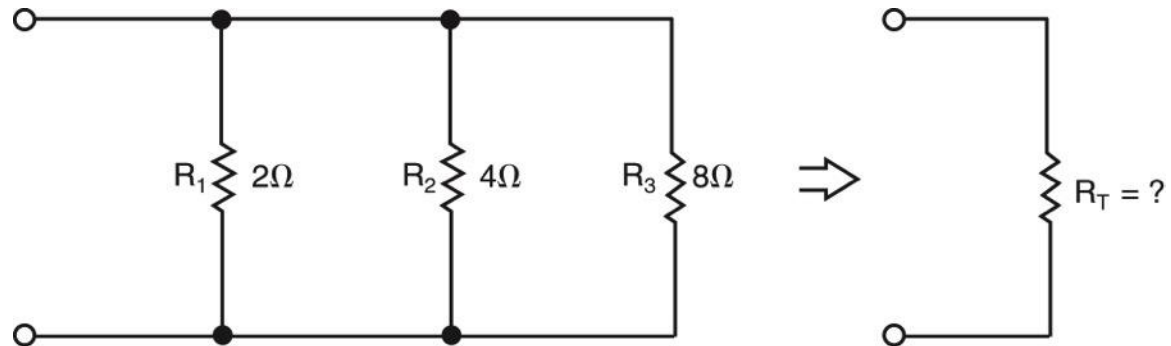
$$\begin{aligned} \frac{1}{\frac{1}{2} + \frac{1}{4} + \frac{1}{8}} &= \\ \frac{1}{0.5 + 0.25 + 0.125} &= \\ \frac{1}{0.875} &= 1.14\Omega \end{aligned}$$



26104-14\_F03.EPS

## 2.2.1

# Simplified Formulas

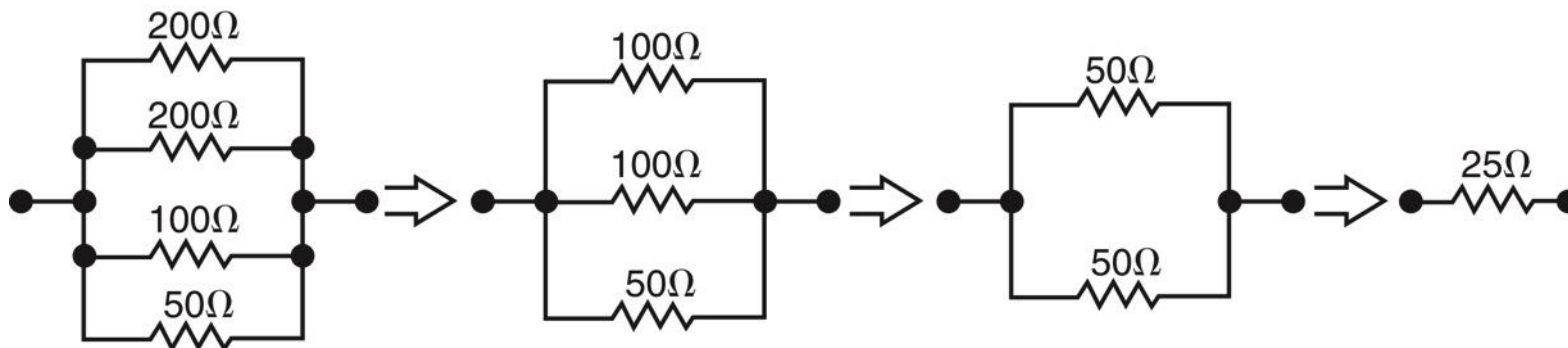


26104-14\_F04.EPS

- The total resistance of equal resistors in parallel is found by dividing the resistance of each resistor by the number of resistors ( $R_T = R/N$ ).
- The total resistance of two unequal resistors in parallel is found by multiplying the values of the two resistors and then dividing the sum of the two resistances:


$$R_T = \frac{R_1 \times R_2}{R_1 + R_2}$$

## 2.3.0


# Series-Parallel Circuits

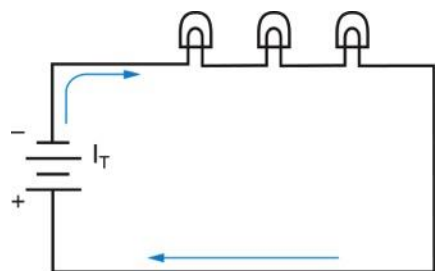

SERIES CIRCUIT

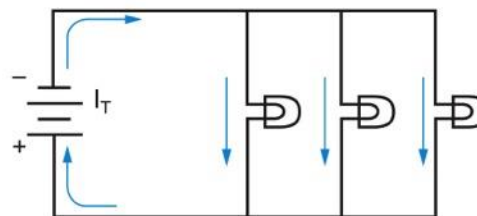

PARALLEL CIRCUIT

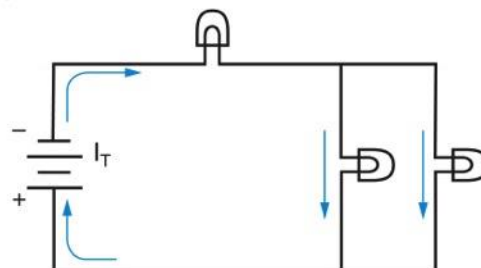

SERIES-PARALLEL CIRCUIT

CURRENT FLOW





26104-14\_F05.EPS

- If a circuit does not divide, it is a series circuit.
- If a circuit divides into separate branches, it is a parallel circuit.
- If a circuit divides into separate branches and there are also series loads, it is a series-parallel circuit.

## 2.3.0
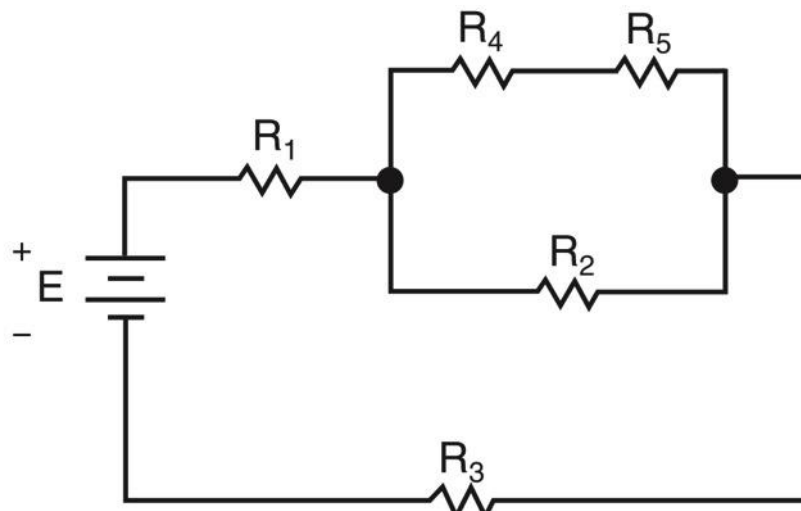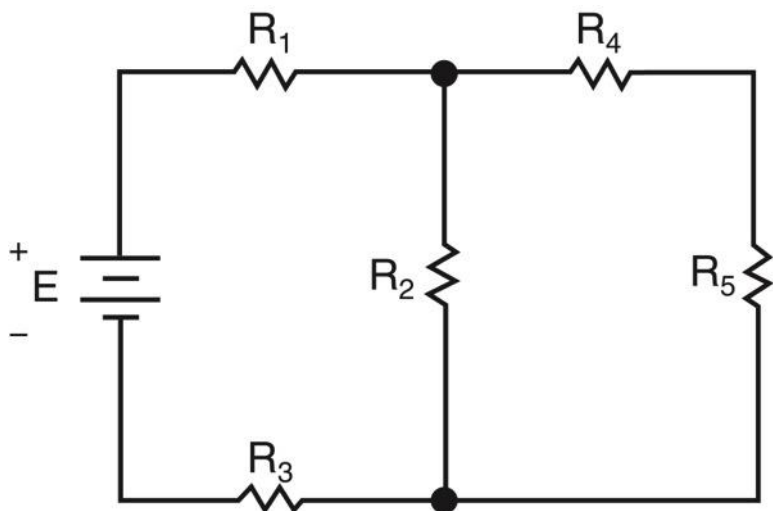
# Redrawing a Series-Parallel Circuit

Series-parallel circuits can be redrawn to separate the series and parallel components.




26104-14\_F06.EPS

## 2.3.0

# Next Session... Series-Parallel Circuits

To calculate the total resistance in a series-parallel circuit, first calculate the effective resistance of the parallel component, then add it to the resistance of the series loads.

## Applying Ohm's Law

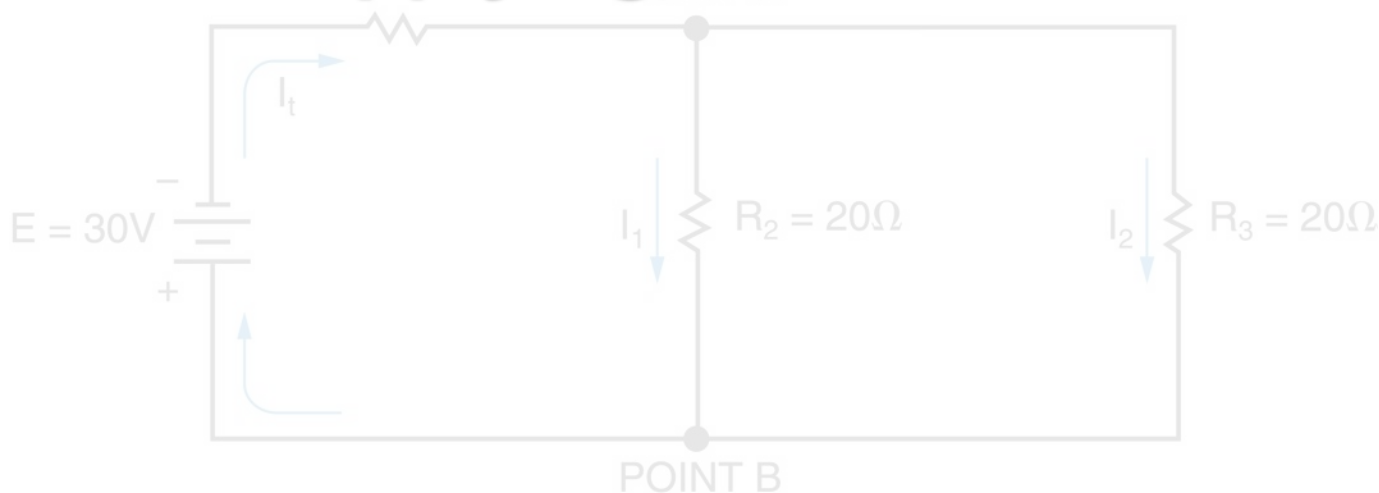


26104-14\_F07.EPS



## 2.4.0 – 2.4.1
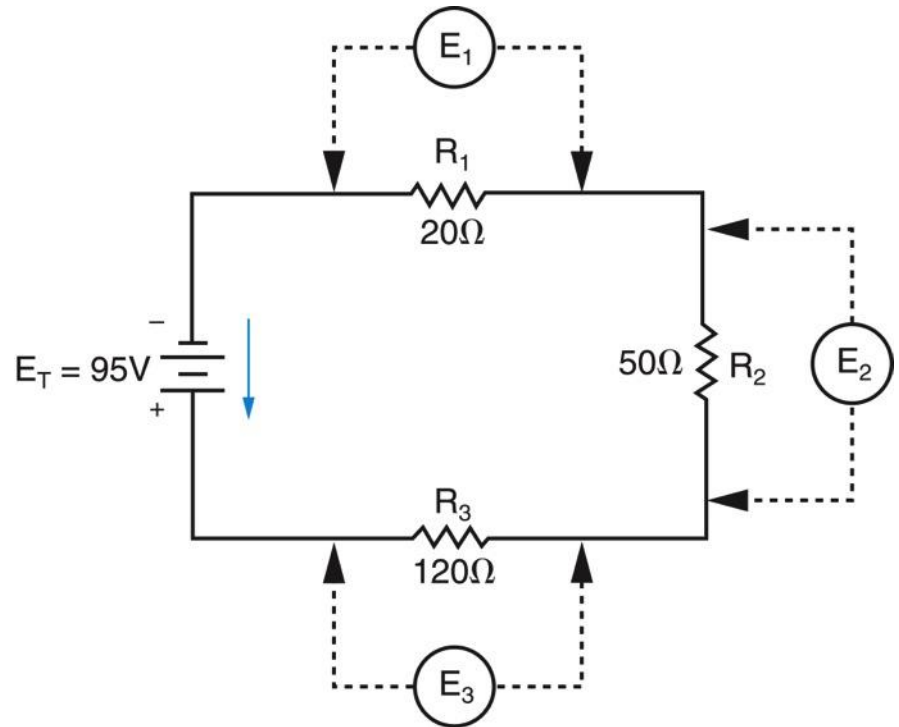
# Applying Ohm's Law


- To find the voltage across individual resistors, first calculate the total resistance in the circuit.
- Next, use the total resistance in the Ohm's Law equation ( $E = IR$ ) to find the individual voltage drops.



26104-14\_F08.EPS

## 2.4.2
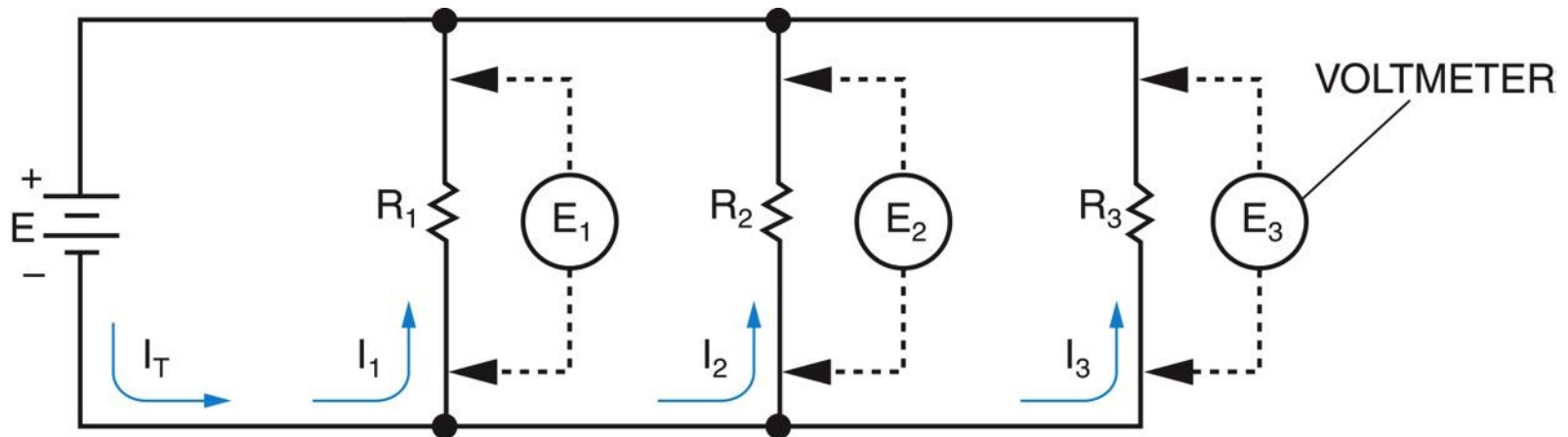
# Voltage and Current in Parallel Circuits





26104-14\_F09.EPS

- In a parallel circuit, the total current is equal to the sum of the branch currents.
- The branch current is equal to the applied voltage divided by the resistance of that branch.

## 2.4.2

# Solving for an Unknown Current

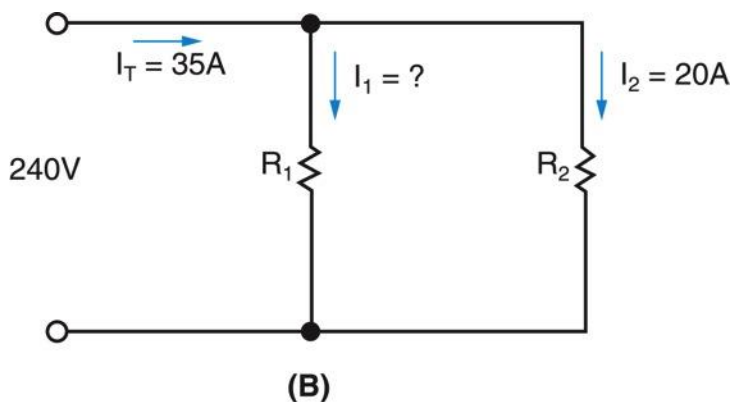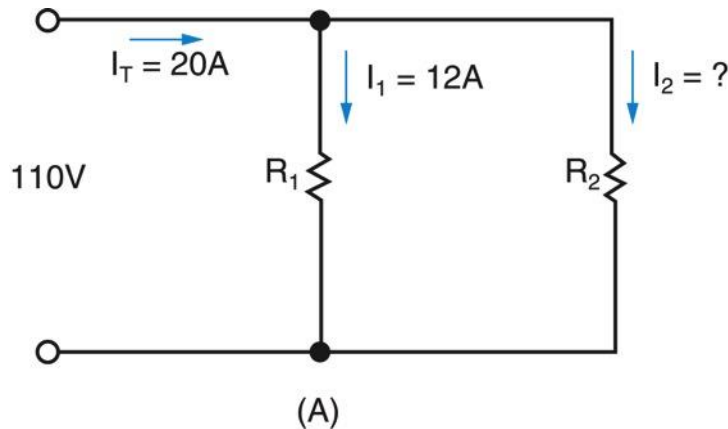

- The current in branch  $R_2$  in Circuit A can be calculated as follows:

$$I_T = I_1 + I_2$$

- Rearrange to find  $I_2$ :

$$I_2 = I_T - I_1$$

$$I_2 = 20\text{A} - 12\text{A} = 8\text{A}$$

- The current in branch  $R_1$  in Circuit B can be calculated as follows:

$$I_T = I_1 + I_2$$

- Rearrange to find  $I_1$ :


$$I_1 = I_T - I_2$$

$$I_1 = 35\text{A} - 20\text{A} = 15\text{A}$$

26104-14\_F10.EPS

## 2.4.3
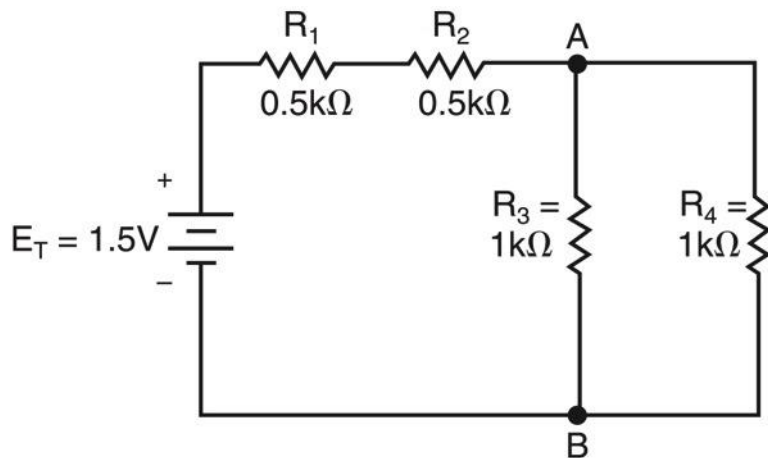
# Voltage and Current in Series-Parallel Circuits



26104-14\_F11.EPS

- The series resistance is found by adding  $R_1 + R_2$ :

$$R_{1+2} = R_1 + R_2$$

$$R_{1+2} = 0.5k\Omega + 0.5k\Omega$$

$$R_{1+2} = 1k\Omega$$

- Calculate the resistance of  $R_3 + R_4$  using either the general reciprocal formula or the product over sum method, as shown here:


$$R_{3+4} = \frac{R_1 \times R_2}{R_1 + R_2}$$

$$R_{3+4} = \frac{1k\Omega \times 1k\Omega}{1k\Omega + 1k\Omega}$$

$$R_{3+4} = 0.5k\Omega$$

## 2.4.3
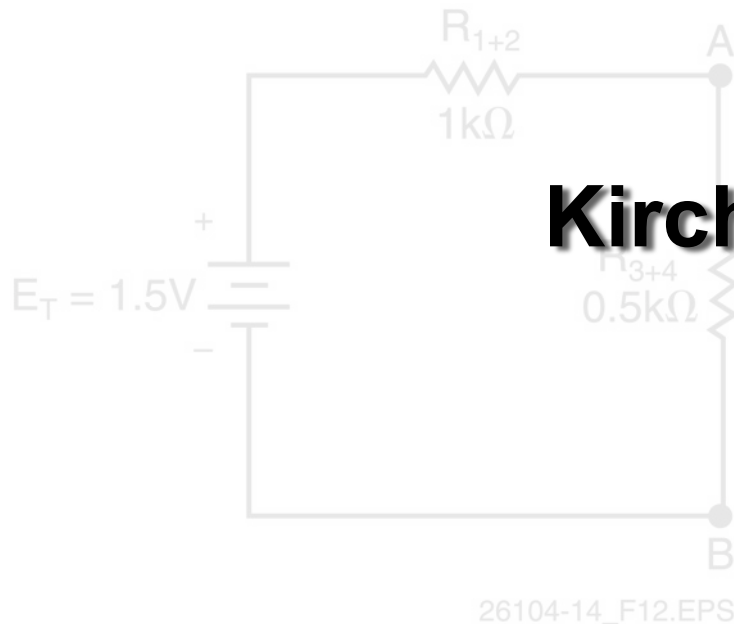
# Next Session... Simplified Series-Parallel Circuit



## Kirchhoff's Laws

- Calculate the total resistance as follows:

$$R_T = R_{1+2} + R_{3+4}$$

$$R_T = 1k\Omega + 0.5k\Omega = 1.5k\Omega$$

- Apply Kirchhoff's law to find the total current as follows:

$$I_T = E_T / R_T$$

$$I_T = 1.5V / 1.5k\Omega = 1mA \text{ or } 0.001A$$

- Individual voltage drops are calculated using Ohm's law:

$$E_{R1} = I_T R_1 = 1mA \times 0.5k\Omega = 0.5V$$

$$E_{R2} = I_T R_2 = 1mA \times 0.5k\Omega = 0.5V$$


## Kirchhoff's Laws

- Kirchhoff's current law states that at any point in a circuit, the total current entering that point must equal the total current leaving that point:

$$I_A + I_B - I_C = 0$$

$$5A + 3A - 8A = 0$$

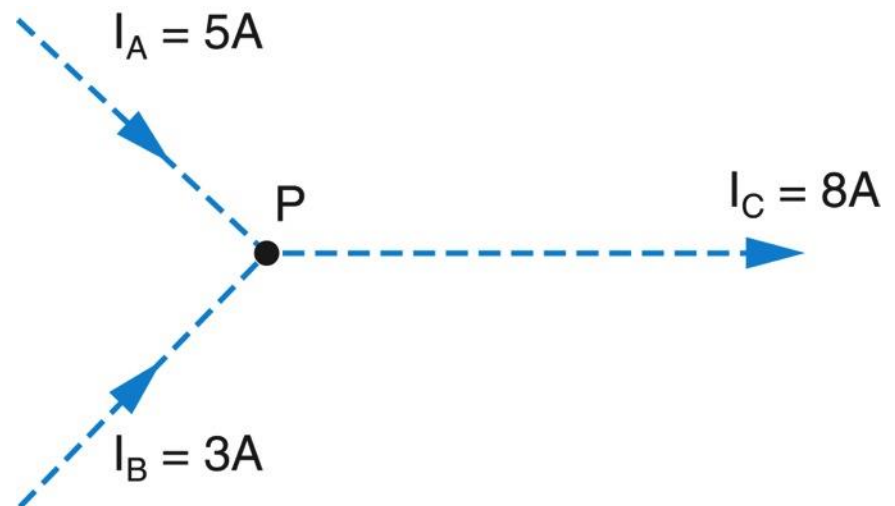- Kirchhoff's current law is the basis for the practical rule in parallel circuits that the total line current must equal the sum of the branch currents.



26104-14\_F13.EPS

## 3.0.0 – 3.1.0

# Application of Kirchhoff's Current Law

- Applying Kirchhoff's current law to this circuit at Point C can be shown as follows:


$$I_T - I_3 - I_{4/5} = 0$$

$$6A - 2A - 4A = 0$$

- Applying Kirchhoff's current law to this circuit at Point D can be shown as follows:

$$I_3 + I_{4/5} - I_T = 0$$

$$A + 4A - 6A = 0$$

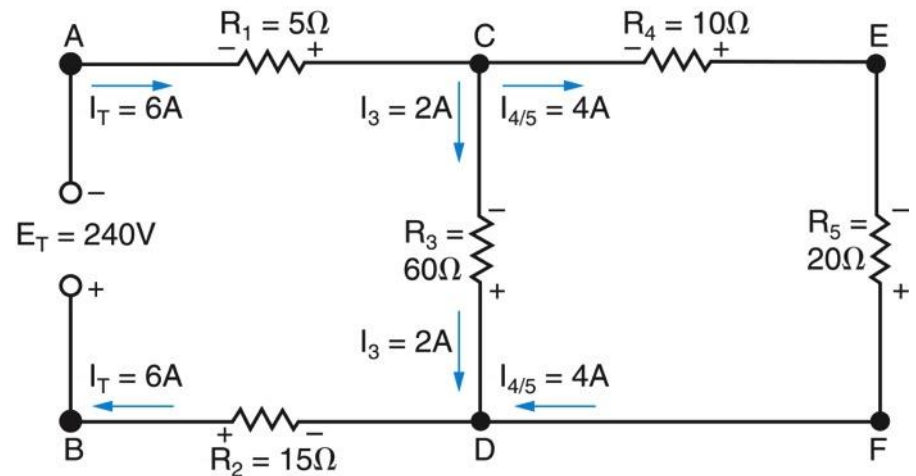

26104-14\_F14.EPS

## 3.2.0


# Kirchhoff's Voltage Law

- Kirchhoff's voltage law states that the algebraic sum of all the potential differences in a closed loop is equal to zero:

$$E_A - E_1 - E_2 - E_3 = 0$$

$$100A - 50A - 30A - 20A = 0$$

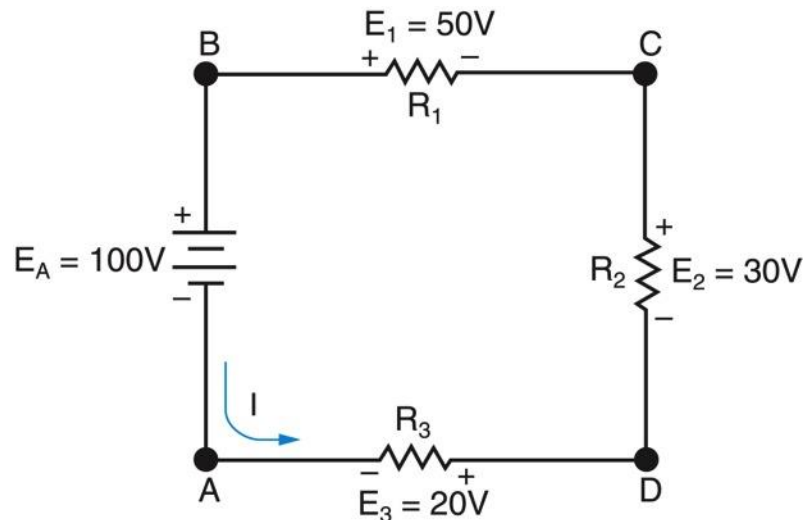- This means that the sum of the voltage drops in a circuit is equal to the applied voltage.




26104-14\_F15.EPS

## 3.3.0
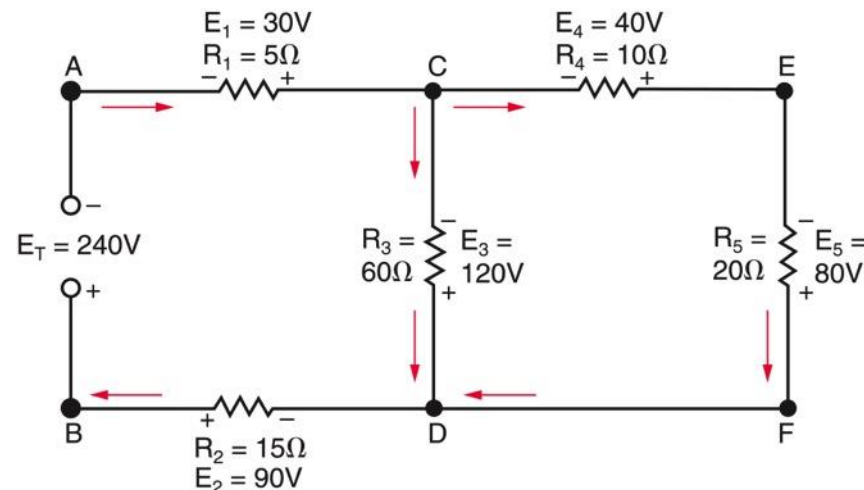
# Loop Equations

- Any closed path for current flow is called a loop. A loop equation specifies the voltages around the loop:
  - $-E_1 - E_3 - E_2 + E_T = 0$
  - $-30V - 120V - 90V + 240V = 0$
- Voltages  $E_1$ ,  $E_3$ , and  $E_2$  have a negative value because there is a decrease in voltage seen across each of these resistors in a clockwise direction.



### 3.3.0

## Applying Kirchhoff's Voltage Law

The voltage  $E_B$  is calculated as follows:


$$-E_3 - E_B - E_2 - E_1 + E_A = 0$$

Rearranged to solve for  $E_B$ :

$$E_B = E_A - E_3 - E_2 - E_1$$

$$E_B = 15V - 2V - 6V - 3V$$

$$E_B = 4V$$

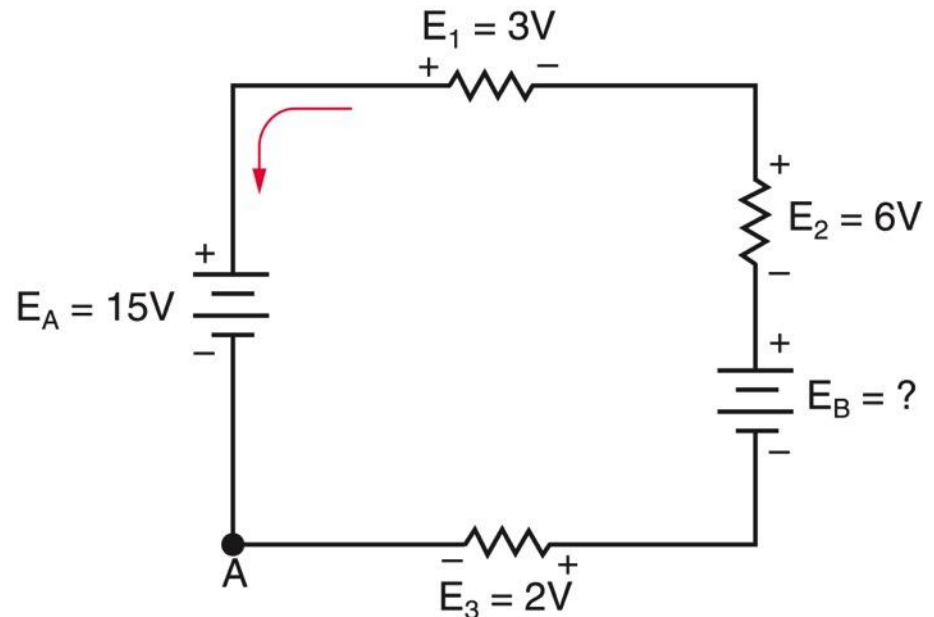

26104-14\_F17.EPS

# Wrap Up

## 3-2-1

- 3 – Write 3 important things learned during class
- 2 – Write 2 questions you have about the material
- 1 – Write 1 thought you had about the material



# Next Session...

## MODULE EXAM

Review the complete module to prepare for the module exam. Complete the Module Review as a study aid.

