

Residential Laboratory Project 2

(Switched Light & Receptacle)

1. Complete the wiring diagram and submit it to the instructor for approval before constructing this circuit in the lab.
2. Diagram is worth 10 points

Light



120v Power Source



Single Pole Switch



Receptacle

