

Residential Laboratory Project 3

(GFI/GFIP)

1. Complete the wiring diagram and submit it to the instructor for approval before constructing this circuit in the lab.
2. Diagram is worth 10 points

120v Power Source



GFI

(Load)



(Line)

GFIP

