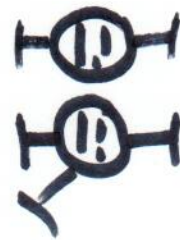


Residential Laboratory Project 4

(Switched Receptacle/Receptacle)

1. Complete the wiring diagram and submit it to the instructor for approval before constructing this circuit in the lab.
2. Diagram is worth 10 points

Receptacle # 1



120v Power Source



Single Pole Switch



Receptacle # 2

