

Residential Laboratory Project 6

(Chime Transformer)

1. Complete the wiring diagram and submit it to the instructor for approval before constructing this circuit in the lab.
2. Diagram is worth 10 points

Chime

FR

Trans


Rear



120v Power Source



16v Transformer

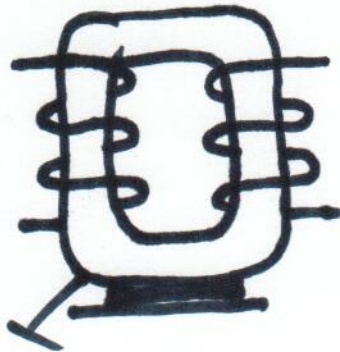

FR. Door Bell Button



R. Door Bell Button

