

ELT 101: Basic Electricity: AC/DC**Unit 13 Exam: Inductance and inductive circuits**

NAME _____

DATE _____

Circle the most correct answer (2 points each for a total of 20 points)

- 1) An inductor stores electrical energy in the form of a(n) _____ field, just as a capacitor stores electrical energy in the form of a(n) _____ field.
A. electric, magnetic
B. magnetic, electric

- 2) Inductors oppose changes in:
A. current
B. voltage
C. resistance
D. inductance

- 3) The total inductance of a series circuit is:
A. less than the value of the smallest inductor
B. equal to the sum of the individual inductors
C. equal to the product over the sum
D. all of the above

- 4) The total inductance of a parallel circuit is calculated by:
A. using the product over the sum formula
B. using L divided by N for equal-value inductors
C. using the reciprocal inductance formula
D. all of the above

- 5) The time constant for an RL circuit is:
- A. $L \times R$
 - B. L/R
 - C. V/R
 - D. 2 times pi times $F \times L$
- 6) Inductive reactance is proportional to:
- A. time or period of the AC applied
 - B. frequency of the AC applied
 - C. the value of the inductance
 - D. two of the above are true
 - E. none of the above
- 7) When tested with an ohmmeter, an open coil will read:
- A. zero resistance
 - B. infinite resistance
 - C. 100 to 200 ohms
 - D. around 1k
- 8) Increasing the length of coil will have what effect on the coil's inductance?
- A. increase it
 - B. decrease it
 - C. length has no effect
 - D. depends on the frequency
- 9) The unit of inductance is the:
- A. maxwell
 - B. ohm
 - C. tesla
 - D. henry


- 10) The unit for inductive reactance is the:
- A. ohm
 - B. henry
 - C. Maxwell
 - D. tesla
- 11) Inductors are classified as either:
- A. fixed or variable
 - B. open or closed
 - C. air or ferrite
 - D. single or polyphase
- 12) _____ leads _____ in a purely inductive circuit.
- A. inductance, inductive reactance
 - B. voltage, inductance
 - C. current, voltage
 - D. voltage, current
- 13) How many time constants will it take for an inductor to fully develop its magnetic field?
- A. two
 - B. three
 - C. four
 - D. five
- 14) Inductance and inductive reactance are basically the same.
- A. true
 - B. false

- 15) You can tell if an inductor has an iron core if its schematic symbol has a pair of solid lines drawn next to the coil.
- A. true
- B. false


Solve the following (5 points each for a total of 20 points) Show your work!

1) What is the total inductance of the circuit shown?

- L1 = 500mH
 L2 = 1H
 L3 = 500mH?

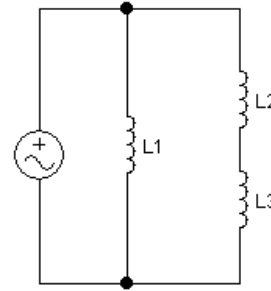

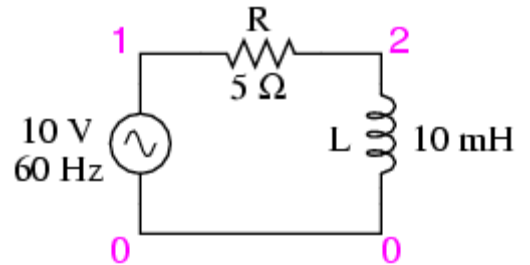2) What is the time constant for the circuit shown?




3) What is the inductive reactance of the circuit shown?



4) Identify the core type of the inductors shown at right.

- A _____
 B _____
 C _____

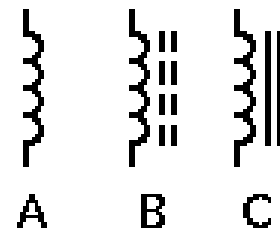

Points possible:

Multiple choice/T/F:	30
<u>Problems:</u>	<u>20</u>
Total	50

***** end of unit 13 exam *****