

**ELT 101: Basic Electricity: AC/DC****Unit 14 Exam: Capacitance and capacitive circuits**

NAME \_\_\_\_\_


DATE \_\_\_\_\_

**Circle the most correct answer (1 point each for a total of 20 points)**

- 1) When a capacitor charges, the:
  - A. Voltage across the plates rises exponentially
  - B. circuit current falls exponentially
  - C. capacitor charges to the source voltage in 5 time constants
  - D. all of the above
  
- 2) The capacitance of a capacitor is directly proportional to:
  - A. the plate area
  - B. the distance between the plates
  - C. the constant of the dielectric used
  - D. both A and C
  - E. both A and B
  
- 3) The capacitance of a capacitor is inversely proportional to:
  - A. the plate area
  - B. the distance between the plates
  - C. the dielectric used
  - D. both A and C
  
- 4) Total capacitance of series capacitors is calculated by:
  - A. adding up the individual capacitances
  - B. using the reciprocal capacitance formula
  - C. dividing four equal value capacitors by four
  - D. both A and C
  - E. both B and C

- 5) A capacitor in an RC circuit will fully charge in how many time constants?
- A. one
  - B. three
  - C. five
  - D. it depends on the circuit
- 6) Capacitors store energy in the form of:
- A. a magnetic field
  - B. an electrostatic field
  - C. an electromagnetic field
  - D. a positive field
- 7) In two time constants a capacitor will discharge to what % of applied voltage.?
- A. 63.2%
  - B. 86.5%
  - C. 36.8%
  - D. 13.5%
- 8) For a given value of C, if f is increased, then  $X_C$  will:
- A. increase
  - B. decrease
  - C. remain the same
  - D. it depends on the frequency
- 9) For a given value of f, if C is decreased,  $X_C$  will:
- A. increase
  - B. decrease
  - C. remain the same
  - D. none of the above

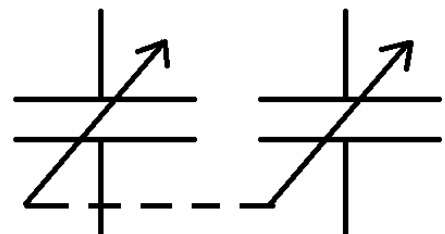- 10) Capacitive reactances in parallel add like resistances in:
- series
  - parallel
  - neither of these
- 11) If  $f$  and  $C$  are both doubled in a given circuit, the  $X_C$  will:
- increase two times
  - decrease two times
  - increase four times
  - decrease four times
- 12) What is the total  $X_C$  of two series connected  $1\mu\text{F}$  capacitors at a frequency of  $200\text{Hz}$ ?
- $3180$  ohms
  - $15.9$  ohms
  - $318$  ohms
  - $1.59\text{K}$  ohms
  - none of the above
- 13) In a purely capacitive circuit:
- the current flowing in the circuit leads the voltage across the capacitor by  $90$ -degrees
  - the circuit current and resistor voltage are in phase
  - the current leads the voltage by  $45$  degrees
  - the current leads the voltage by a phase angle between  $0$  and  $90$  degrees
- 14) For the schematic symbol shown below, what does the dotted line indicate?
- the capacitors are in series
  - the capacitors are in phase
  - the capacitors are in parallel
  - the capacitors are ganged



- 15) The schematic symbol shown at right is for a:
- A. nailed capacitor
  - B. trimmer capacitor
  - C. ganged capacitor
  - D. variable capacitor




**Match the term to its definition (1 point each for a total of 10 points)**

- A) farad \_\_\_\_\_ time needed to reach 63.2% of applied voltage
- B)  $X_C$  \_\_\_\_\_ ability to store a charge
- C) capacitor \_\_\_\_\_ polarity sensitive
- D) phase shift \_\_\_\_\_ non-conductive material
- E) picofarad \_\_\_\_\_ mechanically coupled capacitors with one control
- F) capacitance \_\_\_\_\_ occurs between voltage and current in a capacitive circuit
- G) time constant \_\_\_\_\_ capacitive reactance
- H) ganged capacitor \_\_\_\_\_ two plates separated by a dielectric
- I) dielectric \_\_\_\_\_ unit of capacitance
- J) electrolytic cap \_\_\_\_\_  $1 \times 10^{-12}$  farad


**Solve the following (points shown for each for a total of 10 points) Show your work!**

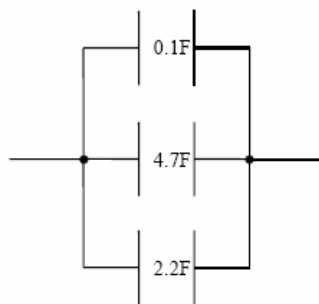- 1) Calculate the total capacitance of the circuit shown below (3 points).




$C_{total} = \dots\dots\dots$   
 $= \dots\dots\dots$

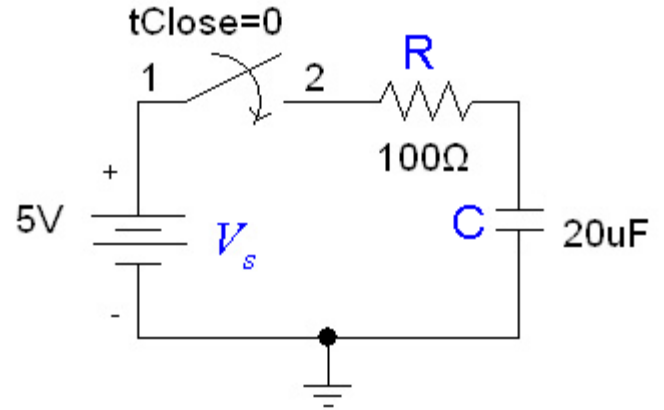- 2) Once the switch is closed, how long will it take the capacitor in the circuit shown to fully charge? (4 points)



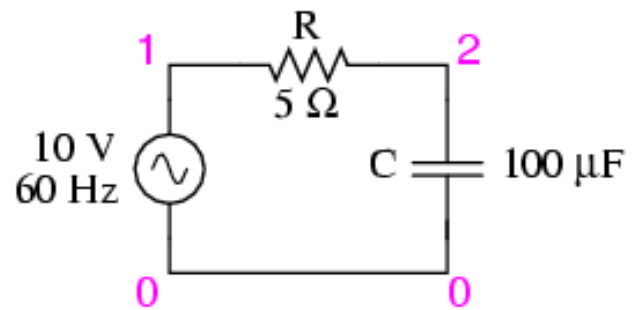- 3) What is the capacitive reactance of the circuit shown? (3 points)



**Points possible:**

Multiple choice:	30
Matching:	10
<u>Problems:</u>	10
Total	50

\*\*\*\*\* end of unit 14 exam \*\*\*\*\*