

**ELT 101: Basic Electricity: AC/DC****Unit 9 Exam: Series-parallel Circuits**


NAME \_\_\_\_\_

DATE \_\_\_\_\_

**Circle the most correct answer (2 points each for a total of 20 points)**

- 1) A series-parallel circuit is a combination of
- components connected end to end
  - series (one-path) circuits
  - both series and parallel circuits
  - parallel (two or more path) circuits

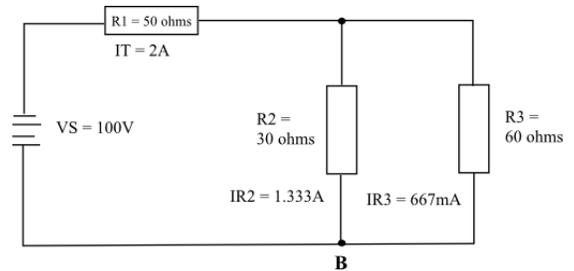- 2) Referring to the circuit at right, what is the current flowing out of node B?
- 887 mA
  - 1.33 A
  - 667 mA
  - 2 A



- 3) Referring to the circuit above, what is the total circuit power?
- 20mW
  - 20 watts
  - 200mW
  - 200 watts
- 4) When calculating  $R_T$  in a complex series-parallel circuit, it is best to start:
- as far away as possible from the voltage source
  - in the middle of the circuit
  - as close to the voltage source as possible
  - working with parallel combinations first

- 5) Any series-parallel circuit can be simplified into a \_\_\_\_\_ and a \_\_\_\_\_.
- A. voltage source, equivalent resistance
  - B. current source, voltage divider
  - C. resistance, power rating
  - D. power rating, battery
- 6) The toughest part of analyzing series-parallel circuits is:
- A. using the trigonometry involved
  - B. determining what's in series and what's in parallel
  - C. calculating power
  - D. none of the above
- 7) The simplest technique to identifying series and parallel components is to:
- A. flow voltage
  - B. flow current
  - C. use Ohm's Law
  - D. guess
- 8) In a series circuit the sum of the individual voltage drops must equal the applied voltage.
- A. true
  - B. false

List the five steps in the five-step method of analyzing a series-parallel circuit

(5 points total)

Step 1: \_\_\_\_\_

Step 2: \_\_\_\_\_

Step 3: \_\_\_\_\_


Step 4: \_\_\_\_\_

Step 5: \_\_\_\_\_

**Solve the following. Make sure to show your work!**

1) In the circuit below, solve for  $R_T$ ,  $I_T$ ,  $I_{R1}$ ,  $I_{R2}$ ,  $V_{R1}$ ,  $V_{R2}$  and  $V_{R3}$  (3 points each for a total of 21 points)

*Series-parallel*

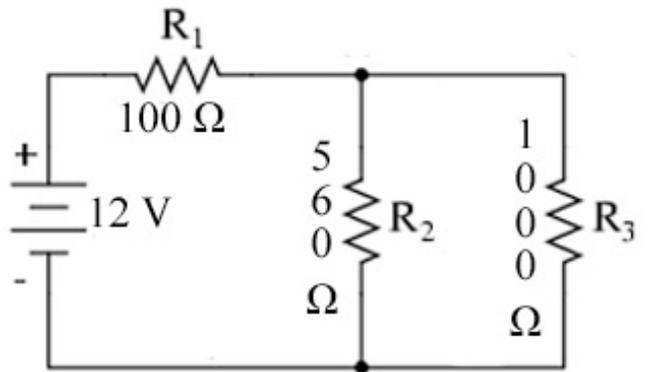

$R_T =$  \_\_\_\_\_

$I_T =$  \_\_\_\_\_

$I_{R1} =$  \_\_\_\_\_


$I_{R2} =$  \_\_\_\_\_

$V_{R1} =$  \_\_\_\_\_

$V_{R2} =$  \_\_\_\_\_

$V_{R3} =$  \_\_\_\_\_

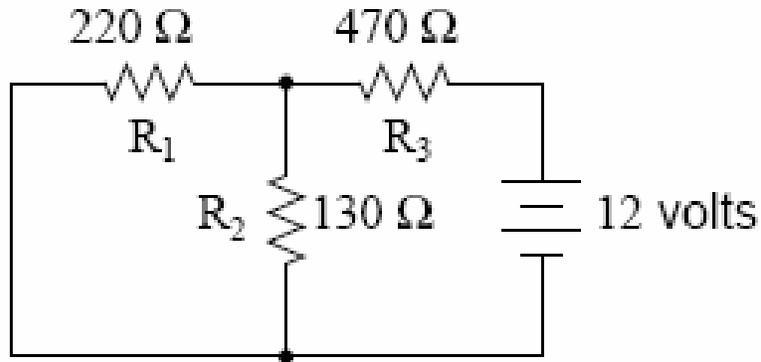2) In the circuit shown below, what are the voltage drops across R1, R2 and R3 assuming R2 is shorted? (6 points total).



With R2 shorted	Voltage
R1	
R2	
R3	

**Points possible:**

Multiple choice: 18  
 Fill in the blank 5  
Problems: 30  
 50

\*\*\*\*\* end of unit 9 exam \*\*\*\*\*