

ELT 101: Basic Electricity: AC/DC

LAB 5-2: The potentiometer

Objectives

- 1) Become familiar with a potentiometer
- 2) Measure the range of resistance on a potentiometer
- 3) Identify whether a potentiometer has a linear or audio taper
- 4) Utilize a potentiometer to create varying voltages



Equipment and materials

- 1) Safety glasses
- 2) Fluke 179 DMM
- 3) Electrical trainer
- 4) Jumper leads



Procedure 1: Becoming familiar with potentiometers

- 1) Note the schematic symbol for a potentiometer shown below.
- 2) A potentiometer is a three-terminal variable resistor. The total resistance of the potentiometer is available on its outer terminals. The middle terminal is the wiper arm and this is where a varying resistance is available typically ranging from 0 ohms up to its maximum rated value.

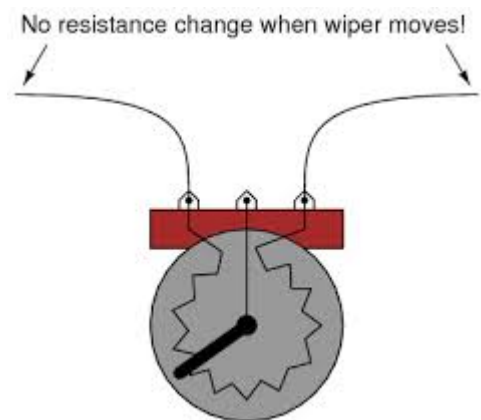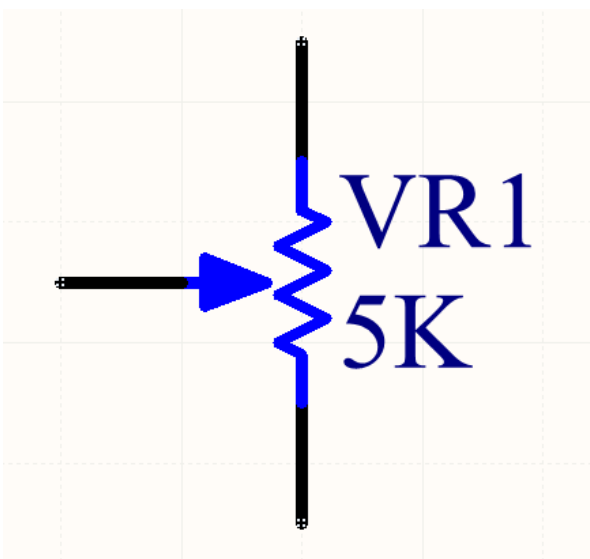


Procedure 2: Measuring the range of a potentiometer

- 1) Complete the pre-use tests on the Fluke 179.
- 2) Set the Fluke 179 to read resistance.
- 3) Connect the meter leads to the outer terminals of the potentiometer on the trainer board and record the resistance below

R = _____

- 4) Vary the wiper arm. What happened? Why?

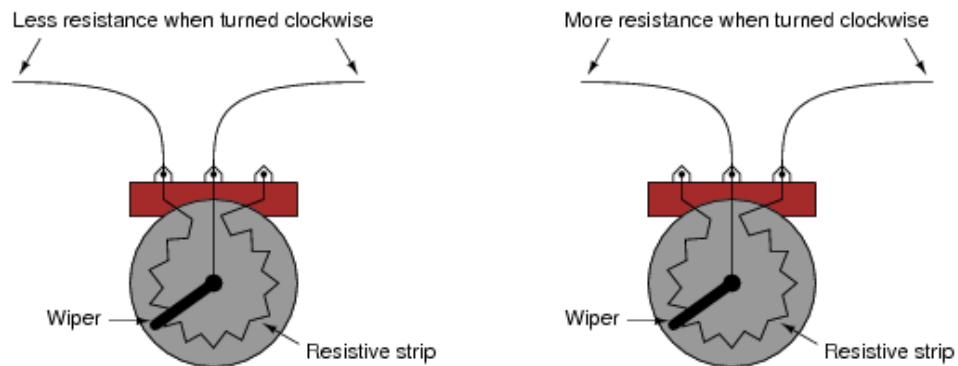
- 5) Move one of the probes to the middle terminal as shown below.



- 6) Vary the wiper arm. What happens?


Procedure 3: Determine the type of taper of the potentiometer

- 1) Record the resistance range of the potentiometer. _____
- 2) Find the mid point of travel of the wiper arm; record the resistance. _____
- 3) Is this potentiometer an audio or a linear taper? Hint: see the illustration on the next page. Why?

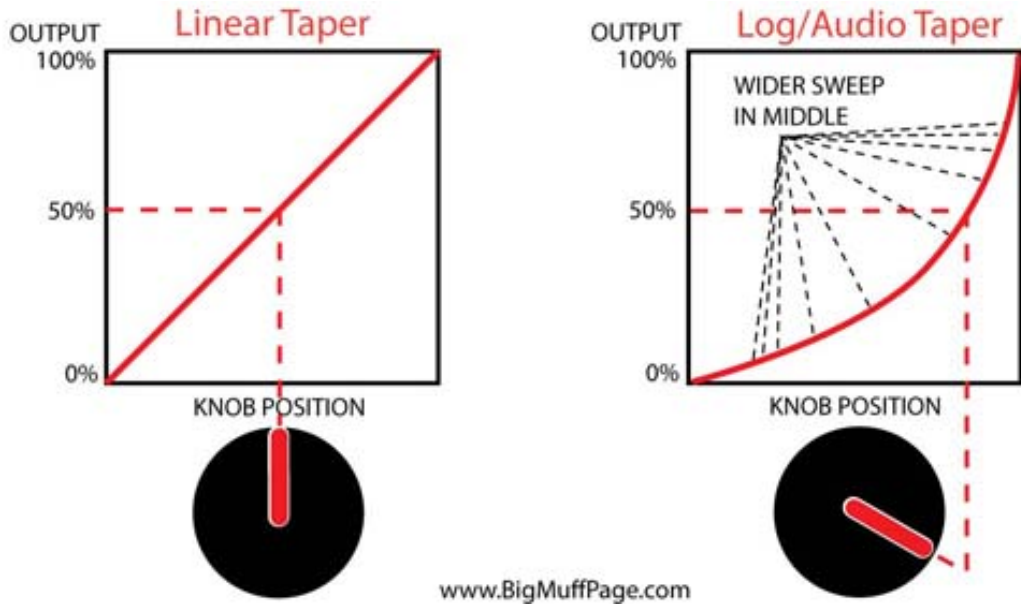

Procedure 4: Utilize a potentiometer to create varying voltages

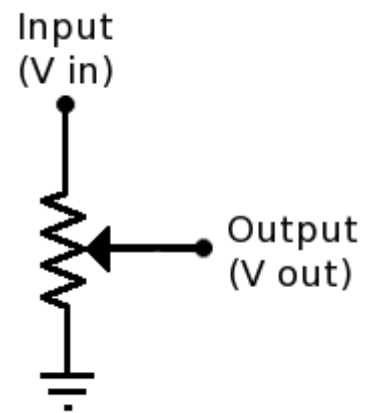- 1) Plug in your trainer and make sure both power switches are off.
- 2) Connect the circuit shown on your trainer board.
- 3) The outside terminals of the potentiometer are connected to the red and black 5V binding posts.
- 4) The middle terminal is connected to your meter.
- 5) Set your DMM to read DC volts.
- 6) Turn on the main power and then the 5V/12V power.
- 7) While observing the meter, vary the potentiometer.
- 8) What happens?



- 9) So as you can see, a potentiometer allows us to produce varying voltages and resistances.
- 10) Can you think of a common application for one of these?

**** end of lab 5-2 ****