

US DOL SPONSORED TAACCCT GRANT: TC23767 F PRIMARY DEVELOPER: Jim Blair – Henry Ford College

# Solid State Electronics – Unit 3: Zener Diodes

Lab – Working with Zener Diode

Name: \_\_\_\_\_\_

All portions of LAB 2 ZENER DIODE LAB covered in this document must be completed and verified before moving on.

### OBJECTIVES

- 1. Assemble circuits using zener diodes.
- 2. Understand zener diode ratings
- 3. Learn how zener diodes function in DC circuits.
- 4. Use digital meters to measure voltages at various points in zener diode circuits.
- 5. Troubleshooting of zener diode circuits.

### MATERIALS

- DC Power Supply
- Multimeter
- 12v zener diode
- resistors
- Breadboard





Multi-State	RELEASE	
Advanced Manufacturing	DATE	
Consortium	VERSION	
US DOL SPONSORED TAACCCT GRANT: TC23767	PAGE	
PRIMARY DEVELOPER: Jim Blair – Henry Ford College		

Lab – Working with Zener Diode

### PROCEDURE


**PART A: Zener diode specifications** 

See the specification sheet.


http://www.jameco.com/Jameco/Products/ProdDS/1538081.pdf
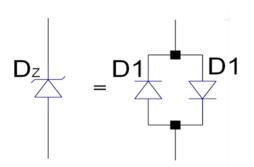
#### PART B: Zener diode characteristics

Step 1. A zener diode can act like two diodes connected in reverse parallel as shown.



If a zener diode is connected in forward bias mode like a conventional diode, as in the previous lab, there will be about .7 volts across it. If the zener is connected in reverse bias mode there will be a voltage across the diode equal to the zener voltage. We will use a 12 volt zener for our lab. Therefor, our diode would have 12v across it if reverse biased. In the examples, current will not flow in one direction unless the is at least about .7 volts across the zener diode. In the reverse biase mode, current flows only after there is 12 volts across the zener diode.

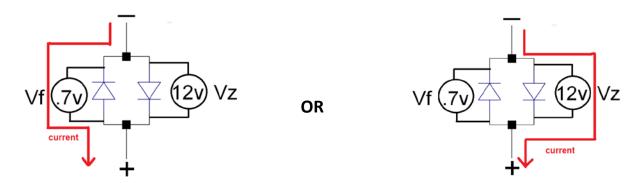



3/18/2016 v 001 2 of 8




Multi-State Advanced Manufacturing	RELEASE DATE	3/18/2016
Consortium	VERSION	v 001
US DOL SPONSORED TAACCCT GRANT: TC23767	PAGE	3 of 8
PRIMARY DEVELOPER: Jim Blair – Henry Ford College		

Solid State Electronics – Unit 3: Zener Diodes Lab – Working with Zener Diode

Step 3. This concept that the diode will have a predictable voltage across it will enable us to use the diode to keep voltage constant across another component or point in the circuit.

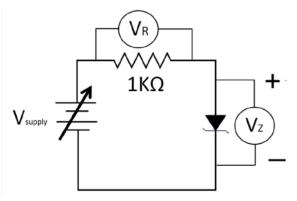Step 4: Set up the following circuit. This will demonstrate the forward bias characteristics of a zener diode.



Step 5: Adjust V<sub>supply</sub> in order to make the voltage across the zener diode (VZ) equal to the voltage values in the following table.

Step 6: Once the voltage across the zener (VZ) is reached, measure the voltage across the  $1K\Omega$  resistor (VR). Place the value for VR in the table. For each value of VR calculate, using Ohm's Law, the current through the resistor. This will also be the current through the zener diode.

Vz	VR	$I_R = I_Z = VR/R$
.1v		
.2v		
.3v		
.4v.		
.5v.		
.6v.		
.7v.		
.8v		






Adva	Multi-State nced Manufacturing Consortium	RELEASE DATE VERSION	3/18/2016 v 001
	ORED TAACCCT GRANT: TC23767 RY DEVELOPER: Jim Blair – Henry Fo	PAGE ord College	4 of 8

Lab – Working with Zener Diode

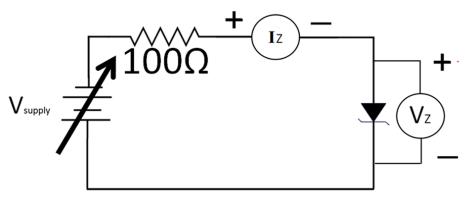Step 7: In order to determine the reverse bias characteristics of the zener diode we will configure the circuit as follows: The  $1K\Omega$  resistor is changed to a  $100\Omega$ . The power supply polarity is reversed.



Step 8: Adjust V<sub>supply</sub> in order to make the current through the zener diode (IZ) equal to the current values in the following table. For each of the values of current (IZ) record the voltage across the zener diode (VZ).

Iz	Vz
50 µA	
100 μA	
1mA	
5mA	
10mA	
15mA	
20mA	
25mA	
30mA	





Lab – Working with Zener Diode


#### PART C: Zener diode voltage regulator

Two important specs for voltage regulators are Line regulation and load regulation.

- Line regulation: voltage level despite changes to the input voltage level.
- **Load regulation is** the ability of a regulator to maintain a constant voltage, or current level at the output. The regulator should be able to do this despite changes in the regulator's load.

Step 9. The zener diode can be used as a voltage regulator as long as the current rating for the diode is not exceeded.

Step 10. Connect the following circuit.

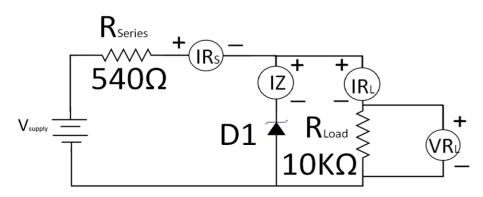

To show line regulation complete the following.

Step 11. Set the supply voltage to 0 volts.

Step 12. Measure the voltage across the load and place the value in the table.

Step 13. Increase the value of the supply voltage in increments of 1 volt as shown in the table. Measure the voltage across the load and record the value for each increment.





Multi-State Advanced Manufacturing Consortium RELEASE<br/>DATE3/18/2016VERSIONv 001PAGE6 of 8

US DOL SPONSORED TAACCCT GRANT: TC23767 P PRIMARY DEVELOPER: Jim Blair – Henry Ford College

# **Solid State Electronics – Unit 3: Zener Diodes**

Lab – Working with Zener Diode

Vsupply	VLoad
0v	
1v	
2v	
3v	
4v	
5v	
бv	
7v	
8v	
9v	
10v	
11v	
12v	
13v	
14v	
15v	
16v	
17v	
18v	
19v	
20v	





Lab – Working with Zener Diode

Step 14. Graph the results using Excel.

#### To demonstrate the load regulation complete the following.

Step 15. This will determine how the voltage is regulated with a changing load (resistance).

Step 16. Use the same circuit as used for line regulation.

Step 17. Complete the chart for the given loads. Begin with the supply voltage set for 15 volts. Also begin with the load value of  $10K\Omega$ . Each measurement will be made with the supply at 15 volts as loads are decreased. A decrease in load resistance means an increase in load current.

RL	VL	$I_L = V_L/R_L$	Is = (VSUPPLY - VL) / RS	Iz = Is - IL	Pz = (VL)(Iz)
10KΩ					
8.2KΩ					
6.8KΩ					
4.7KΩ					
2.2KΩ					

Step 18. Looking at your graph, was a certain amount of voltage overhead needed for the circuit to regulate?

Yes No

Step 19. Did a changing load have an impact on the regulation of the circuit?

Yes No





Mul	ti-State	
Advanced	Manufacturing	
Consortium		

RELEASE<br/>DATE3/18/2016VERSIONv 001PAGE8 of 8

US DOL SPONSORED TAACCCT GRANT: TC23767 F PRIMARY DEVELOPER: Jim Blair – Henry Ford College

# Solid State Electronics – Unit 3: Zener Diodes

Lab – Working with Zener Diode

### SAFETY DISCLAIMER:

M-SAMC educational resources are in no way meant to be a substitute for occupational safety and health standards. No guarantee is made to resource thoroughness, statutory or regulatory compliance, and related media may depict situations that are not in compliance with OSHA and other safety requirements. It is the responsibility of educators/employers and their students/employees, or anybody using our resources, to comply fully with all pertinent OSHA, and any other, rules and regulations in any jurisdiction in which they learn/work. M-SAMC will not be liable for any damages or other claims and demands arising out of the use of these educational resources. By using these resources, the user releases the Multi-State Advanced Manufacturing Consortium and participating educational institutions and their respective Boards, individual trustees, employees, contractors, and sub-contractors from any liability for injuries resulting from the use of the educational resources.

#### **DOL DISCLAIMER:**

This product was funded by a grant awarded by the U.S. Department of Labor's Employment and Training Administration. The product was created by the grantee and does not necessarily reflect the official position of the U.S. Department of Labor. The Department of Labor makes no guarantees, warranties, or assurances of any kind, express or implied, with respect to such information, including any information on linked sites and including, but not limited to, accuracy of the information or its completeness, timeliness, usefulness, adequacy, continued availability, or ownership.

#### **RELEVANCY REMINDER:**

M-SAMC resources reflect a shared understanding of grant partners at the time of development. In keeping with our industry and college partner requirements, our products are continuously improved. Updated versions of our work can be found here: <u>http://www.msamc.org/resources.html</u>.

