



Solid State Electronics – Unit 9: Transistors

Lab 1 - Transistor

Name _____

OBJECTIVES

- Evaluate the common emitter amplifier.
- Assemble components for NPN and PNP Transistor circuits.
- Understand Transistor ratings Learn how a transistor operates as a switch.
- Learn how a transistor operates as an amplifier.
- View inputs and outputs of a transistor amplifier.
- Use digital meters to measure voltages at various points of transistor circuits.
- Troubleshooting of transistor circuits.
- Use circuit simulation software to understand semiconductor circuits.

MATERIALS

- PNP Transistor
- NPN Transistor
- Resistors
- Power Supply
- Oscilloscope
- Multimeter
- Breadboard
- Circuit Simulation Software

PROCEDURE

Complete the steps for the transistor switch and for the transistor amplifier.

PART A TRANSISTOR TESTING

1. Examine the specification sheet of the 2N4403 and 2N2222 transistor.

What is the maximum voltage that can be put across the transistor?

2N4403 _____ 2N2222 _____





Solid State Electronics – Unit 9: Transistors

Lab 1 - Transistor

What is the maximum current that can flow through the transistor?


2N4403 _____ 2N2222 _____

What is the maximum power that can be dissipated by the transistor?


2N4403 _____ 2N2222 _____

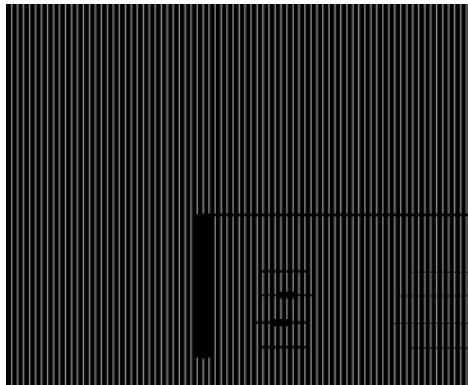2. Correctly place your transistor in a breadboard. Also, hook three short (1"-1.5") wires to each leg in the breadboard. Use a multimeter to verify if your transistor is a functioning transistor and also determine if it is an NPN or PNP transistor.

Use the following picture to determine this.



Checking A Transistor With An Ohm Meter.

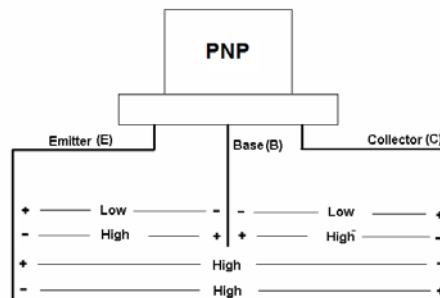

A faulty PN junction will not show a difference in resistance in the forward or reverse connection. A low resistance in both directions shows a junction is shorted. A high resistance in both directions indicates a junction is open.

PART B THE TRANSISTOR AS A SWITCH.

Introduction

A transistor has three regions in which it can operate. The regions are: The Saturation, Cutoff, and Active regions. When a transistor is operating in the saturation and cutoff region only, it is said to be






Solid State Electronics – Unit 9: Transistors

Lab 1 - Transistor

operating as a switch. When the transistor is operating in the saturation region it is operating like a switch that is turned on. When the transistor is operating in the cutoff region, it is operating like a switch that is off.

When the transistor is in the saturation region there is very little voltage across the emitter - collector (VCE). When the transistor is in cutoff there is very little current flow through the transistor (IC). During operation in the cutoff region, VCE is approximately equal to the supply voltage.

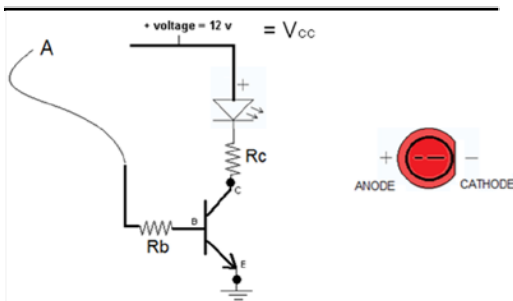3. Connect the NPN type transistor on the breadboard as shown in the following schematic diagram. Fill in the values of voltage and current as you complete the lab. Also, fill in the chart at the end with your data from the NPN transistor only. The PNP operates sin a similar way.



Connect the wire labeled "A" to ground. Leave the wire connected here until instructed to change positions.

4. Measure the voltage across the resistor labeled RC. _____

5. Measure the voltage across VCE. _____

Measure the collector current. _____

6. Is the transistor operating in the saturation or cutoff region? _____

7. Connect the wire labeled "A" to the +12 volt supply voltage.

8. Does the LED light? Yes No





Solid State Electronics – Unit 9: Transistors

Lab 1 - Transistor

9. Measure the voltage across the resistor labeled RC. _____
10. Measure the voltage across VCE. _____
- Measure the collector current. _____
11. Is the transistor operating in the saturation or cutoff region? _____
12. Measure the voltage across the base-emitter junction in both cases.
VBE in saturation = _____
VBE in cutoff = _____
13. Measure the voltage across the base resistor in both cases.
VRB in saturation = _____
VRB in cutoff = _____
14. If a transistor is in cutoff, about what percentage of the supply voltage is across the transistor?

15. If a transistor is in saturation, about what percentage of the supply voltage is across the transistor?


16. Could other loads be substituted for the LED in the collector lead? Yes No
17. What would be the maximum current that could be switched by the transistor? _____
18. What could the maximum voltage of the load be? _____
19. Connect the PNP type transistor on the breadboard as shown in the following schematic diagram.
Notice the transistor is a PNP type and the polarity of the power supply has been switched.





Solid State Electronics – Unit 9: Transistors

Lab 1 - Transistor

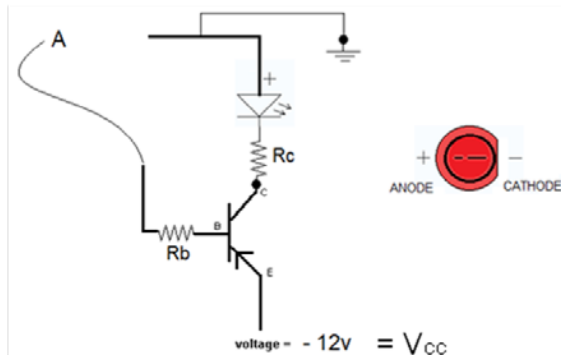

20. Measure the voltage across the resistor labeled RC. _____
21. Measure the voltage across VCE. _____
Measure the collector current. _____
22. Is the transistor operating in the saturation or cutoff region? _____
23. Connect the wire labeled "A" to the +12 volt supply voltage.
24. Does the LED light? Yes No
25. Measure the voltage across the resistor labeled RC. _____
26. Measure the voltage across VCE. _____
Measure the collector current. _____
27. Is the transistor operating in the saturation or cutoff region? _____
28. Measure the voltage across the base-emitter junction in both cases.
VBE in saturation = _____
VBE in cutoff = _____





Solid State Electronics – Unit 9: Transistors

Lab 1 - Transistor

29. Measure the voltage across the base resistor in both cases.
 VRB in saturation = _____
 VRB in cutoff = _____
30. If a transistor is in cutoff, about what percentage of the supply voltage is across the transistor?

31. If a transistor is in saturation, about what percentage of the supply voltage is across the transistor?

32. Could other loads be substituted for the LED in the collector lead? Yes No
33. What would be the maximum current that could be switched by the transistor? _____
34. What could the maximum voltage of the load be? _____
35. Fill in the following chart with your data from above. To calculate, use the formulas given by:
 $I_C = V_{RC} / R_C$ $I_B = V_{RB} / R_B$

	Measured Values				Calculated Values		Operating Region
	VCE	VRC	VRB	IC	IC	IB	
circuit 1							
circuit 2							

When the base-emitter junction is reverse biased, the transistor is operating in the cutoff region. This happened when wire "A" was connected to ground. The collector current was also greatly reduced. The source voltage appears across VCE. Since there is no collector current, there will be no voltage across the collector resistor. $I_C \times R_C = V_{RC}$





Solid State Electronics – Unit 9: Transistors

Lab 1 - Transistor

When VCE is very small the transistor is in the saturation region. The collector current will be high and there will be a large voltage across RC. The value of IB will also be large.


PART C THE TRANSISTOR AS AN AMPLIFIER.

The following was stated in the introduction of the transistor when used as a switch.

A transistor has three regions in which it can operate. The regions are: The Saturation, Cutoff, and Active regions. When a transistor is operating in the saturation and cutoff region only, it is said to be operating as a switch. When the transistor is operating in the saturation region it is operating like a switch that is turned on. When the transistor is operating in the cutoff region, it is operating like a switch that is off.

When the transistor is in the saturation region there is very little voltage across the emitter - collector (VCE). When the transistor is in cutoff there is very little current flow through the transistor (IC). During operation in the cutoff region, VCE is approximately equal to the supply voltage.

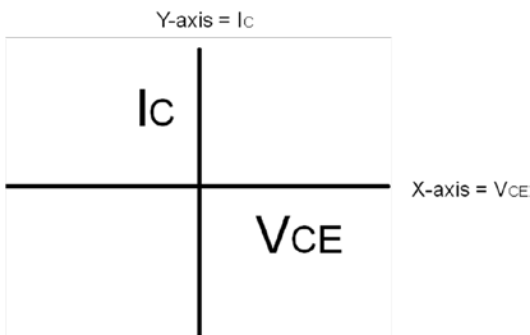A graph can be made of a transistor as a switch. The x-axis will be VCE the voltage from emitter-collector. The y-axis will be the collector current.



The lab showed when the transistor was in cutoff, no collector current flowed and the voltage measured across the emitter to collector (VCE) was equal to the supply voltage (VCC).

We know what the value of "x" is for the transistor when it is in cutoff. In our lab VCC was equal to 12 volts.



Solid State Electronics – Unit 9: Transistors

Lab 1 - Transistor

This gives:

$$"x" = VCE = VCC = 12v.$$


We also know what the value of "y" is for the transistor when it is in cutoff. When the transistor was in cutoff, there was no collector current (I_C). This is given as:

$$"y" = I_C = 0 \text{ ma.}$$

Every point on a graph can be shown if we have an "x" and a "y" term. We now have one point established on our graph showing how the transistor behaves. This point is given in (x,y) coordinate form is:

$$(12, 0)$$

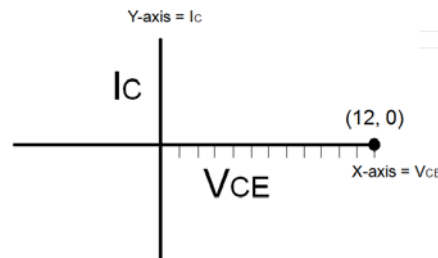If that point is placed on the graph established it will look like this:



A second point can be established in a similar method. This second point would represent when the transistor is in saturation. In the lab, conditions of saturation, showed zero volts across the emitter-collector (VCE). The "x" value in this condition therefore is:

$$"x" = VCE = 0 \text{ volts}$$


The lab also showed greater current flow through the collector than in the cutoff condition. The amount of current flow through the transistor during the saturation condition is determined by the collector resistor. The exact amount of current can be calculated using Ohm's Law. Look at the picture below:





Solid State Electronics – Unit 9: Transistors

Lab 1 - Transistor

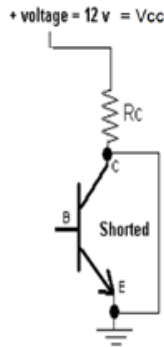

If the transistor was shorted, the current through the collector would be limited by the collector resistor (RC). Using Ohm's Law the current can be calculated.

$$I_C = V_{RC} / R_C$$


V_{RC} will be equal to V_{CC} and for simplicity let $R_C = 1000\Omega$.

$$\begin{aligned} I_C &= V_{RC} / R_C \\ &= 12\text{v} / 1000\Omega \\ &= 12\text{ mA} \end{aligned}$$

This establishes the coordinate pair of the saturated condition or second point.

$$\text{"y"} = 12\text{ mA from above "x"} = 0\text{ v } (0, 12)$$

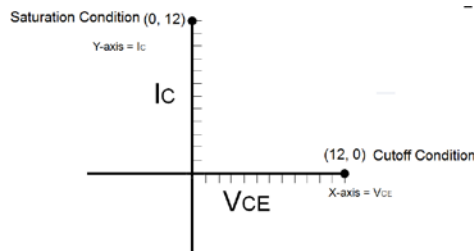The following is the graph with the saturation and cutoff condition established as points on the graph.



The transistor may also operate in the active region. When it is operating in this region it is operating as an amplifier. In this region the transistor can have varying values of collector current (I_C) and voltage across the collector-emitter (V_{CE}). These values will depend on how much the transistor is conducting. The amount of






Solid State Electronics – Unit 9: Transistors

Lab 1 - Transistor

conduction is determined by the base current. The base current is determined by the base resistor.

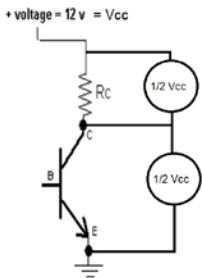When the values of VCE and VRC are about equal, the transistor is operating in approximately the center of the active area.



The graph developed above shows the two extreme values, cutoff and saturation. The characteristics of a transistor could be placed on the same graph.

Characteristics of resistance and characteristics of diodes were explained in the STUDY GUIDE. Please refer back to that if necessary.

The method used to change the transistor from cutoff to saturation was to move the wire "A" from ground to the supply. This was essentially changing our base current (I_B). In the case of cutoff the base current (I_B) became zero when "A" was put to ground. When "A" was put to the supply, the base current (I_B) became some value greater than zero. It became large enough to turn the transistor on and allow as much current to flow through the collector as possible. The only thing limiting the flow was the collector resistor.

In a like manner the only thing limiting the flow of current through the base of the resistor is the base resistor (R_B). If a value of the resistor used for R_B was larger than the resistor used in lab was connected, less base current would have flowed. If less base current would have flowed, the transistor would not have been turned on to fully saturate the transistor with current flow. The transistor would have been operating in the active region instead. Also, if a value of the resistor used for R_B was increased in increments less base current would have flowed in each corresponding increment. If less base current would have flowed, the transistor would not have been turned on to fully saturate the transistor with current flow. The transistor would have been operating in the active region instead. The incremented smaller base currents produced could be reduced until almost zero base current was flowing through the base of the transistor. The final increment of base






Solid State Electronics – Unit 9: Transistors


Lab 1 - Transistor

current would be zero base current. With zero base current the transistor would be in cutoff.

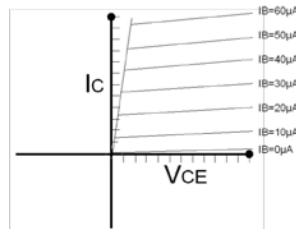These varying base currents could be drawn on the graph we used above.




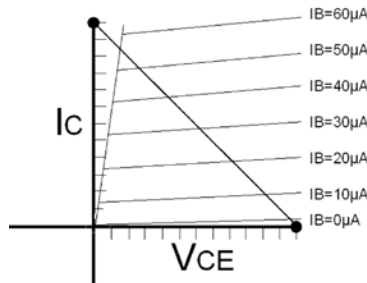A line drawn on the graph between the cutoff and saturation point is shown.



The transistor must operate on this line. The line is called a load line. In this case, since the value of RC is 1000Ω, this line is called the 1000Ω load line. The transistor can be in cutoff region, through the active region, or in the saturation region.

Examples:

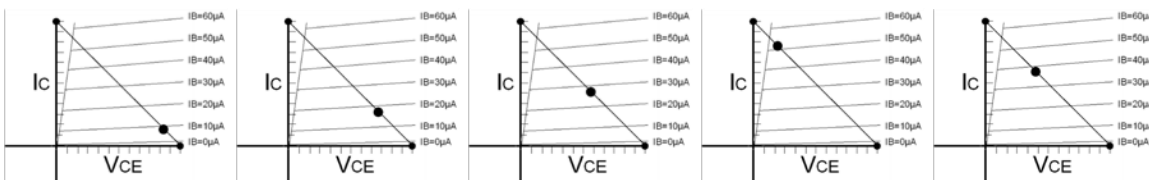

To review:

- The transistor must operate on the load line





Solid State Electronics – Unit 9: Transistors


Lab 1 - Transistor

- The load line is determined by the value of R_C .
- The operation of the transistor on the load line depends on the value of I_B .
- The value of I_B is determined by R_B .
- A larger R_B means a smaller I_B . A smaller R_B means a larger I_B .

The following was stated earlier:

The transistor may also operate in the active region. When it is operating in this region it is operating as an amplifier. In this region the transistor can have varying values of collector current (I_C) and voltage across the collector-emitter (V_{CE}). These values will depend on how much the transistor is conducting. The amount of conduction is determined by the base current. The base current is determined by the base resistor.

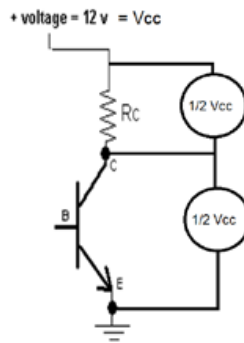When the values of V_{CE} and V_{RC} are about equal, the transistor is operating in approximately the center of the active area.




When the transistor is operating in this area it operates at the center of the load line. This can be shown on the graph.




Solid State Electronics – Unit 9: Transistors

Lab 1 - Transistor

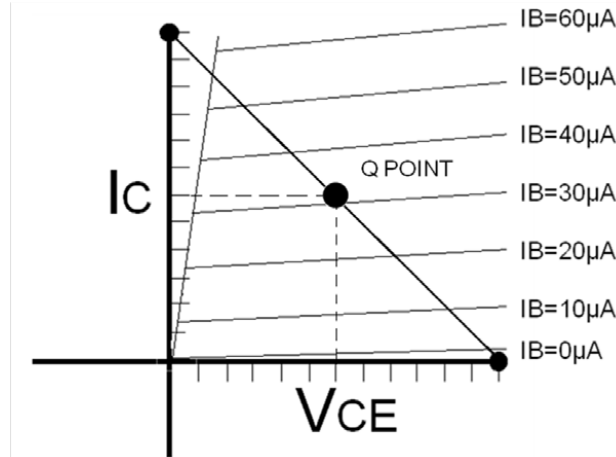

When the transistor operates at the center of the load line it is considered to be operating under optimal conditions. It is said to be operating at the Q Point. The Q Point is short for Quiescent Point. Looking at the graph, at the Q Point, the voltage across the emitter-collector (V_{CE}) for this example is 6 volts. This means there is also 6 volts across the collector resistor (R_C). At the Q Point the collector current is 6 mA. This makes sense because according to Ohm's Law... $V_{RC} / R_C = I_C$. Then this gives: $6v / 1000\Omega = 6mA$. Also, at the Q Point it can be seen that the base current I_B is equal to $30\mu A$.

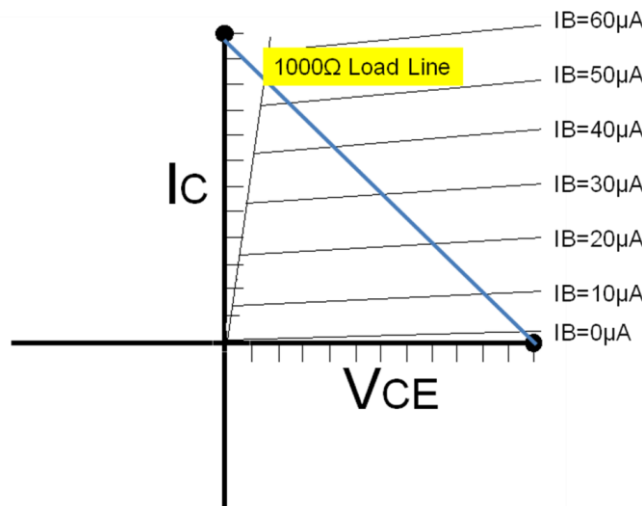36. Use the given set of transistor characteristic curves and draw load lines for a transistor circuit with R_C values of 1500Ω , 2500Ω and 6000Ω . Put all 3 load lines on the same set of curves.






Solid State Electronics – Unit 9: Transistors

Lab 1 - Transistor

37. What value will I_B , I_C , and V_{CE} be at the Q Point of each load line?

	1500 Ω	2500 Ω	6000 Ω
I_B			
I_C			
V_{CE}			

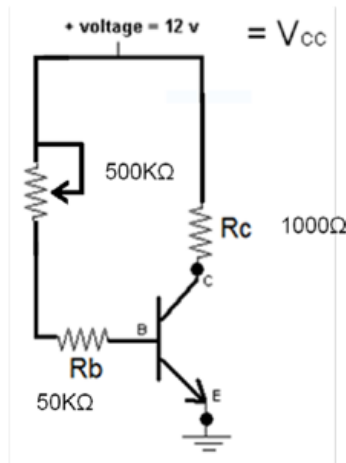38. Set up the following circuit on the breadboard.



39. Connect a voltmeter across V_{CE} .

40. Turn the potentiometer until you measure 6 volts across V_{CE} .

41. Record your measurement for V_{CE} in the table.

42. Measure I_B , I_C , V_{RC} , and V_{RB} and record your measurements.






Solid State Electronics – Unit 9: Transistors

Lab 1 - Transistor

	Measured
VCE	
IB	
IC	
VRC	
VRB	

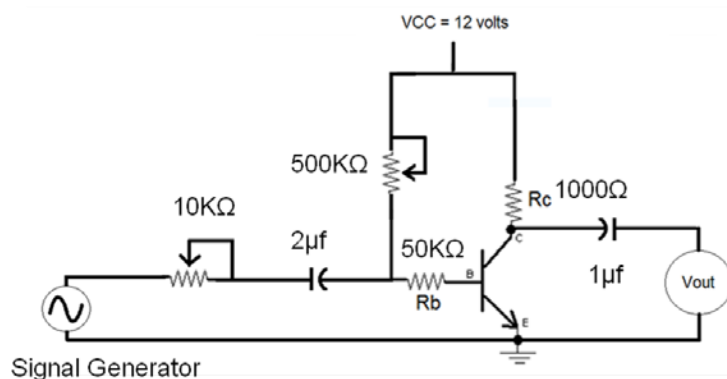- Are the values close to your values you saw in the graph? Yes No
- Connect a signal generator to your circuit as shown below. Be sure to observe polarities of the capacitors.



- Connect channel 2 of an oscilloscope where the diagram shows Vout.
- Adjust the signal generator until you have a 2 volt peak-to-peak signal at the output. Do this at a frequency of 1000 Hz.
- Once your output is established, measure the input signal with channel 1 of the oscilloscope.






Solid State Electronics – Unit 9: Transistors

Lab 1 - Transistor

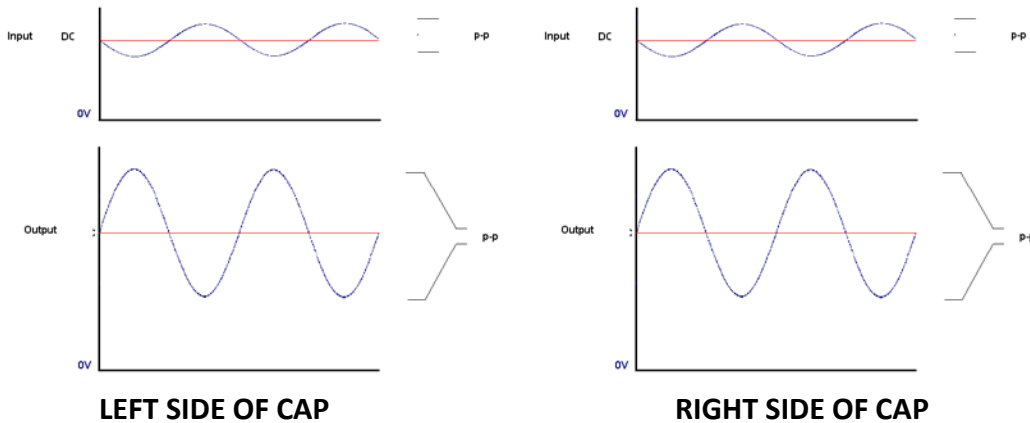48. Show both the input and the output of the amplifier at the same time on the oscilloscope.
49. Notice the output is out of phase with the input by 180o.
50. Fill in your information in the provided waveforms.



51. An amplifier takes a small input signal and multiplies it to make a larger output signal. This is called gain. There is current gain, voltage gain, and power gain.
52. Find the voltage gain of your amplifier circuit. To do this divide the output voltage by the input voltage. Voltage gain is given the variable name AV.

$$AV = V_{out} / V_{in}$$

Your AV = _____


Slowly increase the amplitude of the signal generator while monitoring the output voltage. Increase the input signal until the output just begins to distort. Fill in your information in the provided waveforms.






Solid State Electronics – Unit 9: Transistors

Lab 1 - Transistor

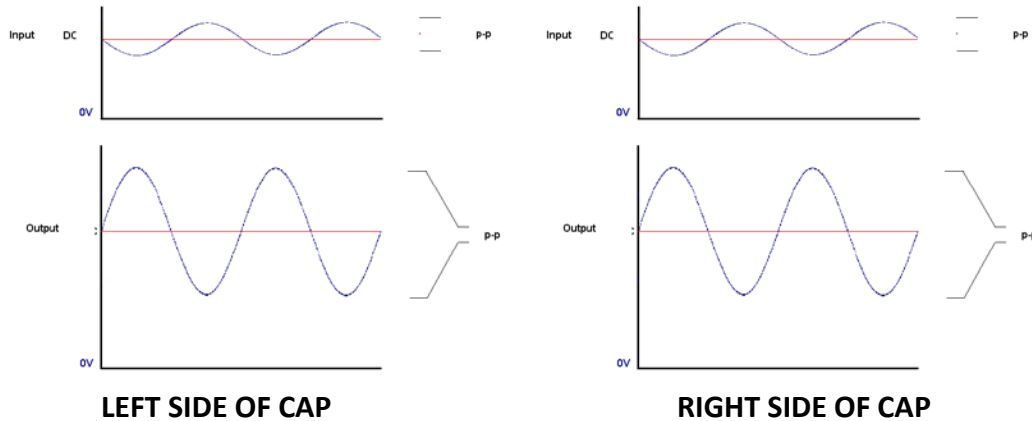

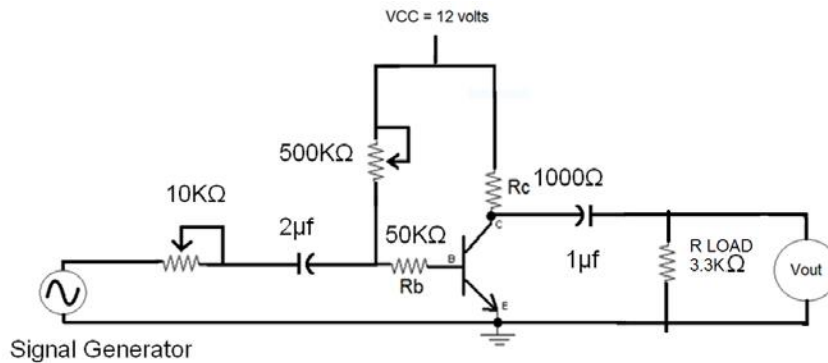53. Connect a load resistor to the amplifier circuit.



54. Connect channel 2 of an oscilloscope where the diagram shows Vout.

55. Adjust the signal generator until you have a 2 volt peak-to-peak signal at the output. Do this at a frequency of 1000 Hz.

56. Once your output is established, measure the input signal with channel 1 of the oscilloscope.

57. Show both the input and the output of the amplifier at the same time on the oscilloscope.

58. Notice the output is out of phase with the input by 180o.






Solid State Electronics – Unit 9: Transistors

Lab 1 - Transistor

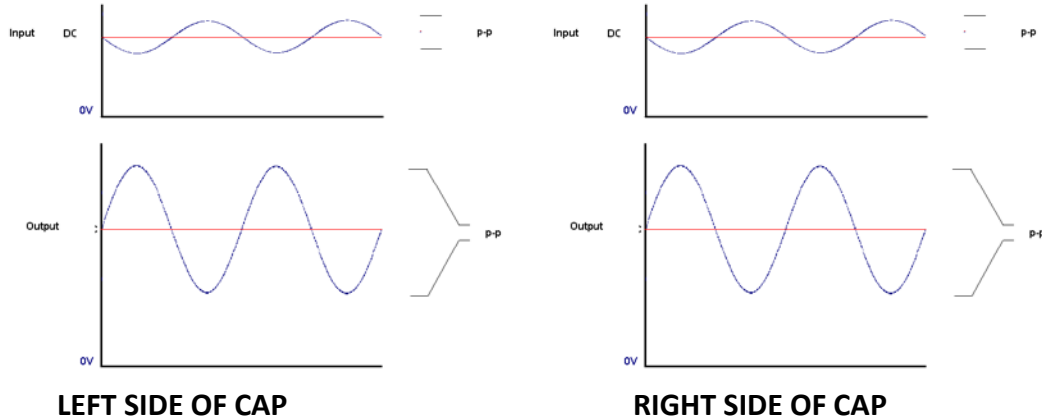59. Fill in your information in the provided waveforms. LEFT SIDE OF CAP RIGHT SIDE OF CAP



60. An amplifier takes a small input signal and multiplies it to make a larger output signal. This is called gain. There is current gain, voltage gain, and power gain.
61. Find the voltage gain of your amplifier circuit with the load. To do this divide the output voltage by the input voltage. Voltage gain is given the variable name AV.

$$AV = V_{out} / V_{in}$$

Your AV = _____

Slowly increase the amplitude of the signal generator while monitoring the output voltage. Increase the input signal until the output just begins to distort. Fill in your information in the provided waveforms.

The circuit used up to this point is not the only circuit used to build an amplifier. In order to acquire a greater circuit stability the following circuit is more common.


62. Connect the following circuit.





Solid State Electronics – Unit 9: Transistors

Lab 1 - Transistor

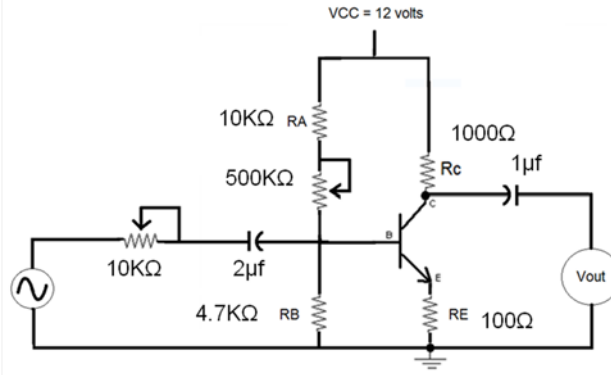


63. Disconnect the signal generator from the circuit. Simply shutting off the signal generator is not the same as disconnecting.
64. Connect a voltmeter across RB.
65. Adjust the 500KΩ pot until you measure 1 volt across RB.
66. Re-connect the signal generator.
67. Connect channel 2 of an oscilloscope where the diagram shows Vout.
68. Adjust the signal generator until you have a 2 volt peak-to-peak signal at the output. Do this at a frequency of 1000 Hz.
69. Once your output is established, measure the input signal with channel 1 of the oscilloscope.
70. Show both the input and the output of the amplifier at the same time on the oscilloscope.
71. Notice the output is out of phase with the input by 180o.
72. Fill in your information in the provided waveforms.





Solid State Electronics – Unit 9: Transistors

Lab 1 - Transistor

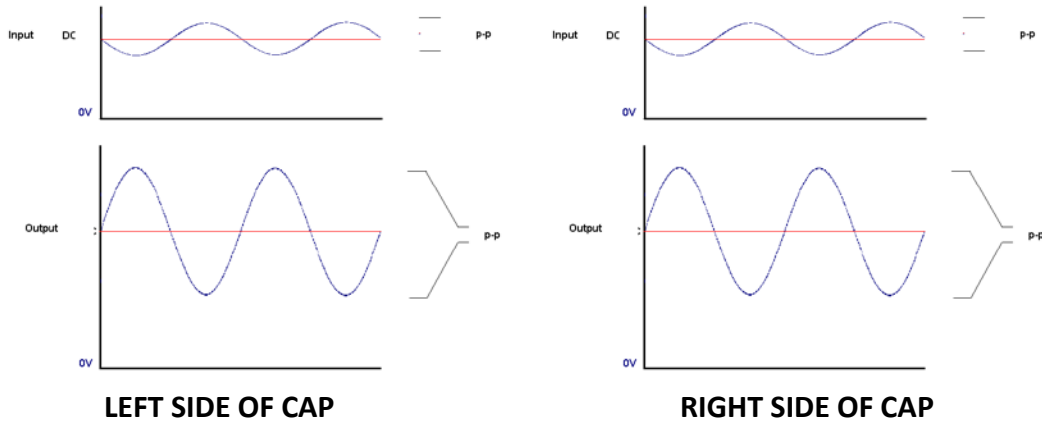


73. An amplifier takes a small input signal and multiplies it to make a larger output signal. This is called gain. There is current gain, voltage gain, and power gain.
74. Find the voltage gain of your amplifier circuit. To do this divide the output voltage by the input voltage. Voltage gain is given the variable name AV.

$$AV = V_{out} / V_{in}$$

Your AV = _____

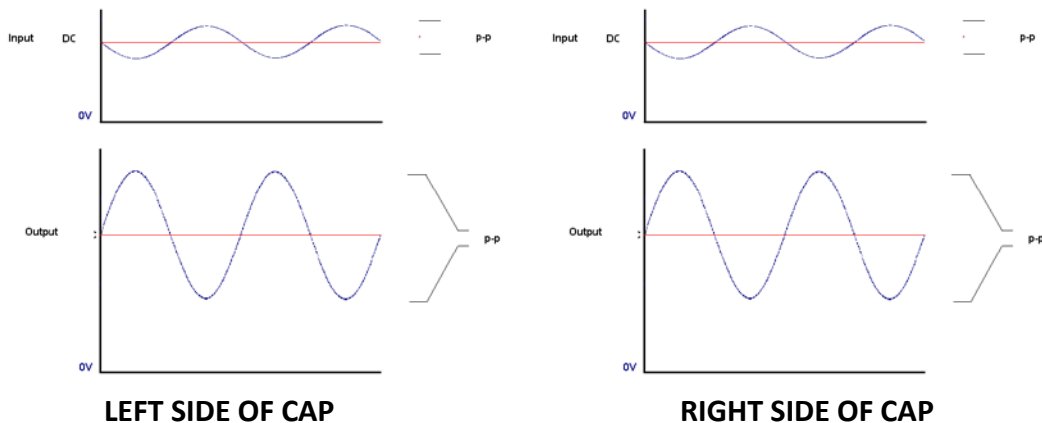Slowly increase the amplitude of the signal generator while monitoring the output voltage. Increase the input signal until the output just begins to distort. Fill in your information in the provided waveforms.







Solid State Electronics – Unit 9: Transistors

Lab 1 - Transistor

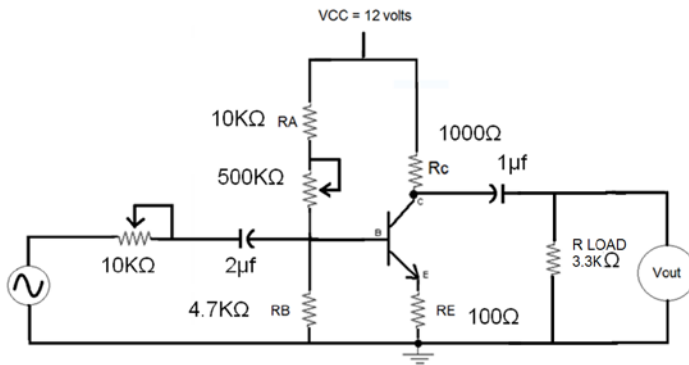75. Connect a load resistor to the amplifier circuit.



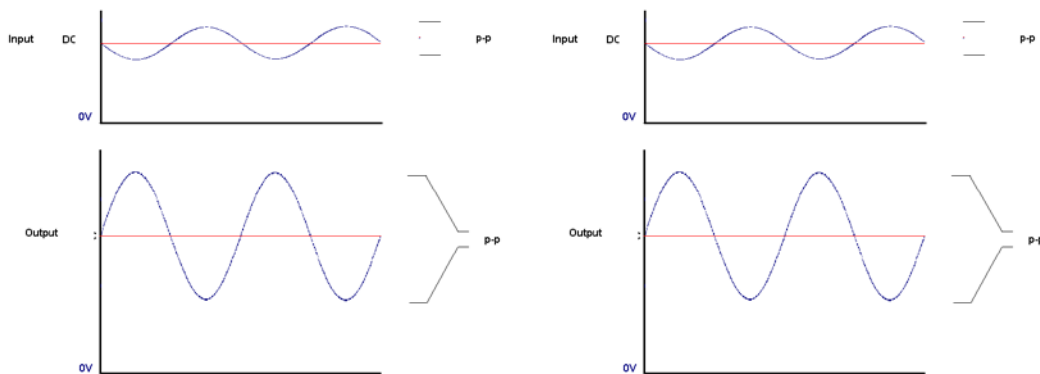76. Connect channel 2 of an oscilloscope where the diagram shows Vout.
77. Adjust the signal generator until you have a 2 volt peak-to-peak signal at the output. Do this at a frequency of 1000 Hz.
78. Once your output is established, measure the input signal with channel 1 of the oscilloscope.
79. Show both the input and the output of the amplifier at the same time on the oscilloscope.
80. Notice the output is out of phase with the input by 180o.
81. Fill in your information in the provided waveforms.



LEFT SIDE OF CAP


RIGHT SIDE OF CAP



Solid State Electronics – Unit 9: Transistors

Lab 1 - Transistor

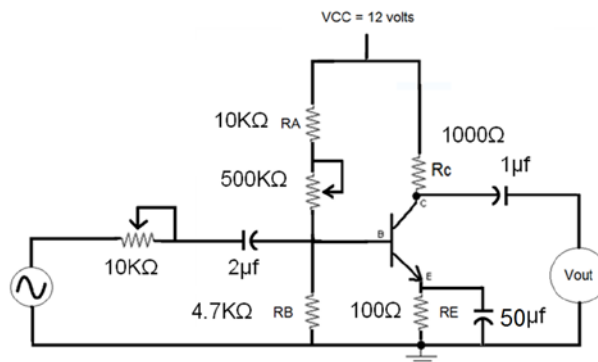82. An amplifier takes a small input signal and multiplies it to make a larger output signal. This is called gain. There is current gain, voltage gain, and power gain.
83. Find the voltage gain of your amplifier circuit with the load. To do this divide the output voltage by the input voltage. Voltage gain is given the variable name AV.
 $AV = V_{out} / V_{in}$
Your AV = _____
Slowly increase the amplitude of the signal generator while monitoring the output voltage. Increase the input signal until the output just begins to distort. Fill in your information in the provided waveforms.
84. Connect the capacitor across RE.



85. Set the input signal to achieve a maximum undistorted output signal.
86. Find the voltage gain of your amplifier circuit with the load. To do this divide the output voltage by the input voltage. Voltage gain is given the variable name AV.
 $AV = V_{out} / V_{in}$
Your AV = _____
The capacitor increases the gain.
87. Disconnect the signal generator.
88. Measure VRA = _____





Solid State Electronics – Unit 9: Transistors


Lab 1 - Transistor

89. Measure V_{RB} = _____
90. Measure V_{RC} = _____
91. Measure V_{RE} = _____
92. Measure V_{CE} = _____
93. Calculate the emitter current = $I_E = V_{RE} / R_E$ _____
94. Calculate the collector current = $I_C = V_{RC} / R_C$ _____
95. Calculate the base current = $I_B = I_E - I_C$ _____
96. The Beta (β) of a transistor is the current gain of the transistor. On the spec sheet of a transistor it is usually called H_{fe} . It is calculated by dividing I_C by I_B . Calculate your Beta.
- $\beta = I_C / I_B =$ _____
97. Construct the following circuit in the electronic simulation software.



Solid State Electronics – Unit 9: Transistors

Lab 1 - Transistor

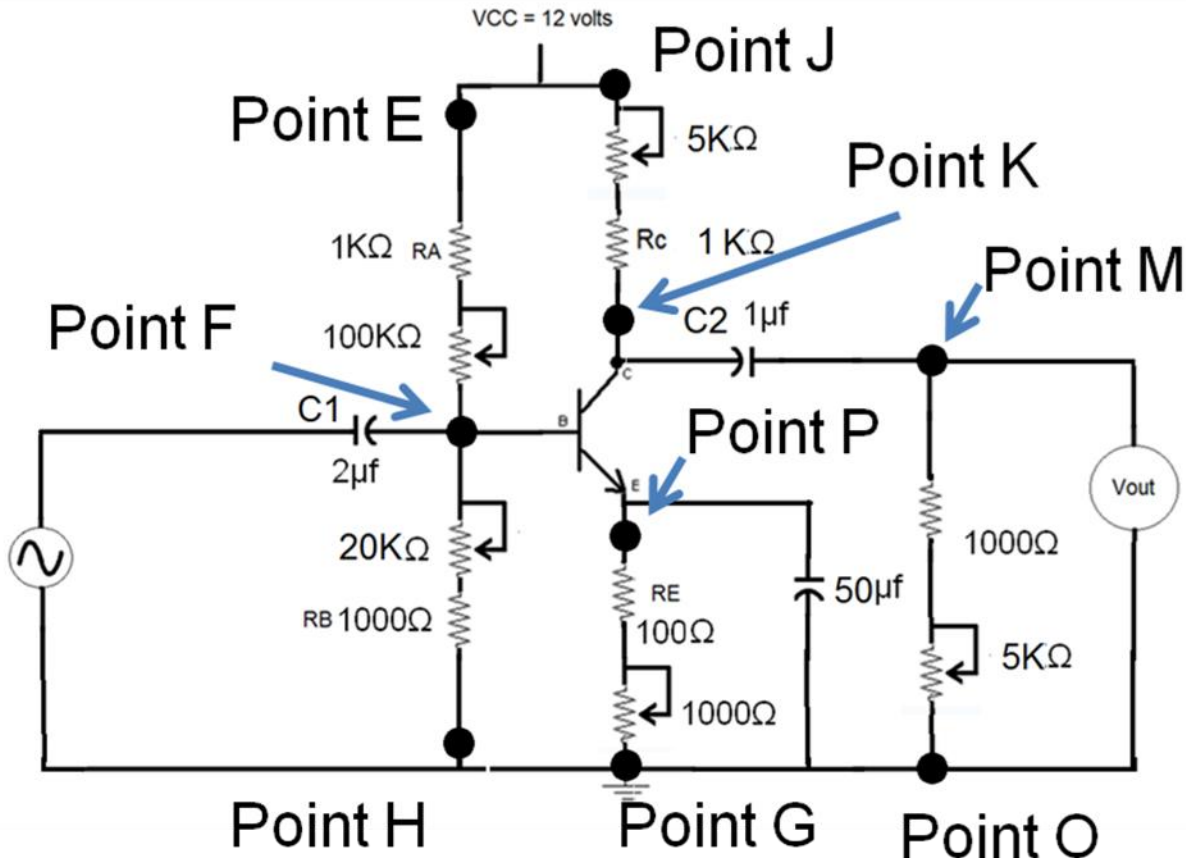

Notice VRL is the voltage across the load. The load in this case is the resistance between points M and O.

VRE is the voltage across RE and the 5000Ω Pot. This is the resistance between points P and G.

VRC is the voltage across RC and the 1000Ω Pot. This is the resistance between points J and K.

VRA is the voltage across RA and the 100KΩ Pot. This is the resistance between points E and F.

VRB is the voltage across RB and the 20KΩ Pot. This is the resistance between points F and H.

These values should be adjusted individually so their reason for being in the circuit can be defined.

98. Develop a detailed data table and graph for the following:





Solid State Electronics – Unit 9: Transistors

Lab 1 - Transistor

1. What happens to VRL as the input frequency is adjusted between 20-20,000 Hz?
2. What happens to VRL as the C1 is varied between .1 μ fd - 20 μ fd?
3. What happens to VRL as the C2 is varied between .1 μ fd - 20 μ fd?
4. What happens to VRL as the VRA is varied between min and max?
5. What happens to VRL as the VRB is varied between. min and max?
6. What happens to VRL as the VRC is varied between. min and max?
7. What happens to VRL as the VRE is varied between. min and max?
8. What happens to VRL as the VRB is varied between. min and max?
9. What happens to VRL as the VRL is varied between. min and max?





**Multi-State
Advanced Manufacturing
Consortium**

US DOL SPONSORED TAACCCT GRANT: TC23767
PRIMARY DEVELOPER: Jim Blair – Henry Ford College

RELEASE DATE 2/22/2016
VERSION v 001
PAGE 26 of 26

Solid State Electronics – Unit 9: Transistors

Lab 1 - Transistor

SAFETY DISCLAIMER:

M-SAMC educational resources are in no way meant to be a substitute for occupational safety and health standards. No guarantee is made to resource thoroughness, statutory or regulatory compliance, and related media may depict situations that are not in compliance with OSHA and other safety requirements. It is the responsibility of educators/employers and their students/employees, or anybody using our resources, to comply fully with all pertinent OSHA, and any other, rules and regulations in any jurisdiction in which they learn/work. M-SAMC will not be liable for any damages or other claims and demands arising out of the use of these educational resources. By using these resources, the user releases the Multi-State Advanced Manufacturing Consortium and participating educational institutions and their respective Boards, individual trustees, employees, contractors, and sub-contractors from any liability for injuries resulting from the use of the educational resources.

DOL DISCLAIMER:

This product was funded by a grant awarded by the U.S. Department of Labor's Employment and Training Administration. The product was created by the grantee and does not necessarily reflect the official position of the U.S. Department of Labor. The Department of Labor makes no guarantees, warranties, or assurances of any kind, express or implied, with respect to such information, including any information on linked sites and including, but not limited to, accuracy of the information or its completeness, timeliness, usefulness, adequacy, continued availability, or ownership.

RELEVANCY REMINDER:

M-SAMC resources reflect a shared understanding of grant partners at the time of development. In keeping with our industry and college partner requirements, our products are continuously improved. Updated versions of our work can be found here: <http://www.msamc.org/resources.html>.

