


 VERSION
 v 001

 PAGE
 1 of 6

US DOL SPONSORED TAACCCT GRANT: TC23767
PRIMARY DEVELOPER: Jim Blair – Henry Ford College

Basic Electricity – Unit 6: Other Basic Circuit FundamentalsLab 1

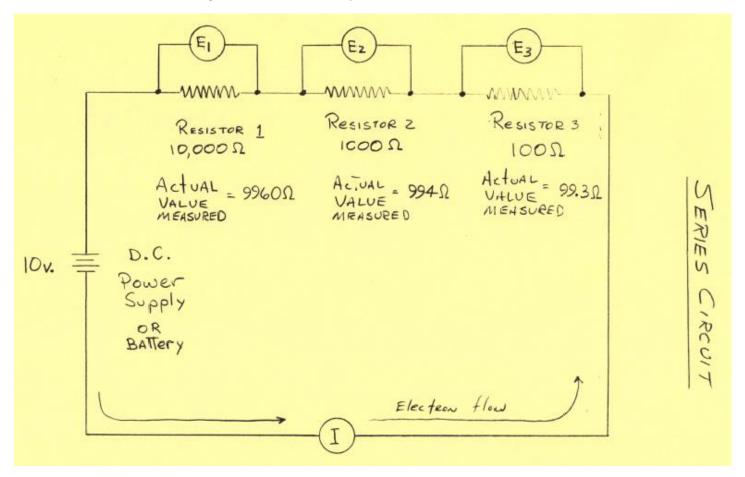Instructions: Solve the following series circuit and verify the results in the lab.







VERSION v 001
PAGE 2 of 6


2/22/2016

RELEASE DATE

US DOL SPONSORED TAACCCT GRANT: TC23767
PRIMARY DEVELOPER: Jim Blair – Henry Ford College

Basic Electricity – Unit 6: Other Basic Circuit Fundamentals *Lab 1*

Solution:

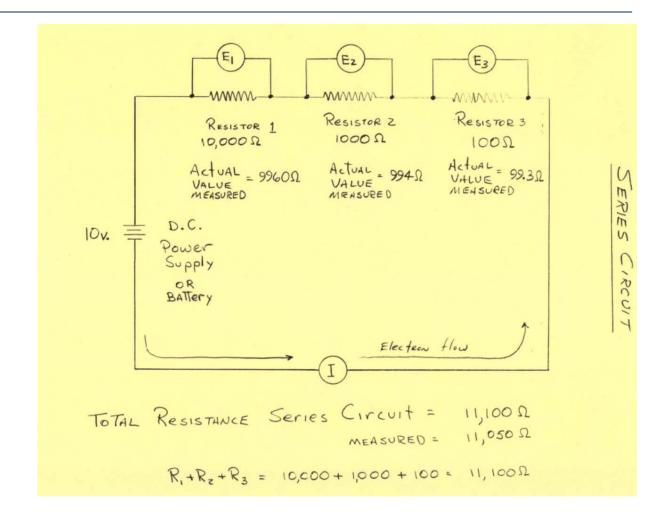







US DOL SPONSORED TAACCCT GRANT: TC23767

 RELEASE DATE
 2/22/2016

 VERSION
 v 001

 PAGE
 3 of 6

Basic Electricity – Unit 6: Other Basic Circuit FundamentalsLab 1

PRIMARY DEVELOPER: Jim Blair - Henry Ford College

TOTAL VOLTAGE = 10 V GIVEN TOTAL RESISTANCE = R. +Rz+R3 = 11,1000 TOTAL Current I = ETOTAL = 1000 = .0009009A OR . 9 mA RULE #1 SINCE This IS A SERIES CIRCUIT, THE current through EACH RESISTOR IS THE SAME AND IS EQUAL TO THE TOTAL CURRENT. I through R1 = .0009009 A. I through Rz = . cco oco A. I through R3 = . 00000000 A. therefore I, = Iz = Iz = IT







VERSION v 001 PAGE 4 of 6

2/22/2016

RELEASE DATE

US DOL SPONSORED TAACCCT GRANT: TC23767
PRIMARY DEVELOPER: Jim Blair – Henry Ford College

Basic Electricity – Unit 6: Other Basic Circuit Fundamentals *Lab 1*

Since Voltage (E) is Equal to current times Resistance:

Voltage across
$$R_1 = (I_1) \times (R_1) = E_1$$

Voltage across $R_2 = (I_2) \times (R_2) = E_2$

Voltage Across $R_3 = (I_3) \times (R_3) = E_3$

Then this means

 $E_1 = (.0009009 \text{ A}) \times (10000) = 9.009 \text{ V}.$
 $E_2 = (.0009009 \text{ A}) \times (10000) = .09009 \text{ V}.$
 $E_3 = (.0009009 \text{ A}) \times (10000) = .09009 \text{ V}.$

NOTE: VALUES ROLLED .09009 WHEN ACTUAL MEASUREMENTS WERE THEEN:

 E_1 MEASURED 9.01 V

 E_2 MEASURED .900

 E_3 MEASURED .900

 E_3 MEASURED .900

 E_3 MEASURED .900







 VERSION
 v 001

 PAGE
 5 of 6

US DOL SPONSORED TAACCCT GRANT: TC23767
PRIMARY DEVELOPER: Jim Blair – Henry Ford College

Basic Electricity – Unit 6: Other Basic Circuit Fundamentals *Lab 1*

RULE #2 The VOLTAGES AROUND A SEries CIRCUIT ADD UP TO EQUAL THE TOTAL Supply VOLTAGE. there fore: USING THE CALCULATED VALUES FOR E_1 , E_2 , E_3 E, = 9.009 V. Ez = .9009 V. E3 = ,09009 V. 9.99999 v. USING MEASURED VALUES. E, = 9.0/v Ez = .900 V E3 = + . 0899 V







US DOL SPONSORED TAACCCT GRANT: TC23767
PRIMARY DEVELOPER: Jim Blair – Henry Ford College

 RELEASE DATE
 2/22/2016

 VERSION
 v 001

 PAGE
 6 of 6

Basic Electricity – Unit 6: Other Basic Circuit Fundamentals *Lab 1*

SAFETY DISCLAIMER:

M-SAMC educational resources are in no way meant to be a substitute for occupational safety and health standards. No guarantee is made to resource thoroughness, statutory or regulatory compliance, and related media may depict situations that are not in compliance with OSHA and other safety requirements. It is the responsibility of educators/employers and their students/employees, or anybody using our resources, to comply fully with all pertinent OSHA, and any other, rules and regulations in any jurisdiction in which they learn/work. M-SAMC will not be liable for any damages or other claims and demands arising out of the use of these educational resources. By using these resources, the user releases the Multi-State Advanced Manufacturing Consortium and participating educational institutions and their respective Boards, individual trustees, employees, contractors, and subcontractors from any liability for injuries resulting from the use of the educational resources.

DOL DISCLAIMER:

This product was funded by a grant awarded by the U.S. Department of Labor's Employment and Training Administration. The product was created by the grantee and does not necessarily reflect the official position of the U.S. Department of Labor. The Department of Labor makes no guarantees, warranties, or assurances of any kind, express or implied, with respect to such information, including any information on linked sites and including, but not limited to, accuracy of the information or its completeness, timeliness, usefulness, adequacy, continued availability, or ownership.

RELEVANCY REMINDER:

M-SAMC resources reflect a shared understanding of grant partners at the time of development. In keeping with our industry and college partner requirements, our products are continuously improved. Updated versions of our work can be found here: http://www.msamc.org/resources.html.



