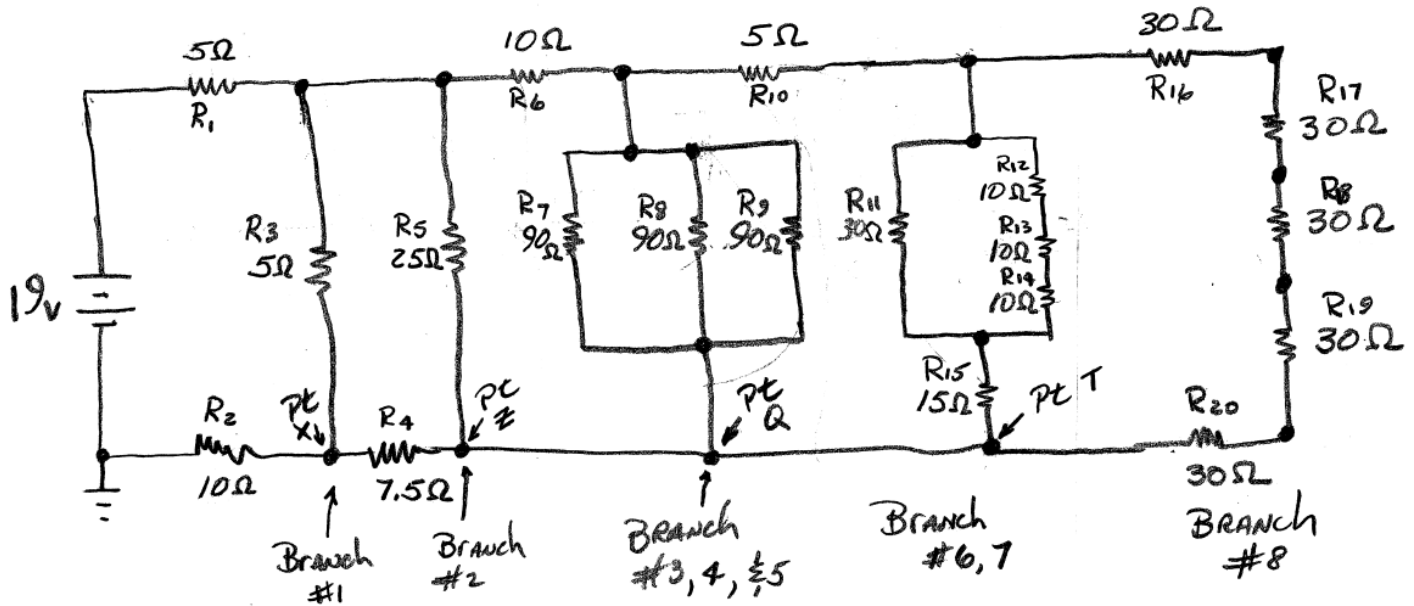




Basic Electricity – Unit 6: Other Basic Circuit Fundamentals

Homework 4

Instructions: Solve the following circuit.






Basic Electricity – Unit 6: Other Basic Circuit Fundamentals

Homework 4






Solution:

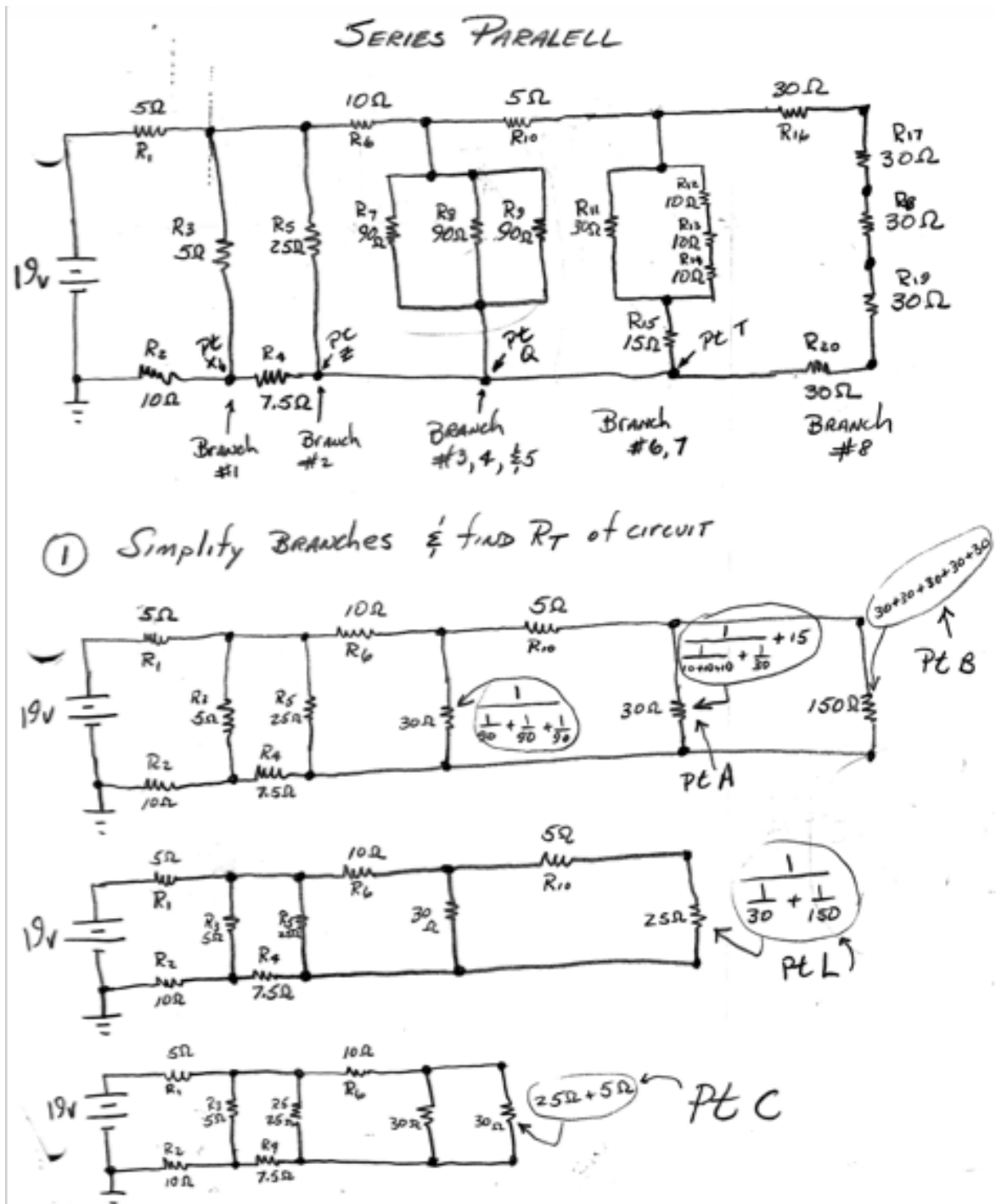



Basic Electricity – Unit 6: Other Basic Circuit Fundamentals

Homework 4

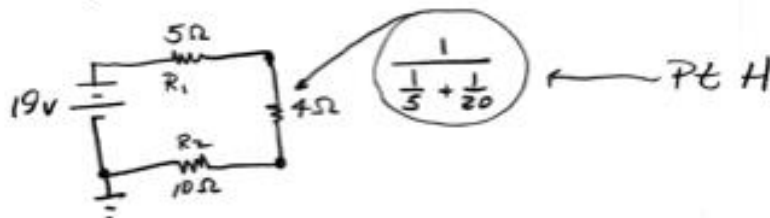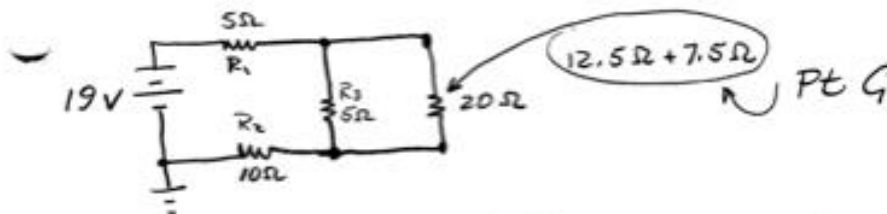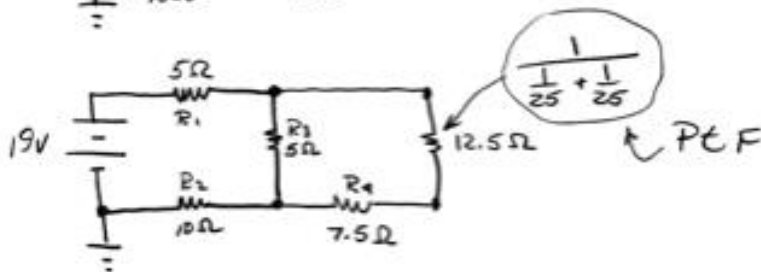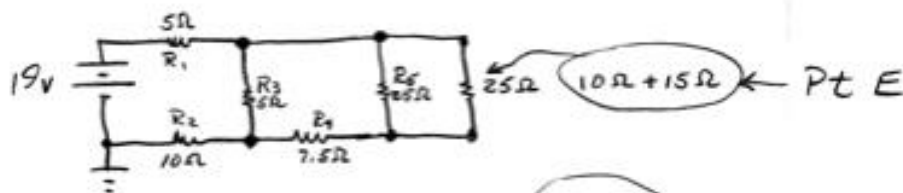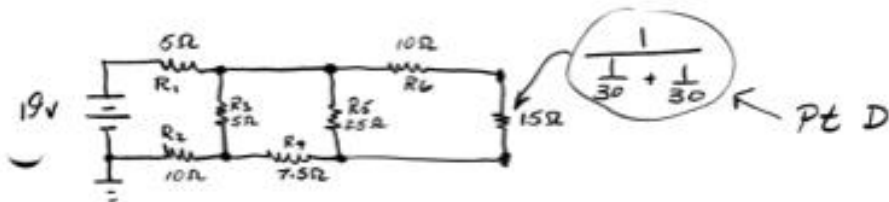

Now $R_T = 5\Omega + 4\Omega + 10\Omega$ Pt G

$R_T = 19\Omega$

To get R_T on calculator press the keys on next page.

Once R_T is found I_T of TOTAL Circuit should be found.





Basic Electricity – Unit 6: Other Basic Circuit Fundamentals

Homework 4

Handwritten calculations for circuit analysis:

$$10 + 10 = 1/k + 30 = 1/k = 1/k + 15 = 1/k = 1/k + 570 = P_{TA}$$

$$30 + 30 + 30 + 30 + 30 = 1/k = 1/k + 1$$

$$+ 5 = P_{TC} = 1/k + 30 = 1/k = P_{TD} + 10 = P_{TE}$$

$$1/k + 25 = 1/k = 1/k = P_{TF} + 7.5 = P_{TG} + 5 = 1/k =$$

$$1/k = P_{TH} + 5 + 10 = R_{T} = P_{TG}$$

$$R_{T} = 19 \Omega$$

$$\therefore I_T = \frac{E_T}{R_T}$$

$$= \frac{19.0V}{19 \Omega}$$

$$= 1 \text{ Amp} = 1000 \text{ Milliamps}$$

This means 1 Amp flows through R_1 & R_2 (flows through R_2 at start of flow & through R_1 on return of flow)

$\therefore (1A)(5\Omega) = V_{R_1} = 5.0V$
 $(1A)(10\Omega) = V_{R_2} = 10.0V$

for I_T TOTAL CIRCUIT





Basic Electricity – Unit 6: Other Basic Circuit Fundamentals

Homework 4

Since these voltages are dropped across $R_1 \neq R_2$ Subtract from Supply.

(2) $V_{R_3} = V_T - V_{R_1} - V_{R_2} = 19V - 5V - 10V = 4.0V$

(3) Since R_3 in parallel with supply
4.0V across R_3

$$I_{R_3} = \frac{V_{R_3}}{R_3} = \frac{4.0V}{5\Omega} = .8A = 800ma$$

current out of pt X = current into pt X.
↓
= 1 Amp (from step 1)

since part of this 1 Amp flows through $R_3 \neq$ some through R_4 (see circuit)
we know 800ma goes through R_3
the rest goes through R_4 .

$$\begin{aligned} \therefore I_{R_4} &= I_{R_2} - I_{R_3} = \\ &= 1000ma - 800ma \\ &= 200ma \end{aligned}$$

$$\begin{aligned} V_{R_4} &= (I_{R_4})(R_4) \\ &= (200ma)(7.5\Omega) \\ &= 1.5V \end{aligned}$$

(4) $V_{R_5} = V_{R_3} - V_{R_4} = V_{\text{branch previous}} - V_{\text{series drop}}$

$$\begin{aligned} &= 4.0V - 1.5V \\ &= 2.5V \end{aligned}$$

$$I_{R_5} = \frac{V_{R_5}}{R_5} = \frac{2.5V}{25\Omega} = .1A = 100ma$$





Basic Electricity – Unit 6: Other Basic Circuit Fundamentals


Homework 4

current into pt Z = current out of pt Z.
Can treat R_6 like it is at bottom of circuit

$$\begin{aligned} \therefore IR_6 &= IR_4 - IR_5 \\ &= 200\text{ma} - 100\text{ma} \\ &= 100\text{ma} \end{aligned}$$

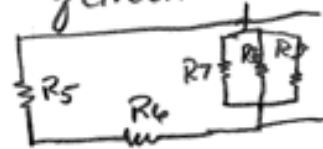(5)

$$\begin{aligned} VR_6 &= (100\text{ma})(10\Omega) \\ &= (.1)(10\Omega) \\ &= 1.0\text{v} \end{aligned}$$



(6)

Since $R_7, R_8 \text{ \& } R_9$ are all in parallel all have the same voltage across them.

$$\begin{aligned} VR_7 = VR_8 = VR_9 &= VR_5 - VR_6 = V_{\text{Branch previous}} - V_{\text{series drop}} \\ &= 1.5\text{v} \end{aligned}$$

$IR_7 = IR_8 = IR_9$ is equal in value since they are same value resistors.

$$IR_7 = IR_8 = IR_9 = \frac{ER_7, ER_8 \text{ \& } ER_9}{R_7, R_8 \text{ \& } R_9}$$

$$= \frac{1.5\text{v}}{90\text{v}}$$

$$= .016666666\text{ A}$$

$$= 17\text{ma through } R_7, R_8 \text{ \& } R_9$$

Note:
ALL 3 R's
HAVE 1.5V across them
& 17ma of current
through them





Basic Electricity – Unit 6: Other Basic Circuit Fundamentals

Homework 4


7) Do like R_7, R_6
current into pt Q = current out of pt Q

$$\begin{aligned}\therefore I_{R_{10}} &= I_{R_6} - I_{R_7} - I_{R_8} - I_{R_9} \\ &= .1 - .0166666666 - .0166666666 - .0166666666 \\ &= 100\text{ma} - 17\text{ma} - 17\text{ma} - 17\text{ma} \\ &= .05\text{A} \\ &= 50\text{ma}\end{aligned}$$

$$\begin{aligned}V_{R_{10}} &= (I_{R_{10}})(R_{10}) \\ &= (50\text{ma})(5\Omega) \\ &= (.05)(5\Omega) \\ &= .25\text{V}\end{aligned}$$

8)

Next:
CALCULATE
THIS BRANCH
OF CIRCUIT.

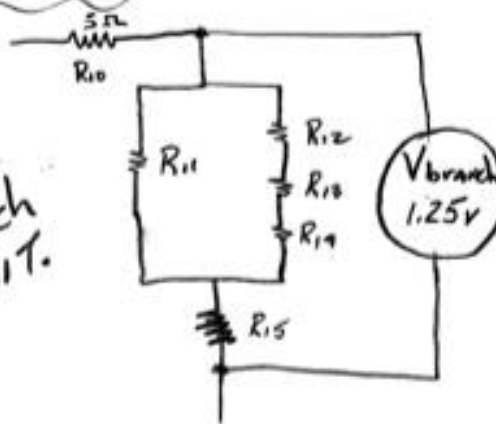

$$\begin{aligned}V_{\text{branch}} &= V_{\text{branch Previous}} - V_{R_{10}} = \\ &= 1.5\text{V} - .25\text{V} \\ &= 1.25\text{V}\end{aligned}$$



Basic Electricity – Unit 6: Other Basic Circuit Fundamentals

Homework 4

Since this branch is a series parallel branch need to find R_t of the branch

$$\therefore R_t = \frac{1}{\frac{1}{10\Omega + 10\Omega + 10\Omega} + \frac{1}{30\Omega}} + 15\Omega$$

$$\boxed{10} + \boxed{10} + \boxed{10} = \boxed{\frac{1}{x}} + \boxed{30} \boxed{\frac{1}{x}} = \boxed{\frac{1}{x}}$$
$$\boxed{+ 15} =$$

$$= 30\Omega$$

$$I_{\text{branch}} = \frac{V_{\text{branch}}}{R_{T \text{ branch}}}$$

$$= \frac{1.25V}{30\Omega}$$

$$= .041666666 A$$

$$= 41.7 \text{ ma}$$

this current all flows through R_{15} (series)

$$\therefore I_{R_{15}} = 41.7 \text{ ma}$$

this is split 2 ways half through R_{11} the other half through the 3 series resistors R_{12} , R_{13} , R_{14} it splits in half since both branch R_t 's = 30Ω


$$\therefore I_{R_{11}} = .020833333 A = I_{12} = I_{13} = I_{14} = 20.8 \text{ ma}$$





Basic Electricity – Unit 6: Other Basic Circuit Fundamentals

Homework 4

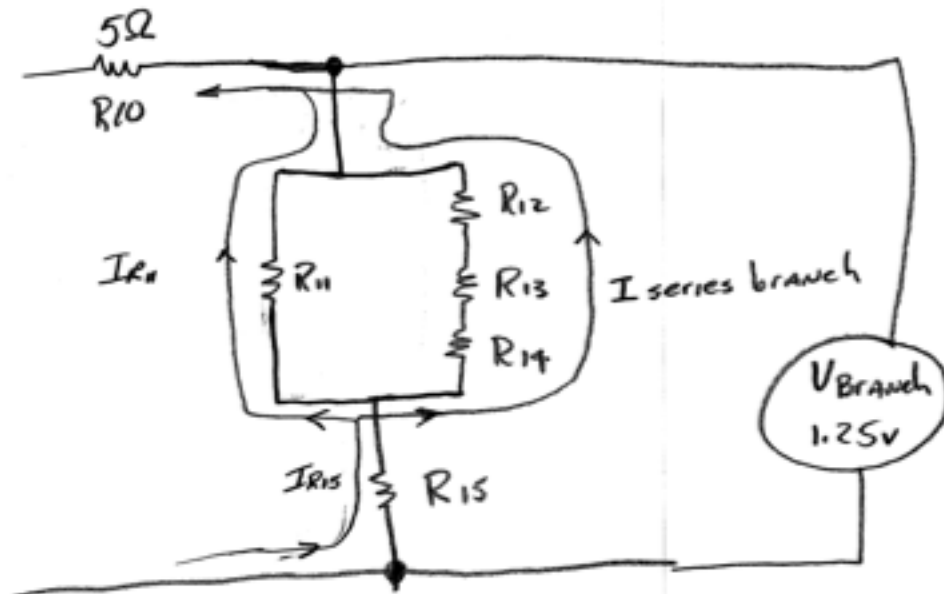

$$I_{R15} = 41.7 \text{ ma}$$

$$I_{R11} = 20.8 \text{ ma}$$

$$I_{R12} = 20.8 \text{ ma}$$

$$I_{R13} = 20.8 \text{ ma}$$

$$I_{R14} = 20.8 \text{ ma}$$

VOLTAGES $V = I \times R$

$$V_{R15} = (I_{R15})(R_{15}) = (41.7 \text{ ma})(15\Omega) = .615 \text{ V} = 615 \text{ mV}$$

$$V_{R11} = (I_{R11})(R_{11}) = (20.8 \text{ ma})(30\Omega) = .624 \text{ V} = 624 \text{ mV}$$

$$V_{R12} = (I_{R12})(R_{12}) = (20.8 \text{ ma})(10\Omega) = .208 \text{ V} = 208 \text{ mV}$$

$$V_{R13} = (I_{R13})(R_{13}) = (20.8 \text{ ma})(10\Omega) = .208 \text{ V} = 208 \text{ mV}$$

$$V_{R14} = (I_{R14})(R_{14}) = (20.8 \text{ ma})(10\Omega) = .208 \text{ V} = 208 \text{ mV}$$

$$V_{R12} + V_{R13} + V_{R14} \text{ should} = V_{R11}$$

$$\frac{1}{2} V_{R11} + V_{R15} = V_{\text{branch}} = V_{R12} + V_{R13} + V_{R14} + V_{R15}$$

[elec_103.2.6_6_homework4_v1_20160222.pdf](#) found in [Resources](#) by





Basic Electricity – Unit 6: Other Basic Circuit Fundamentals

Homework 4

⑨ the rest of the resistors are in series with each other but in parallel with the circuit.

$$\begin{aligned} \text{ii } V_{\text{across}} &= V_{\text{across}} \\ \text{Remaining} & \text{ previous} \\ \text{R's} & \text{ branch} \\ &= 1.25\text{V} \end{aligned}$$

R_t of remaining branch

$$\begin{aligned} R_t &= 30\Omega + 30\Omega + 30\Omega + 30\Omega + 30\Omega \\ &= 150\Omega \end{aligned}$$

$$I_{\text{remaining branch}} = \frac{V_{\text{remaining branch}}}{R_t \text{ remaining branch}}$$

$$= \frac{1.25\text{V}}{150\Omega}$$

$$= 0.008333333\text{ A}$$

$$= 8.33\text{ mA}$$

$$V_{R16} = (I_{R16})(R_{16}) = (8.33\text{ mA})(30\Omega) = 0.25\text{V}$$

$$V_{R17} = (I_{R17})(R_{17}) = (\text{ " })(30\Omega) = 0.25\text{V}$$

$$V_{R18} = (I_{R18})(R_{18}) = (\text{ " })(30\Omega) = 0.25\text{V}$$

$$V_{R19} = (I_{R19})(R_{19}) = (\text{ " })(30\Omega) = 0.25\text{V}$$

$$V_{R20} = (I_{R20})(R_{20}) = (\text{ " })(30\Omega) = 0.25\text{V}$$

[elec_103.2.6_6_homework4_v1_20160222.pdf](#) found in [Resources](#) by





Basic Electricity – Unit 6: Other Basic Circuit Fundamentals

Homework 4

IF CIRCUIT IS SOLVED CORRECTLY ALL VOLTAGE DROPS
AROUND OUTSIDE OF CIRCUIT WILL EQUAL SUPPLY VOLTAGE.

$$\begin{aligned} \therefore V_{R_1} + V_{R_6} + V_{R_{10}} + V_{R_{16}} + V_{R_{17}} + V_{R_{18}} + V_{R_{19}} + V_{R_{20}} + V_{R_4} + V_{R_2} &= V_{T_{EM}} \\ 5V + 1.0V + .25V + .25V + .25V + .25V + .25V + .25V + 1.5V + 10.0V &= 19V \end{aligned}$$

$$V_{TOTAL} = 19V$$

$$\text{Sum of OUTSIDE VOLTAGE DROPS} = 19V$$

Also the currents through the PARALLEL BRANCHES
will EQUAL I_{TOTAL} of CIRCUIT.

$$\begin{aligned} I_{BRANCH_1} + I_{BRANCH_2} + I_{BRANCH_3} + I_{BRANCH_4} + I_{BRANCH_5} \\ + I_{BRANCH_6} + I_{BRANCH_7} + I_{BRANCH_8} \\ \text{should EQUAL } I_{TOTAL} \end{aligned}$$

$$I_{TOTAL} = 1 \text{ AMP}$$

$$\begin{aligned} I_{B_1} + I_{B_2} + I_{B_3} + I_{B_4} + I_{B_5} + I_{B_6} + I_{B_7} + I_{B_8} &\stackrel{?}{=} 1 \text{ AMP} \\ .8A + .1A + .017A + .017A + .017 + .0417 + \text{NOT USED} + .00833A &= \end{aligned}$$

NOTE I_{B_7} NOT USED

SINCE I flow in branch
6, 7 all goes through

R_{15} USE THAT VALUE

$$\text{TOTAL BRANCH CURRENTS} = 1.00103 \text{ A}$$

$$I_{TOTAL} \text{ of CIRCUIT} = 1 \text{ AMP}$$





Basic Electricity – Unit 6: Other Basic Circuit Fundamentals

Homework 4

Note if ACTUAL CALCULATOR VALUES USED
IT WORKS EXACT.


TO SEE:

$$I_{B1} = \frac{V_{R3}}{R_3} \quad I_{B2} = \frac{V_{R5}}{R_5} \quad I_{B3} = \frac{V_{R_{B3}}}{R_{T_{B3}}}$$

$$I_{B4} = \frac{V_{R_{B4}}}{R_{T_{B4}}} \quad I_{B5} = \frac{V_{R_{B5}}}{R_{T_{B5}}}$$

$$I_{B1} = \frac{4.0V}{5\Omega} \quad I_{B2} = \frac{2.5V}{25\Omega} \quad I_{B3} = \frac{1.5V}{30\Omega}$$
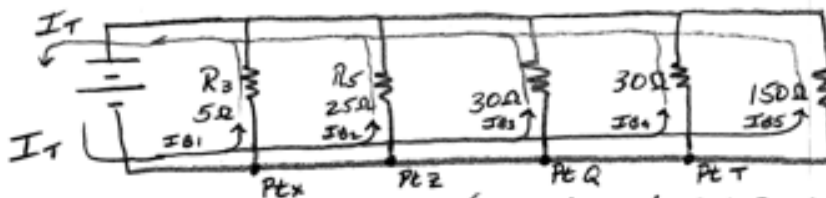
$$I_{B4} = \frac{1.25V}{30\Omega} \quad I_{B5} = \frac{1.25V}{150\Omega}$$



What was done. forget out side resistors
make EQUIVALENT CIRCUIT of INSIDE BRANCHES

$$I_{B1} + I_{B2} + I_{B3} + I_{B4} + I_{B5}$$

$$.8A + .1A + .05A + .041666666 + .008333333$$

$$= 1 \text{ Amp}$$

∴ Correct





Basic Electricity – Unit 6: Other Basic Circuit Fundamentals

Homework 4

Power can also be calculated.

The power delivered by the supply

$$\begin{aligned} P &= I \times E \\ &= (1 \text{ amp})(19 \text{ v}) \\ &= 19 \text{ watts} \end{aligned}$$

This ALSO EQUALS the power consumed by the load or circuit.

The power dissipated is EQUAL TO the power consumed by the load

Power dissipated by a resistor

$$P = I^2 R$$

$(I_1)^2 R_1 = (1 \text{ A})^2 (5 \Omega) = 5 \text{ W}$	$(I_{13})^2 R_{13} = (.0208 \text{ A})^2 (10 \Omega) = .0043264 \text{ W}$
$(I_2)^2 R_2 = (1 \text{ A})^2 (10 \Omega) = 10 \text{ W}$	$(I_{14})^2 R_{14} = (.0208 \text{ A})^2 (10 \Omega) = .0043264 \text{ W}$
$(I_3)^2 R_3 = (.8 \text{ A})^2 (5 \Omega) = 3.2 \text{ W}$	$(I_{15})^2 R_{15} = (.0417 \text{ A})^2 (15 \Omega) = .02608335 \text{ W}$
$(I_4)^2 R_4 = (.2 \text{ A})^2 (7.5 \Omega) = .3 \text{ W}$	$(I_{16})^2 R_{16} = (.00833 \text{ A})^2 (30 \Omega) = .002081667 \text{ W}$
$(I_5)^2 R_5 = (.1 \text{ A})^2 (2.5 \Omega) = .25 \text{ W}$	$(I_{17})^2 R_{17} = \text{''} \text{''} = \text{''} \text{ W}$
$(I_6)^2 R_6 = (.1 \text{ A})^2 (10 \Omega) = .1 \text{ W}$	$(I_{18})^2 R_{18} = \text{''} \text{''} = \text{''} \text{ W}$
$(I_7)^2 R_7 = (.017 \text{ A})^2 (90 \Omega) = .02601 \text{ W}$	$(I_{19})^2 R_{19} = \text{''} \text{''} = \text{''} \text{ W}$
$(I_8)^2 R_8 = (.017 \text{ A})^2 (90 \Omega) = .02601 \text{ W}$	$(I_{20})^2 R_{20} = \text{''} \text{''} = \text{''} \text{ W}$
$(I_9)^2 R_9 = (.017 \text{ A})^2 (90 \Omega) = .02601 \text{ W}$	
$(I_{10})^2 R_{10} = (.050 \text{ A})^2 (5 \Omega) = .0125 \text{ W}$	
$(I_{11})^2 R_{11} = (.0208 \text{ A})^2 (30 \Omega) = .0129792 \text{ W}$	
$(I_{12})^2 R_{12} = (.0208 \text{ A})^2 (10 \Omega) = .0043264 \text{ W}$	


TOTAL of ALL
= 19.00260614 W
WOULD COME OUT EXACT
IF EXACT I VALUES
WERE USED.





Basic Electricity – Unit 6: Other Basic Circuit Fundamentals


Homework 4

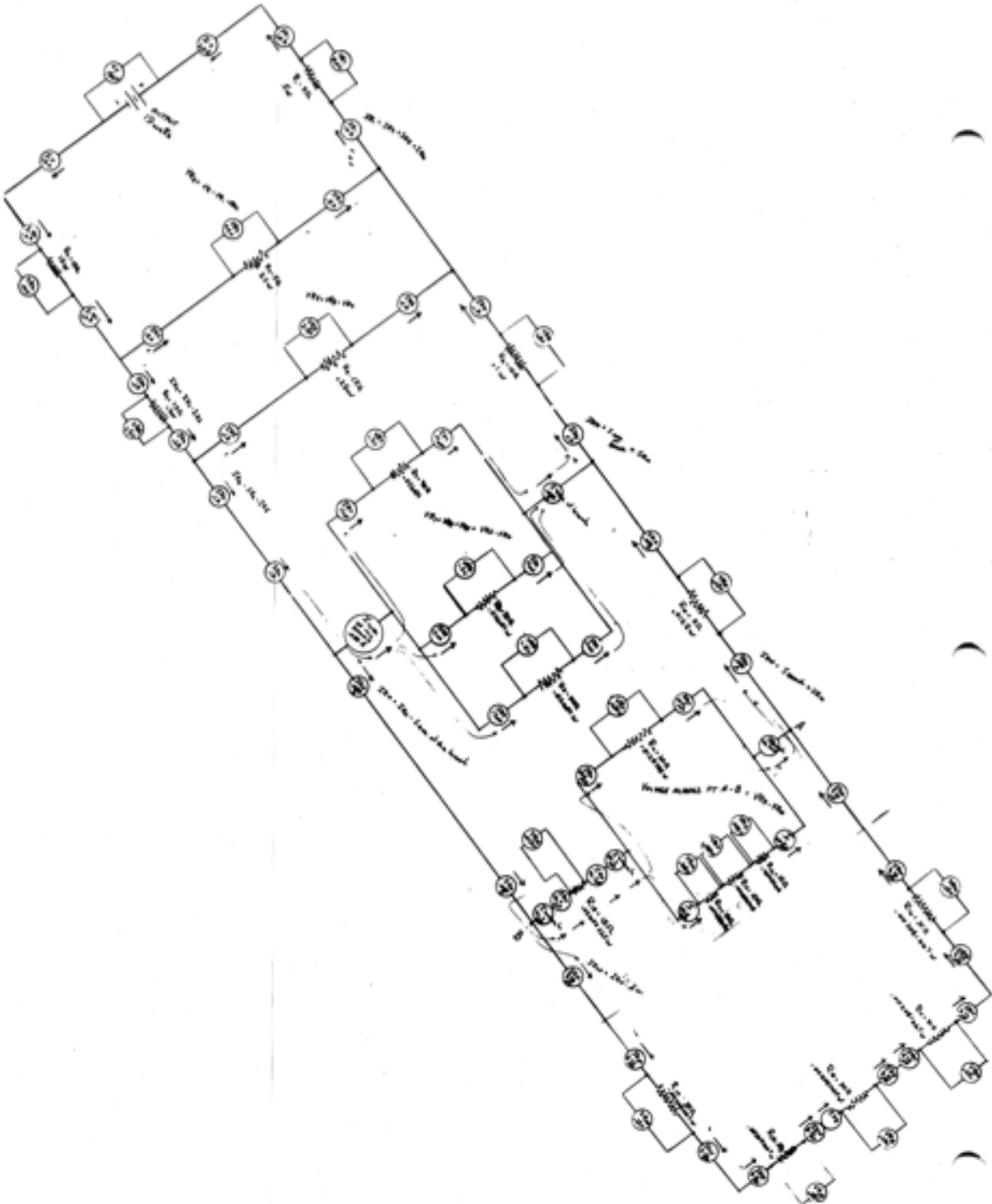



Basic Electricity – Unit 6: Other Basic Circuit Fundamentals


Homework 4

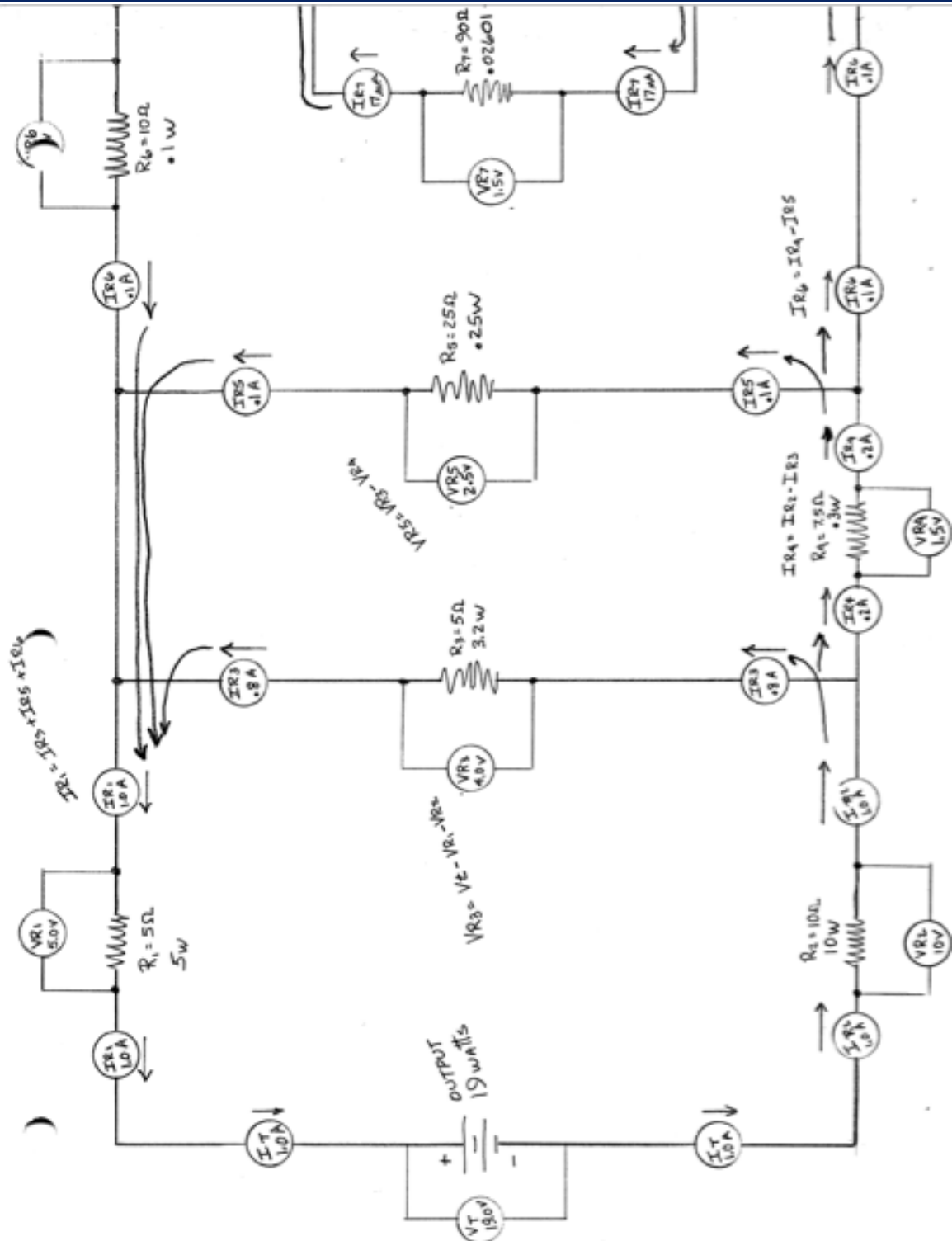



Basic Electricity – Unit 6: Other Basic Circuit Fundamentals


Homework 4

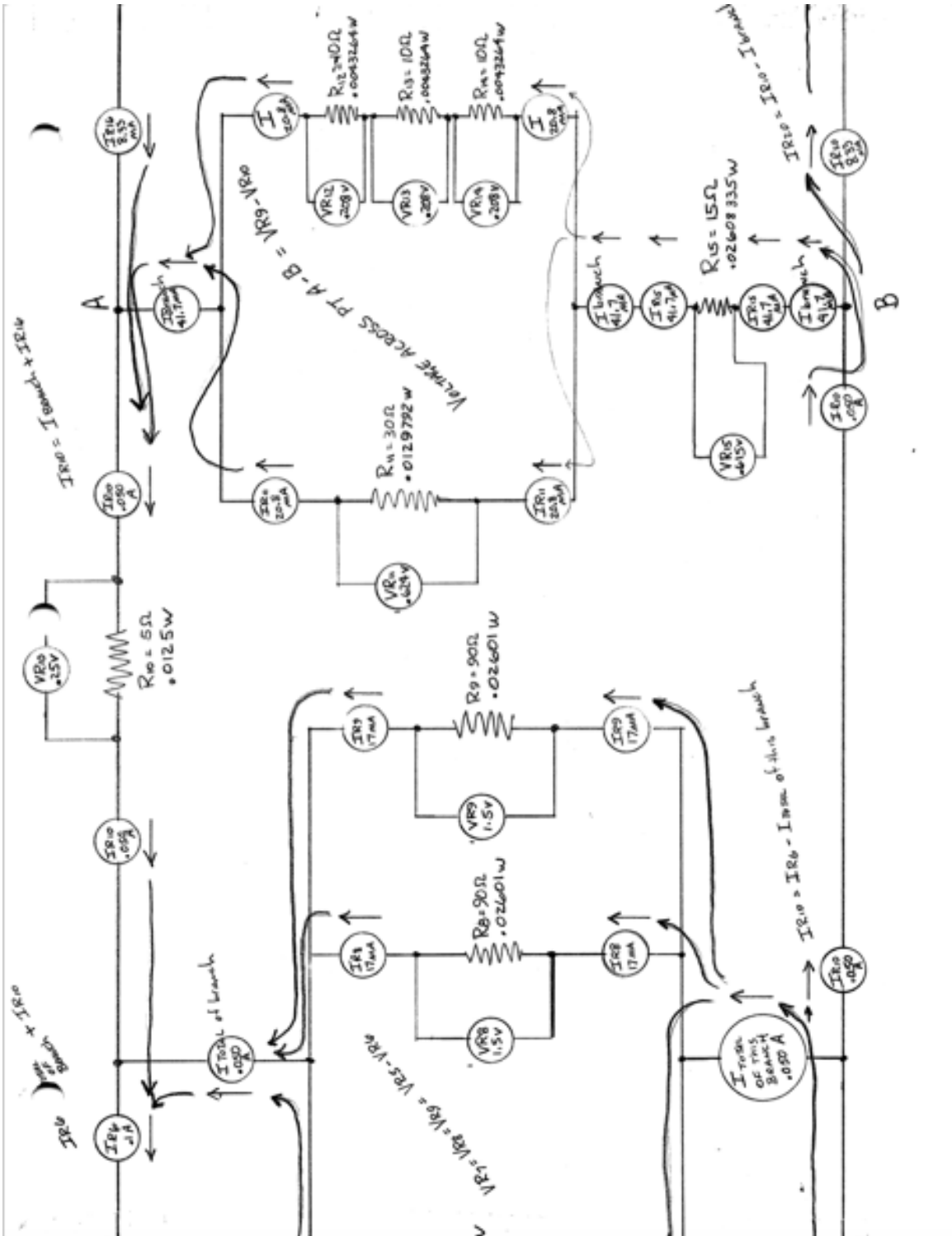



Basic Electricity – Unit 6: Other Basic Circuit Fundamentals

Homework 4

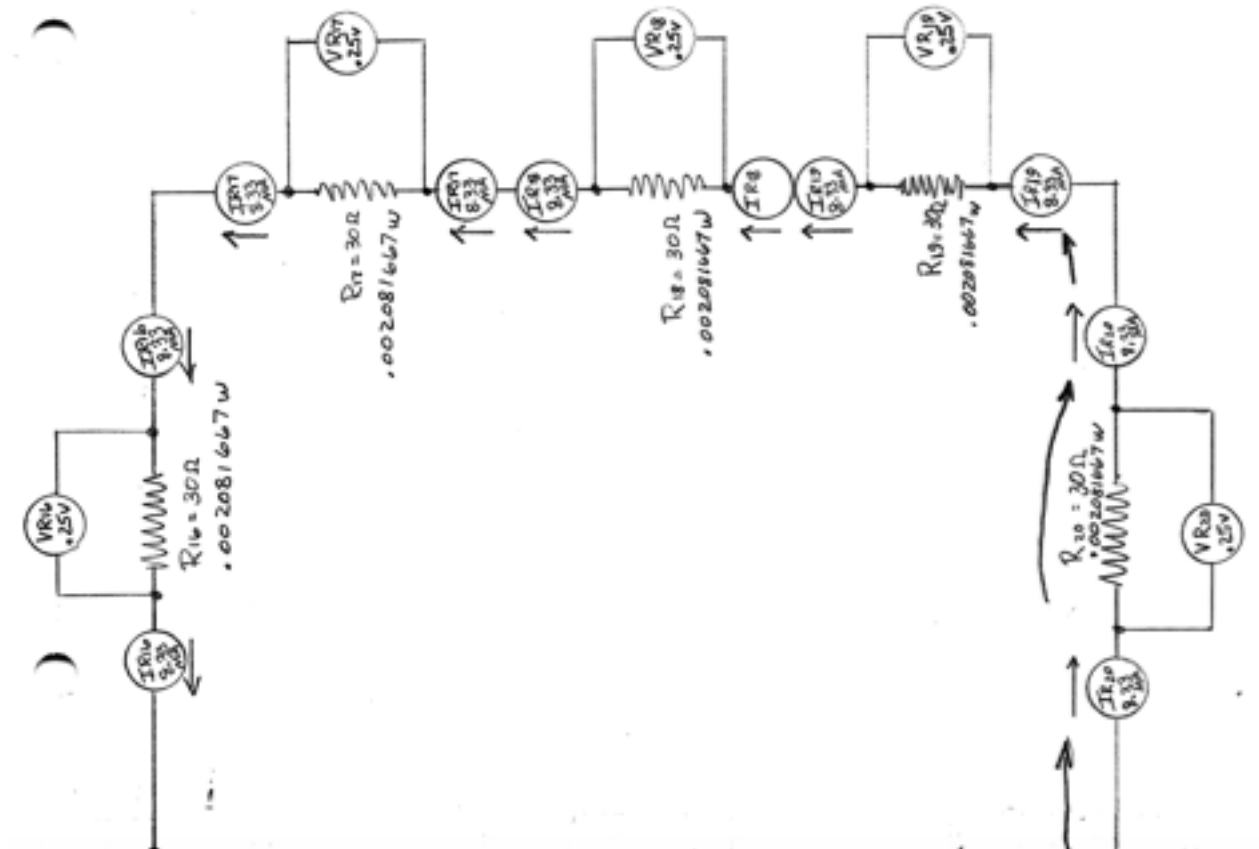



Basic Electricity – Unit 6: Other Basic Circuit Fundamentals

Homework 4

SAFETY DISCLAIMER:

M-SAMC educational resources are in no way meant to be a substitute for occupational safety and health standards. No guarantee is made to resource thoroughness, statutory or regulatory compliance, and related media may depict situations that are not in compliance with OSHA and other safety requirements. It is the responsibility of educators/employers and their students/employees, or anybody using our resources, to comply fully with all pertinent OSHA, and any other, rules and regulations in any jurisdiction in which they learn/work. M-SAMC will not be liable for any damages or other claims and demands arising out of the use of these educational resources. By using these resources, the user releases the Multi-State Advanced Manufacturing Consortium and participating educational institutions and their respective Boards, individual trustees, employees, contractors, and sub-contractors from any liability for injuries resulting from the use of the educational resources.

DOL DISCLAIMER:

This product was funded by a grant awarded by the U.S. Department of Labor's Employment and Training Administration. The product was created by the grantee and does not necessarily reflect the official position of the U.S. Department of Labor. The Department of Labor makes no guarantees, warranties, or assurances of any kind, express or implied, with respect to such information, including any information on linked sites and including, but not limited to, accuracy of the information or its completeness, timeliness, usefulness, adequacy, continued availability, or ownership.

RELEVANCY REMINDER:

M-SAMC resources reflect a shared understanding of grant partners at the time of development. In keeping with our industry and college partner requirements, our products are continuously improved. Updated versions of our work can be found here: <http://www.msamc.org/resources.html>.

