




Basic Electricity – Unit 11: Capacitance

Homework 1

Worked Out Example: CIRCUIT ONE

Initial conditions:

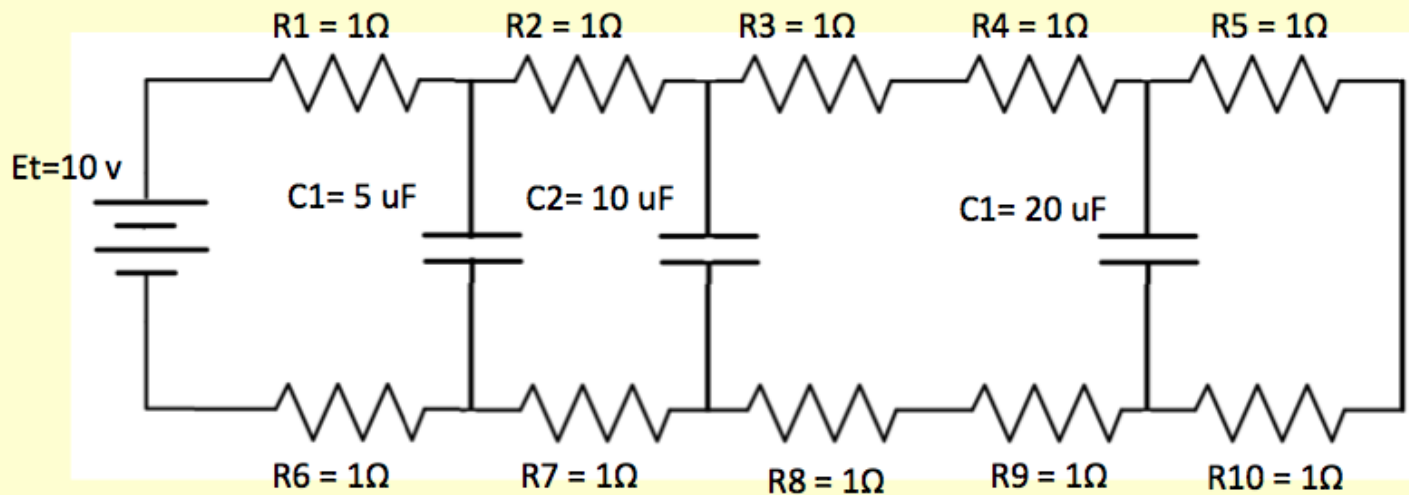Switch 1 open
Capacitors uncharged.
Supply voltage off.







Basic Electricity – Unit 11: Capacitance

Homework 1

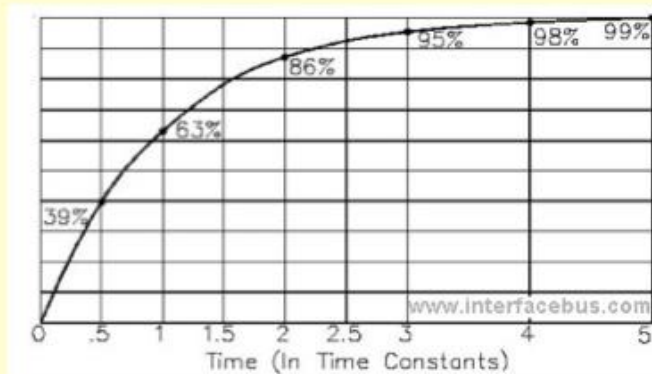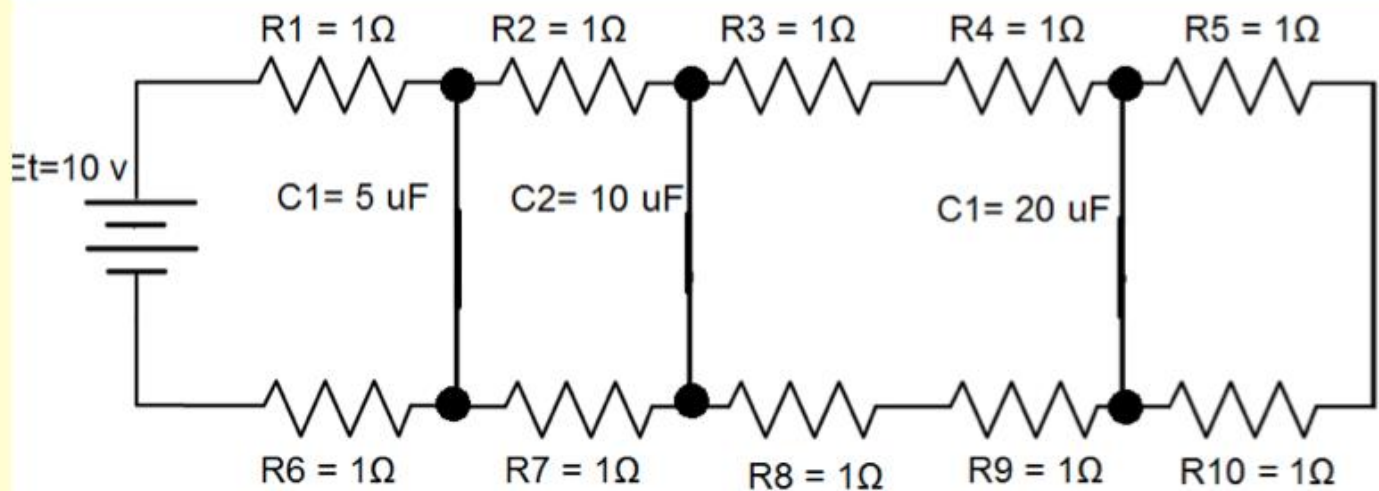As soon as power is applied the capacitors act like a short for current.






Basic Electricity – Unit 11: Capacitance

Homework 1

Steady State Conditions:

Capacitors charged.
Supply voltage on.

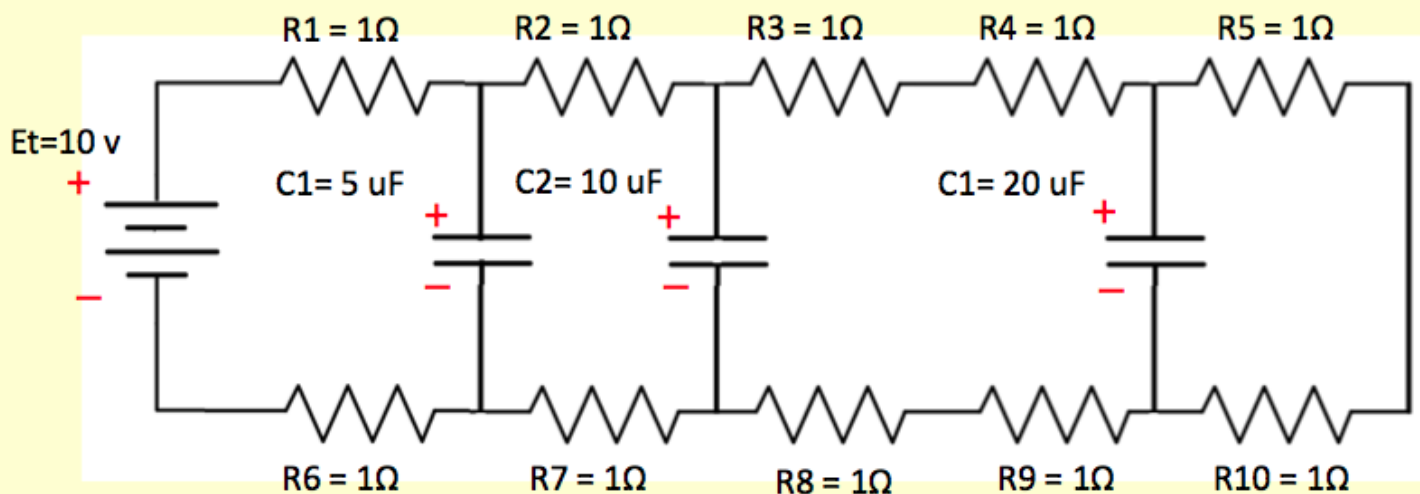

$$R_t = R_1 + R_2 + R_3 + R_4 + R_5 + R_6 + R_7 + R_8 + R_9 + R_{10}$$



Basic Electricity – Unit 11: Capacitance


Homework 1

Capacitors charge.

Current then flows only through resistors.

$$R_t = R_1 + R_2 + R_3 + R_4 + R_5 + R_6 + R_7 + R_8 + R_9 + R_{10} \\ = 10 \Omega$$
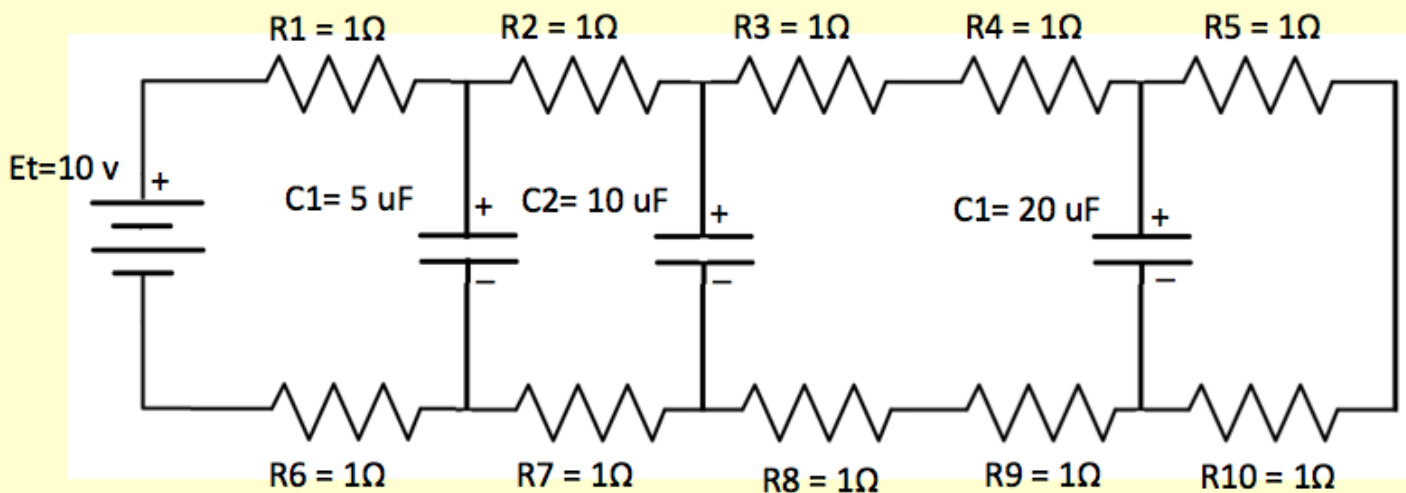
$$I_t = E_t / R_t \\ = 10\text{v} / 10\Omega \\ = 1 \text{ Amp}$$






Basic Electricity – Unit 11: Capacitance

Homework 1

$$\begin{aligned}\text{Voltage across each resistor} &= (I_t)(R) \\ &= (1 \text{ Amp})(1 \Omega) \\ &= 1 \text{ V}\end{aligned}$$

This results in:

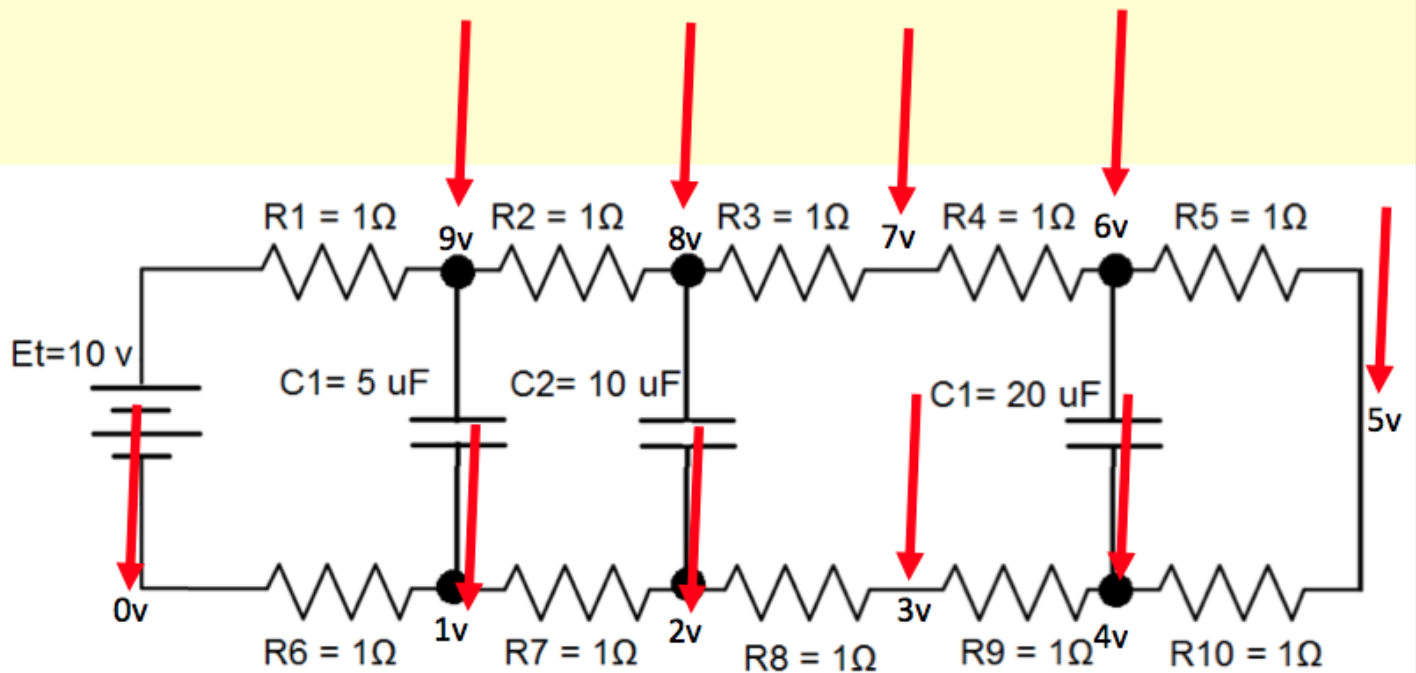



Basic Electricity – Unit 11: Capacitance


Homework 1

The potential difference across each capacitor is as follows:

$$VC1 = 9v - 1v = 8v$$

$$VC2 = 8v - 2v = 6v$$

$$VC3 = 6v - 4v = 2v$$

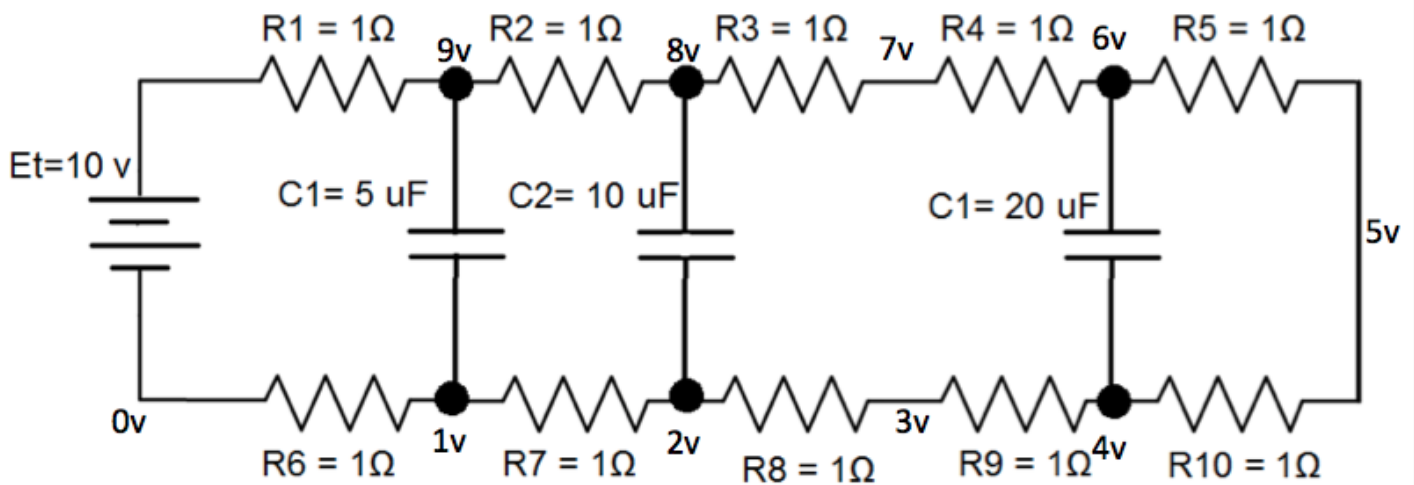



Basic Electricity – Unit 11: Capacitance

Homework 1


$$C = \frac{Q}{V}$$

Where:

C = Capacitance

Q = Charge in micro coulombs = μC

V = Voltage

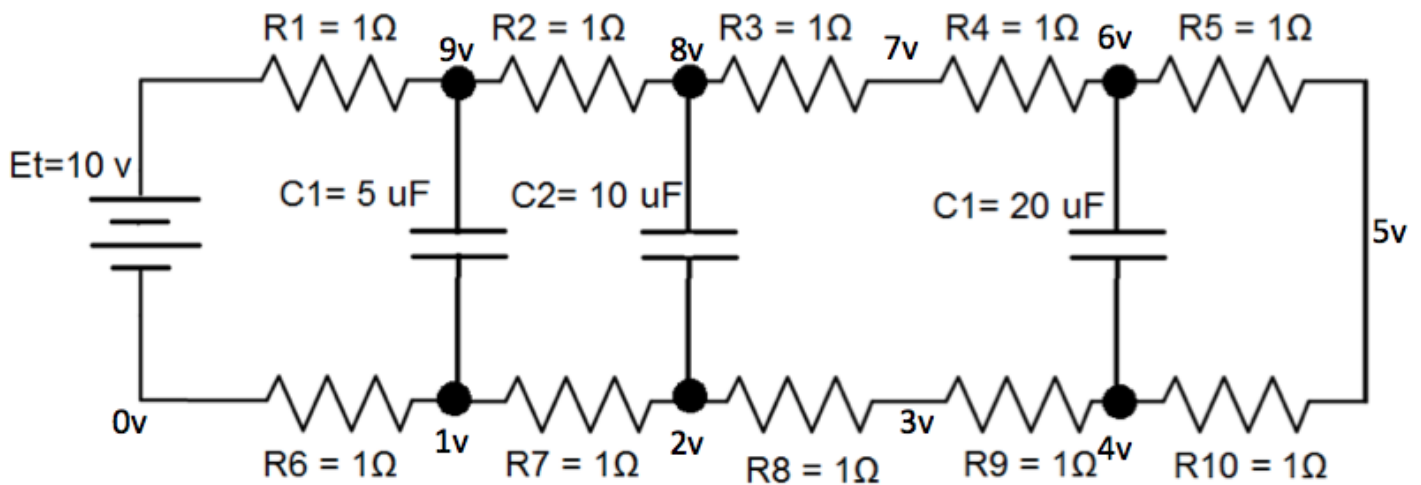



Basic Electricity – Unit 11: Capacitance


Homework 1

$$C = \frac{Q}{V}$$

If we manipulate the formula:

$$Q = CV$$

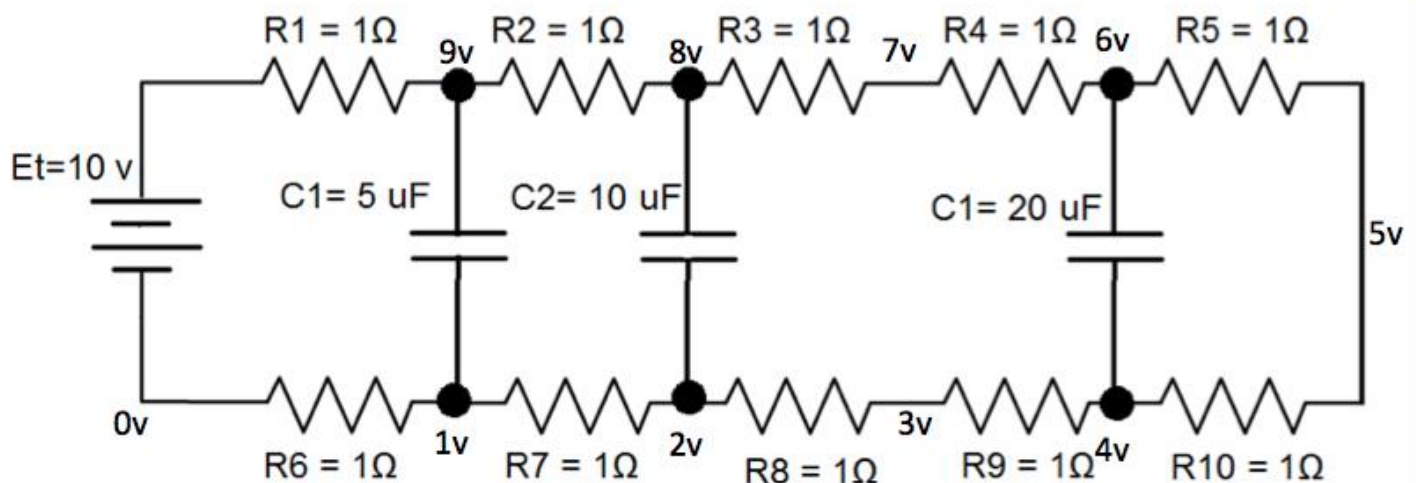We can now solve for each capacitor charge.





Basic Electricity – Unit 11: Capacitance


Homework 1

$$Q = CV$$

$$Q_1 = (C_1)(V_1) = (5\mu\text{F})(8\text{v}) = 40\ \mu\text{C}$$

$$Q_2 = (C_2)(V_2) = (10\mu\text{F})(6\text{v}) = 60\ \mu\text{C}$$
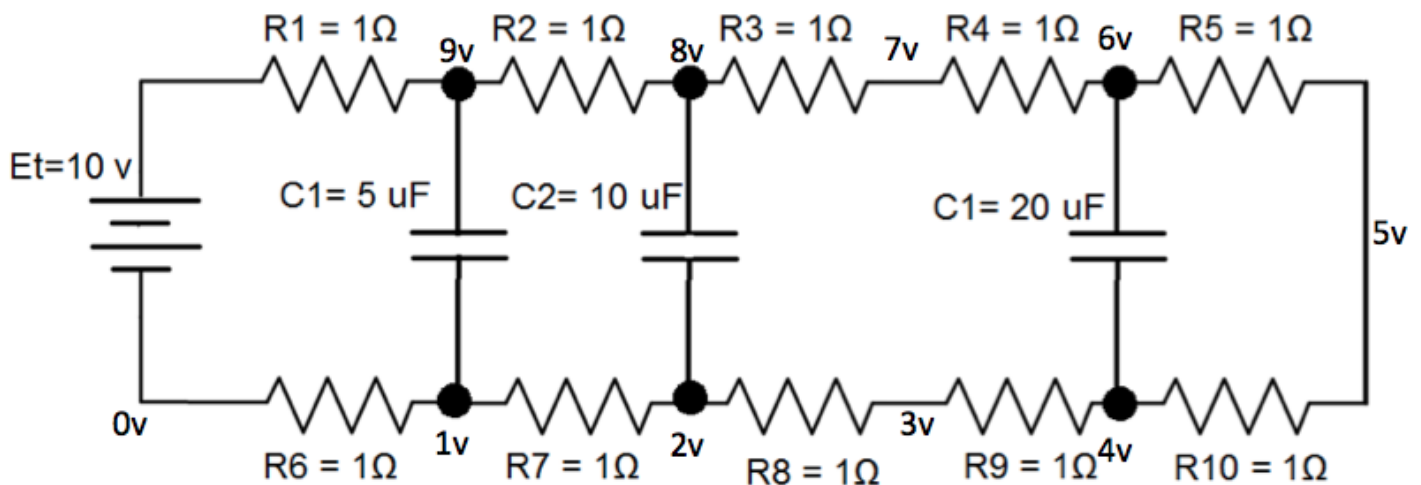
$$Q_3 = (C_3)(V_3) = (20\mu\text{F})(2\text{v}) = 40\ \mu\text{C}$$






Basic Electricity – Unit 11: Capacitance

Homework 1

Homework Instructions: Solve the following DC Capacitive circuit based on the worked out examples.

CIRCUIT 2

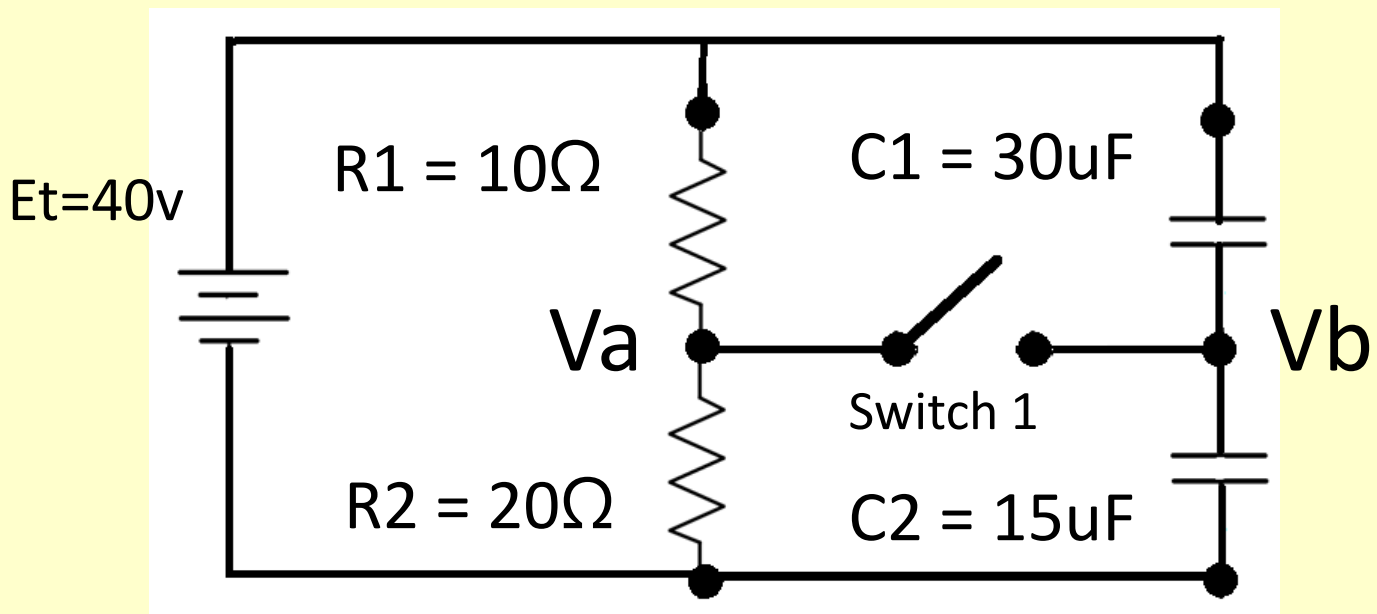

What is V_a , V_b , Q_1 and Q_2
Switch open and switch closed.




Basic Electricity – Unit 11: Capacitance

Homework 1

Homework Solution:

CIRCUIT 2

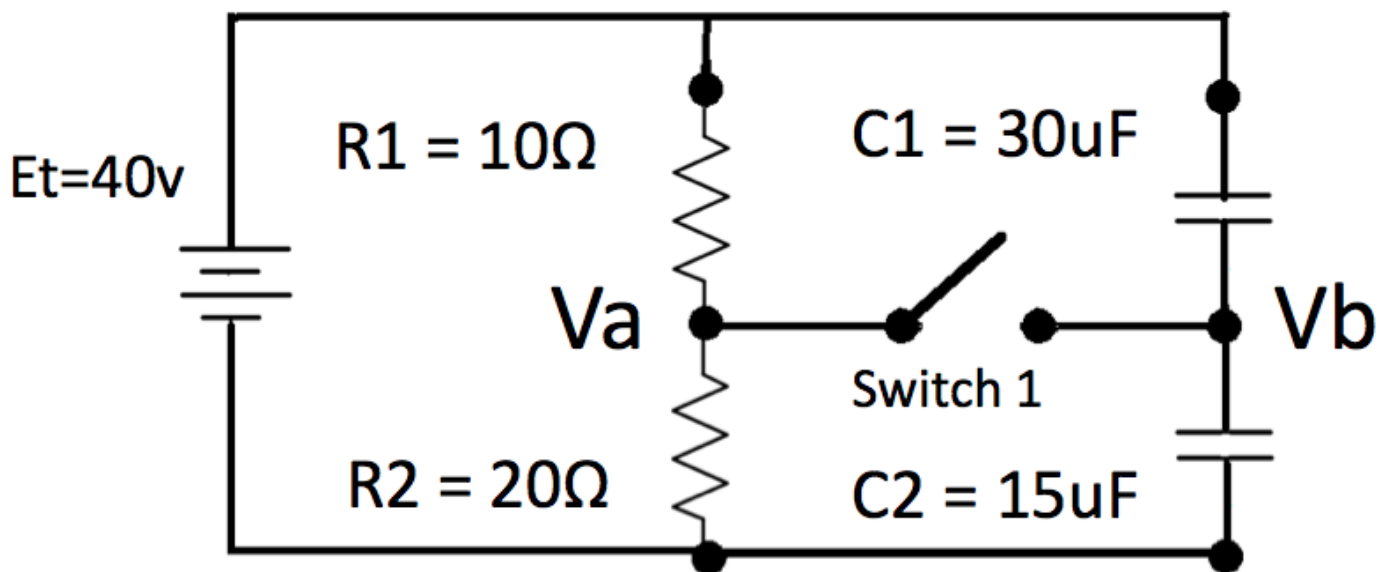

What is V_a , V_b , Q_1 and Q_2
Switch open and switch closed.




Basic Electricity – Unit 11: Capacitance

Homework 1

Initial conditions:

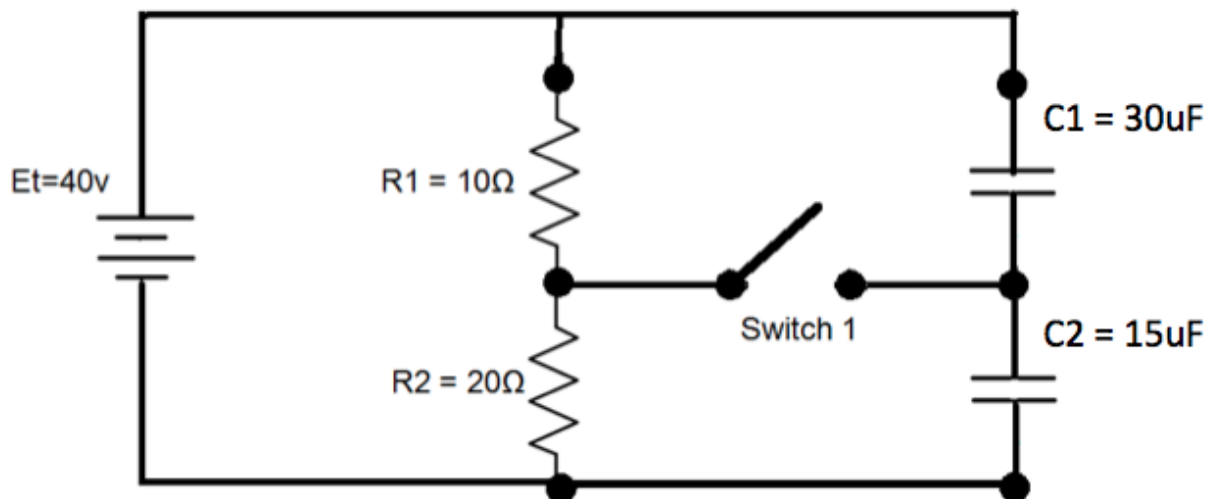Switch 1 open
Capacitors uncharged.
Supply voltage off.






Basic Electricity – Unit 11: Capacitance

Homework 1

Steady State Conditions:

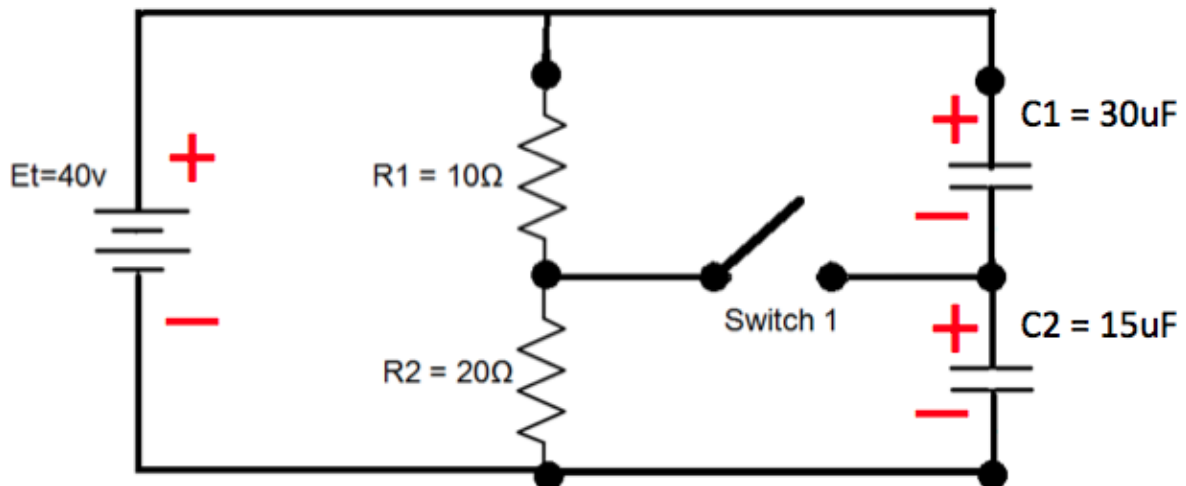Switch 1 open
Capacitors charged.
Supply voltage on.






Basic Electricity – Unit 11: Capacitance

Homework 1

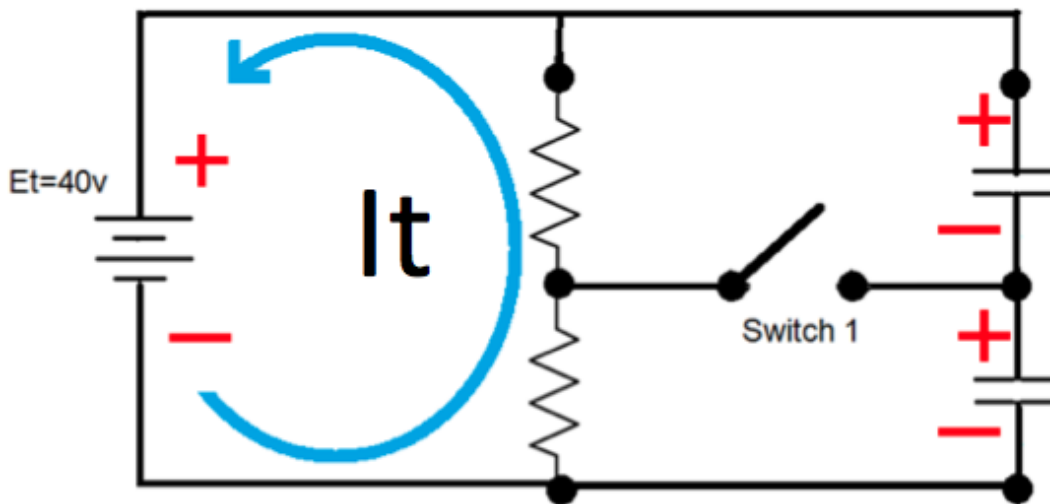Once capacitors are fully charged
current flows **ONLY** through the
resistors.





Basic Electricity – Unit 11: Capacitance

Homework 1


$$\begin{aligned}R_t &= R_1 + R_2 \\ &= 10\Omega + 20\Omega \\ &= 30\Omega\end{aligned}$$

$$\begin{aligned}I_t &= E_t / R_t \\ &= 40v / 30\Omega \\ &= 1.33 \text{ Amps}\end{aligned}$$



Basic Electricity – Unit 11: Capacitance

Homework 1

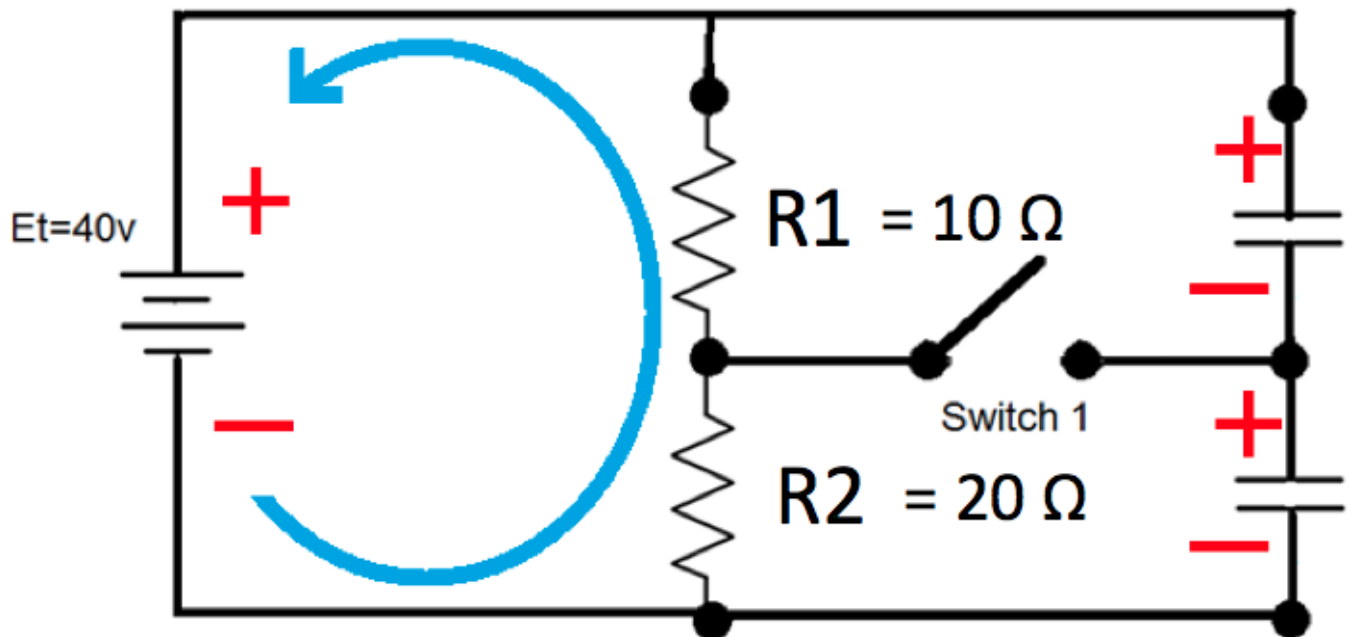


$$VR1 = (1.333A)(10\Omega) = 13.333 \text{ V}$$

$$VR2 = (1.333A)(20\Omega) = 26.667 \text{ V}$$



Basic Electricity – Unit 11: Capacitance


Homework 1

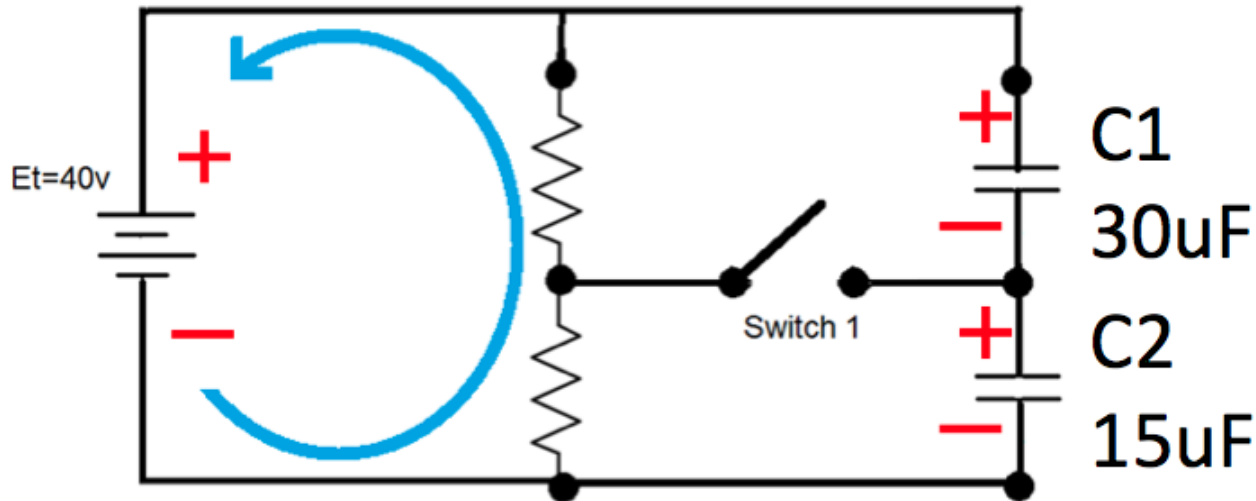

$$Q = CV$$

Using the product sum formula for capacitors in series:

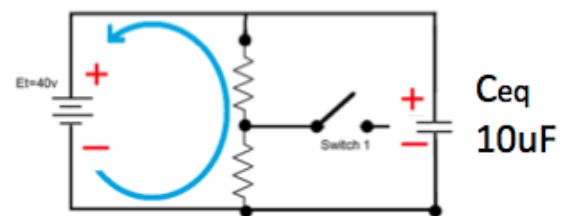
$$\begin{aligned} C_{eq} &= [(C1)(C2)]/[C1+C2] \\ &= 450/45 \\ &= 10 \mu\text{F} \end{aligned}$$





Basic Electricity – Unit 11: Capacitance

Homework 1

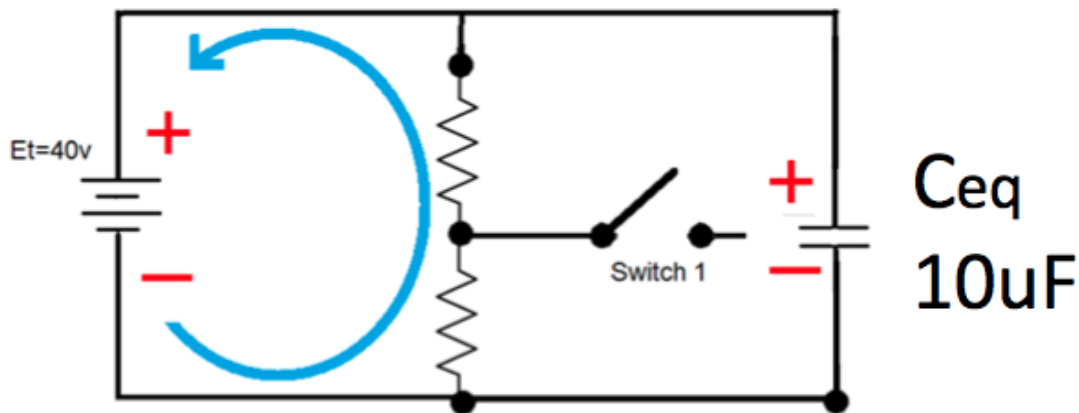

The total charge across C_{eq} is worked out as follows:

$$\begin{aligned} Q_{\text{total}} &= (C_{eq})(V_t) \\ &= (10\mu\text{F})(40\text{v}) \\ &= 400 \mu\text{C} = 400 \text{ micro Coulombs} \end{aligned}$$



Basic Electricity – Unit 11: Capacitance

Homework 1

The charge across each series capacitor is the same as the charge across C_{eq} .

The voltages $V_{C1} + V_{C2}$ will add up.



Basic Electricity – Unit 11: Capacitance

Homework 1

$$Q = CV$$

$$\begin{aligned}VC1 &= QC1/C1 \\ &= 400 \text{ uC} / 30\text{uF} \\ &= 13.333 \text{ V}\end{aligned}$$

$$\begin{aligned}VC2 &= QC2/C2 \\ &= 400 \text{ uC} / 15\text{uF} \\ &= 26.667 \text{ V}\end{aligned}$$



Basic Electricity – Unit 11: Capacitance


Homework 1

In order for the same charge to be placed on a smaller capacitor the voltage across the capacitor must be greater.



Basic Electricity – Unit 11: Capacitance

Homework 1

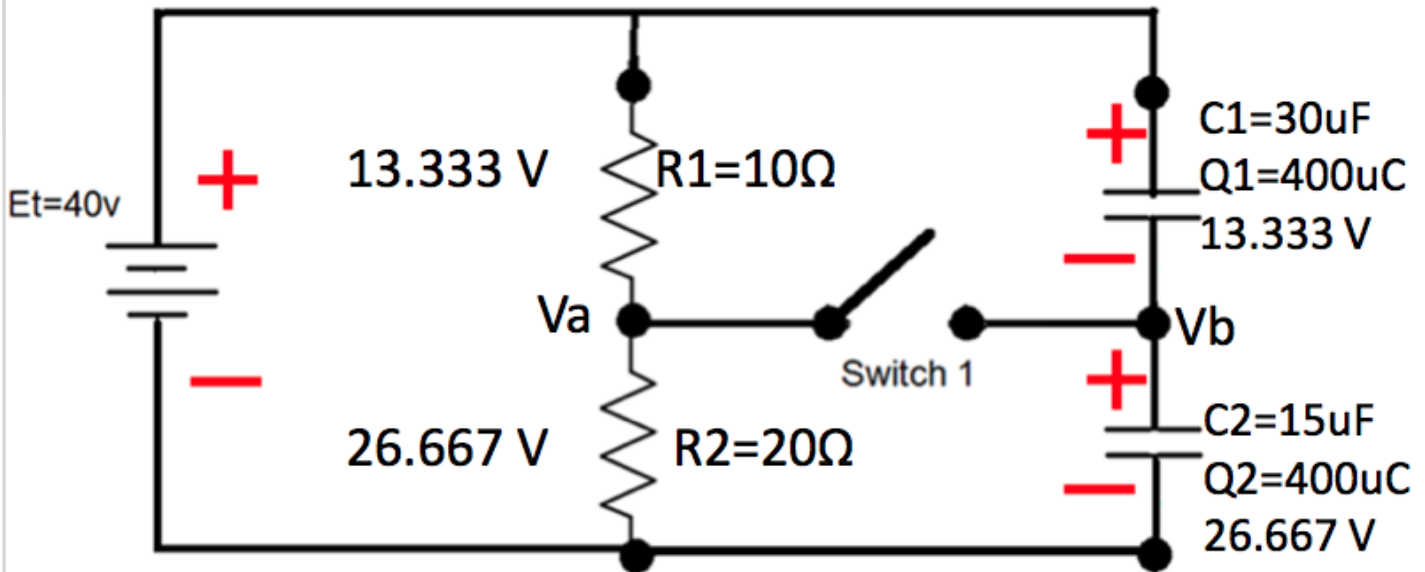

$$V_a = 26.667 \text{ V}$$

$$V_b = 26.667 \text{ V}$$





**Multi-State
Advanced Manufacturing
Consortium**

US DOL SPONSORED TAACCCT GRANT: TC23767
PRIMARY DEVELOPER: Jim Blair – Henry Ford College

RELEASE DATE 2/22/2016

VERSION v 001

PAGE 23 of 25

Basic Electricity – Unit 11: Capacitance

Homework 1


Switch Closed





Basic Electricity – Unit 11: Capacitance

Homework 1

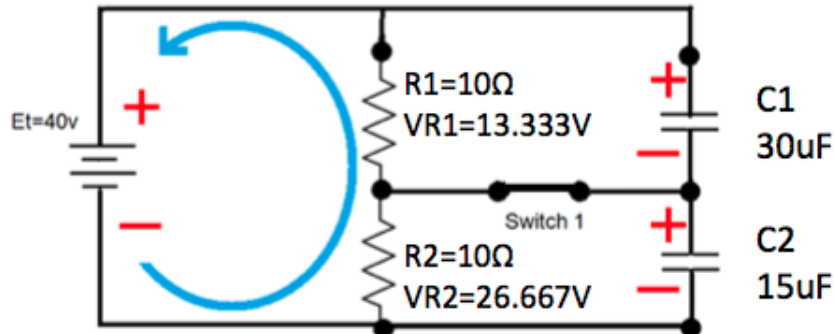

C1 and C2 are no longer in series with each other.

$$Q1 = C1V1 = (30\mu\text{F})(13.333\text{V}) = 0.00039999 \mu\text{C}$$

$$Q2 = C2V2 = (15\mu\text{F})(26.667\text{V}) = 0.000400005 \mu\text{C}$$

$$\text{Total Charge on both capacitors} = 0.000799995 \mu\text{C}$$



Basic Electricity – Unit 11: Capacitance

Homework 1

SAFETY DISCLAIMER:

M-SAMC educational resources are in no way meant to be a substitute for occupational safety and health standards. No guarantee is made to resource thoroughness, statutory or regulatory compliance, and related media may depict situations that are not in compliance with OSHA and other safety requirements. It is the responsibility of educators/employers and their students/employees, or anybody using our resources, to comply fully with all pertinent OSHA, and any other, rules and regulations in any jurisdiction in which they learn/work. M-SAMC will not be liable for any damages or other claims and demands arising out of the use of these educational resources. By using these resources, the user releases the Multi-State Advanced Manufacturing Consortium and participating educational institutions and their respective Boards, individual trustees, employees, contractors, and sub-contractors from any liability for injuries resulting from the use of the educational resources.

DOL DISCLAIMER:

This product was funded by a grant awarded by the U.S. Department of Labor's Employment and Training Administration. The product was created by the grantee and does not necessarily reflect the official position of the U.S. Department of Labor. The Department of Labor makes no guarantees, warranties, or assurances of any kind, express or implied, with respect to such information, including any information on linked sites and including, but not limited to, accuracy of the information or its completeness, timeliness, usefulness, adequacy, continued availability, or ownership.

RELEVANCY REMINDER:

M-SAMC resources reflect a shared understanding of grant partners at the time of development. In keeping with our industry and college partner requirements, our products are continuously improved. Updated versions of our work can be found here: <http://www.msamc.org/resources.html>.

