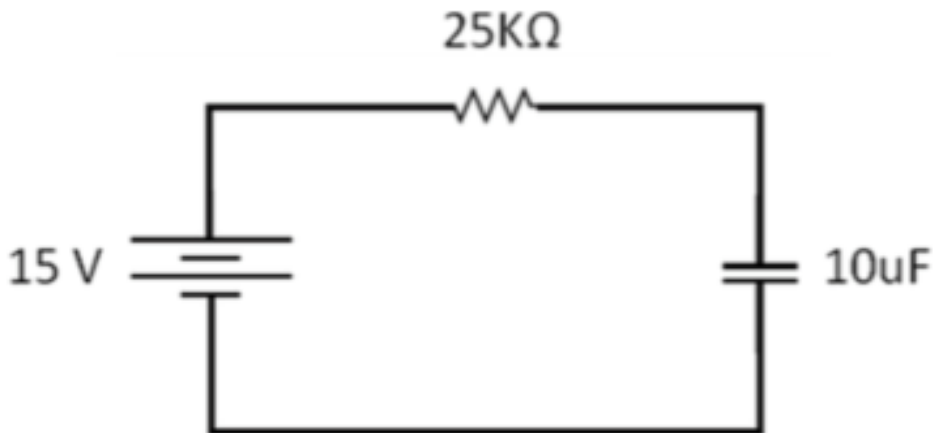






Basic Electricity – Unit 11: Capacitance

Test 2 – RC Test

Use the following circuit and calculate problems 1-5.



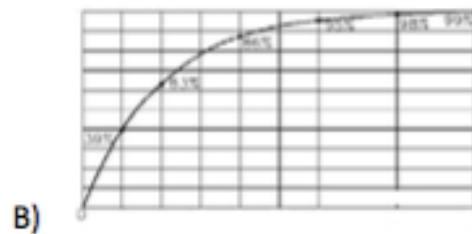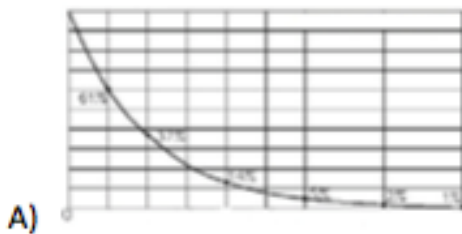1. What is 1 time constant equal to? _____
2. Which of the following graphics show the voltage charging across the capacitor?



3. Use the given circuit and graphics. What will the voltage across the capacitor be after 2 time constants?

4. How much current flows in the circuit at the instant the switch is closed?

5. Once the capacitor is fully charged, how much current flows in the circuit?






Basic Electricity – Unit 11: Capacitance

Test 2 – RC Test

Use the following circuit to answer 6-20

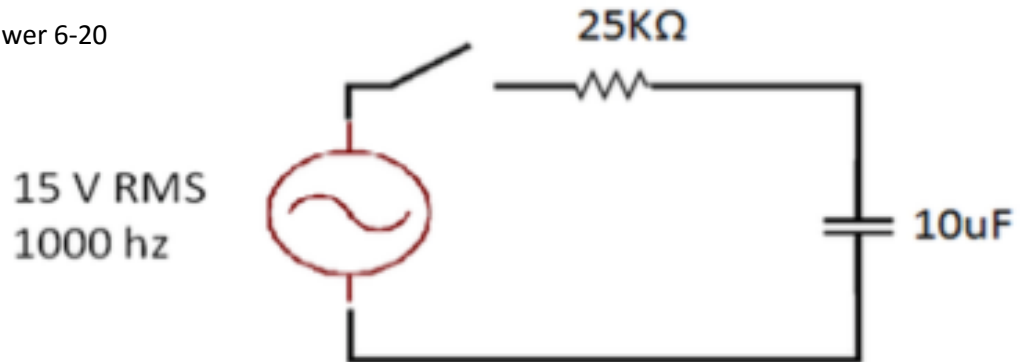


6. What is X_c ? _____
7. What is Z ? _____
8. What is R ? _____
9. What is V_t ? _____
10. What is V_R ? _____
11. What is V_{X_c} ? _____
12. What is the power consumed by the resistor? _____
13. What is the power consumed by X_c ? _____
14. What is the value of theta? _____
15. What is the total power? _____
16. What is the phase angle? _____
17. What are the units of power for resistance? _____
18. What are the units of power for X_c ? _____
19. What are the units of power for total power? _____
20. What is the total current? _____




Basic Electricity – Unit 11: Capacitance

Test 2 – RC Test

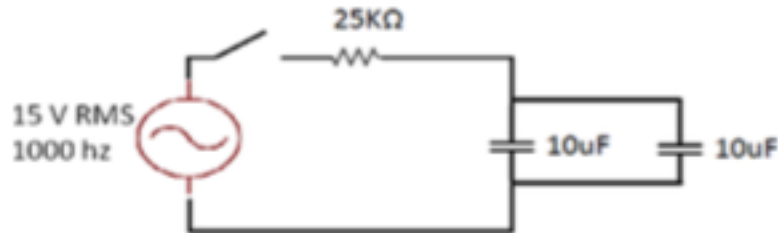21. What is X_c of the following circuit? _____



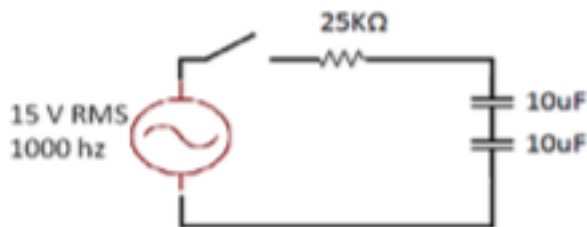22. What is X_c of the following circuit? _____



23. Which of the following are true?

- a) $C = V/Q$
- b) $C = 1/V$
- c) $Q = 1/C$
- d) $Q = CV$
- e) None of these

24. Capacitors allow AC current to flow?

- a) true
- b) false

25. Capacitors allow DC current to flow after the capacitor is charged?

- a) true
- b) false





Basic Electricity – Unit 11: Capacitance

Test 2 – RC Test

Answers:

1. What is 1 time constant equal to? **250 milli seconds**
2. Which of the following graphics show the voltage charging across the capacitor? **B**
3. Use the given circuit and graphics.
What will the voltage across the capacitor be after 2 time constants? **12.9 volts**
4. How much current flows in the circuit at the instant the switch is closed? **.0006 A = .6 mA = 600 uA**
5. Once the capacitor is fully charged, how much current flows in the circuit? **0 amps**
6. What is X_c ? **$X_c = 15.916 \Omega$**
7. What is Z ? **$Z = 25000.00507 \Omega$**
8. What is R ? **25000Ω**
9. What is V_t ? **$15 V$**
10. What is V_R ? **$14.99999696 V$**
11. What is V_{Xc} ? **$V_{Xc} = .009549598 V$**
12. What is the power consumed by the resistor? **$P_{true} = .008999996 \text{ watts}$**
13. What is the power consumed by X_c ? **$P_R = 00000573 \text{ VARS}$**
14. What is the value of theta? **$\Phi = .03647678^\circ$**
15. What is the total power? **$P_{apparent} = .008999998 \text{ VA}$**
16. What is the phase angle? **$\Phi = .03647678^\circ$**
17. What are the units of power for resistance? **Watts**
18. What are the units of power for X_c ? **Volt Amp Reactance = VARS**
19. What are the units of power for total power? **VA = Volt Amps**
20. What is the total current? **$I_t = .0006 \text{ Amps}$**
21. What is X_c of the following circuit? **7.957747Ω**
22. What is X_c of the following circuit? **31.8309886Ω**
23. Which of the following are true? **d) $Q = CV$**
24. Capacitors allow AC current to flow? **a) true**
25. Capacitors allow DC current to flow after the capacitor is charged? **b) false**





Basic Electricity – Unit 11: Capacitance

Test 2 – RC Test

SAFETY DISCLAIMER:

M-SAMC educational resources are in no way meant to be a substitute for occupational safety and health standards. No guarantee is made to resource thoroughness, statutory or regulatory compliance, and related media may depict situations that are not in compliance with OSHA and other safety requirements. It is the responsibility of educators/employers and their students/employees, or anybody using our resources, to comply fully with all pertinent OSHA, and any other, rules and regulations in any jurisdiction in which they learn/work. M-SAMC will not be liable for any damages or other claims and demands arising out of the use of these educational resources. By using these resources, the user releases the Multi-State Advanced Manufacturing Consortium and participating educational institutions and their respective Boards, individual trustees, employees, contractors, and sub-contractors from any liability for injuries resulting from the use of the educational resources.

DOL DISCLAIMER:

This product was funded by a grant awarded by the U.S. Department of Labor's Employment and Training Administration. The product was created by the grantee and does not necessarily reflect the official position of the U.S. Department of Labor. The Department of Labor makes no guarantees, warranties, or assurances of any kind, express or implied, with respect to such information, including any information on linked sites and including, but not limited to, accuracy of the information or its completeness, timeliness, usefulness, adequacy, continued availability, or ownership.

RELEVANCY REMINDER:

M-SAMC resources reflect a shared understanding of grant partners at the time of development. In keeping with our industry and college partner requirements, our products are continuously improved. Updated versions of our work can be found here: <http://www.msamc.org/resources.html>.

