




## Basic Electricity – Unit 18: Thevenin's Theorem

### Thevenin's Theorem Worksheet - ANSWERS


ET 29 Construct and debug a series/parallel electrical circuit.  
Apply Thevenin's Theorem to simplify the circuit for analysis.  
Verify the results through practical substitution and measurement.

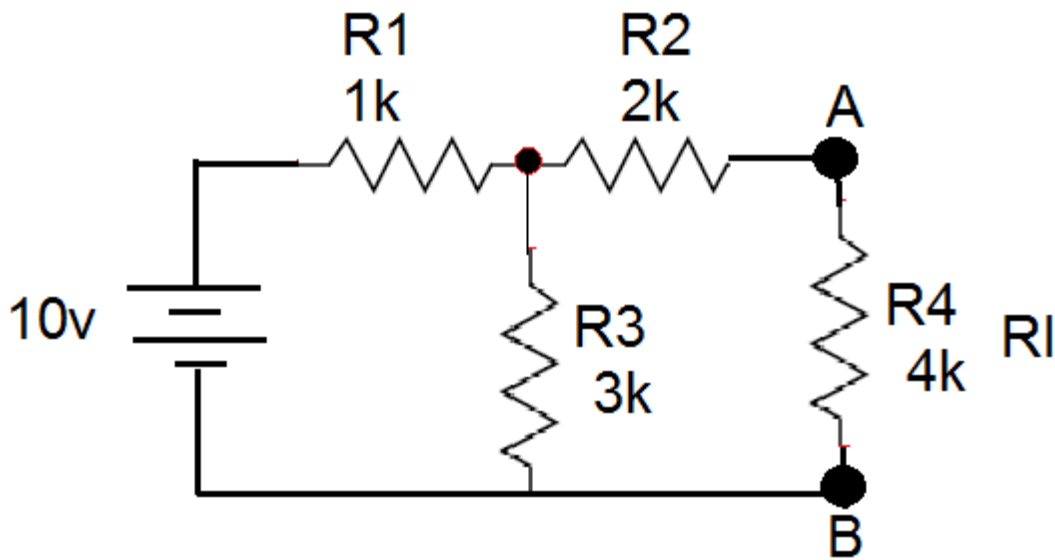1. Find values using Thevenin's Method.

Find  $V_{TH}$ ,  $R_{TH}$  and the load current flowing through and load voltage across the load resistor.  
Thevenin's Theorem



1. Open the 4kΩ load resistor.

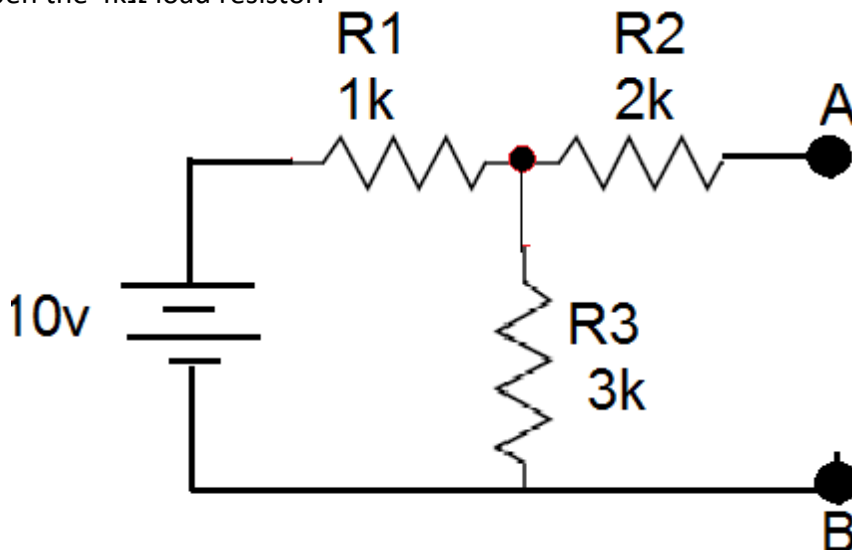




## Basic Electricity – Unit 18: Thevenin's Theorem
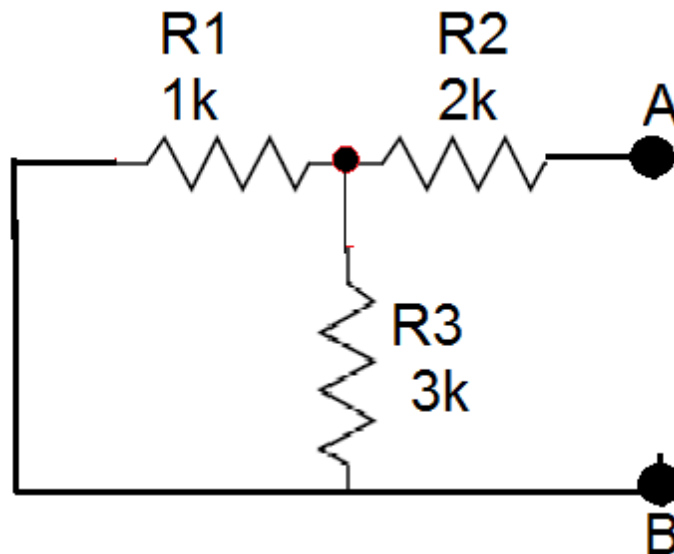
### *Thevenin's Theorem Worksheet - ANSWERS*

- Calculate / measure the Open Circuit Voltage. This is the Thevenin Voltage ( $V_{TH}$ ).
- The load has been removed. The circuit became an open circuit as shown.
- Now we have to calculate the Thevenin's Voltage. Since 2.5mA of current flows in both the 1k $\Omega$  and the 3k $\Omega$  resistors. This is so since this is a series circuit because current will not flow in the 2k $\Omega$  resistor as it is open.
- So 7.5V (2.5mA x 3k $\Omega$ ) will appear across the 3k $\Omega$  resistor.
- Current is not flowing through the 2k $\Omega$  resistor as it is open circuit, but the 2k $\Omega$  resistor is in parallel with 3k resistor.
- The same voltage (i.e. 7.5V) will appear across the 2k $\Omega$  resistor as 3k $\Omega$  resistor. Therefore 7.5V will appear across the AB terminals. So,  $V_{TH} = 7.5V$
- Open Current Sources and Short Voltage Sources.






## Basic Electricity – Unit 18: Thevenin's Theorem

### Thevenin's Theorem Worksheet - ANSWERS

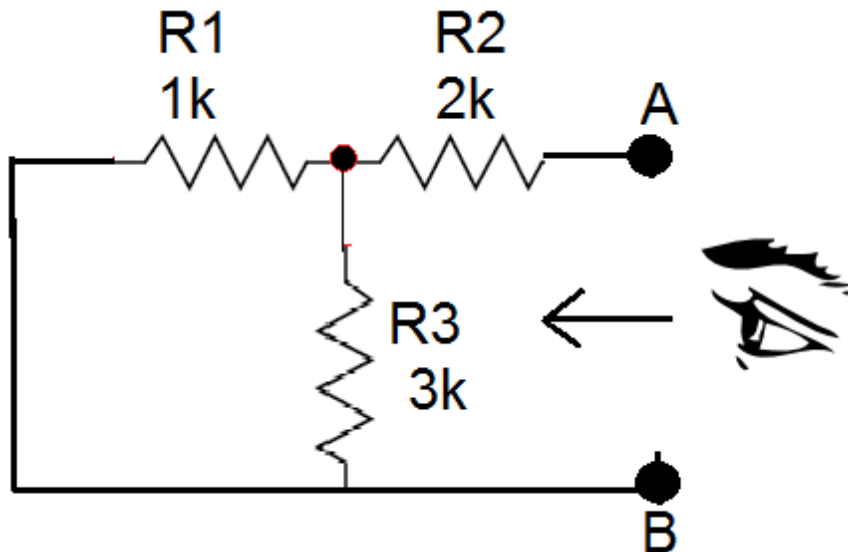9. Calculate /measure the Open Circuit Resistance. This is the Thevenin Resistance ( $R_{TH}$ )
10. The 10V DC source has been reduced to zero.
11.  $R_{TH} = 2k\Omega + [(1k\Omega \times 3k\Omega) / (1k\Omega + 3k\Omega)]$   
 $R_{TH} = 2k\Omega + 750k\Omega$   
 $R_{TH} = 2750\Omega$




12. Connect the  $R_{TH}$  in series with Voltage Source  $V_{TH}$  and re-connect the load resistor.



## Basic Electricity – Unit 18: Thevenin's Theorem
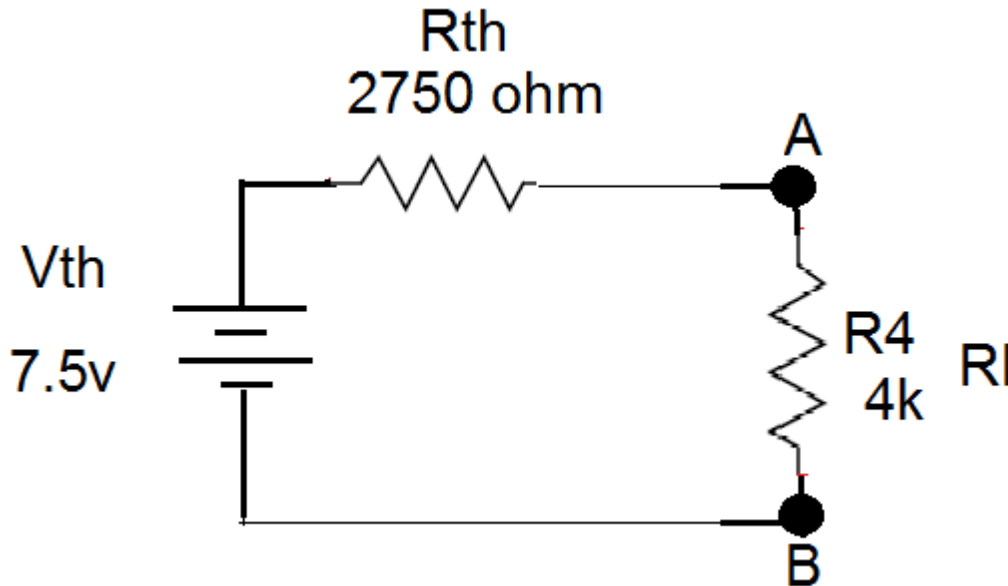
### Thevenin's Theorem Worksheet - ANSWERS



13. Calculate the total load current & load voltage.

$$I_L = V_{TH} / (R_{TH} + R_L)$$
$$= 7.5V / (2750\Omega + 4k\Omega) \rightarrow = 7.5v/6750\Omega$$
$$I_L = 1.111 \text{ mA}$$

And

$$V_L = I_L \times R_L$$
$$V_L = 1.111 \text{ mA} \times 4k\Omega$$
$$V_L = 4.444V$$



---

## **Basic Electricity – Unit 18: Thevenin’s Theorem**

### *Thevenin’s Theorem Worksheet - ANSWERS*

---

#### **SAFETY DISCLAIMER:**

M-SAMC educational resources are in no way meant to be a substitute for occupational safety and health standards. No guarantee is made to resource thoroughness, statutory or regulatory compliance, and related media may depict situations that are not in compliance with OSHA and other safety requirements. It is the responsibility of educators/employers and their students/employees, or anybody using our resources, to comply fully with all pertinent OSHA, and any other, rules and regulations in any jurisdiction in which they learn/work. M-SAMC will not be liable for any damages or other claims and demands arising out of the use of these educational resources. By using these resources, the user releases the Multi-State Advanced Manufacturing Consortium and participating educational institutions and their respective Boards, individual trustees, employees, contractors, and sub-contractors from any liability for injuries resulting from the use of the educational resources.

#### **DOL DISCLAIMER:**

This product was funded by a grant awarded by the U.S. Department of Labor’s Employment and Training Administration. The product was created by the grantee and does not necessarily reflect the official position of the U.S. Department of Labor. The Department of Labor makes no guarantees, warranties, or assurances of any kind, express or implied, with respect to such information, including any information on linked sites and including, but not limited to, accuracy of the information or its completeness, timeliness, usefulness, adequacy, continued availability, or ownership.

#### **RELEVANCY REMINDER:**

M-SAMC resources reflect a shared understanding of grant partners at the time of development. In keeping with our industry and college partner requirements, our products are continuously improved. Updated versions of our work can be found here: <http://www.msamc.org/resources.html>.

